

Name \_\_\_\_\_

EE/EET 2240


**Exam #1**

Thursday, February 14, 2019


BA 302 (Pocatello) and TAB 115 (Idaho Falls), 9:30AM – 10:45AM

[closed book – one one-sided 8½"×11" page of notes and calculator allowed, nothing else]

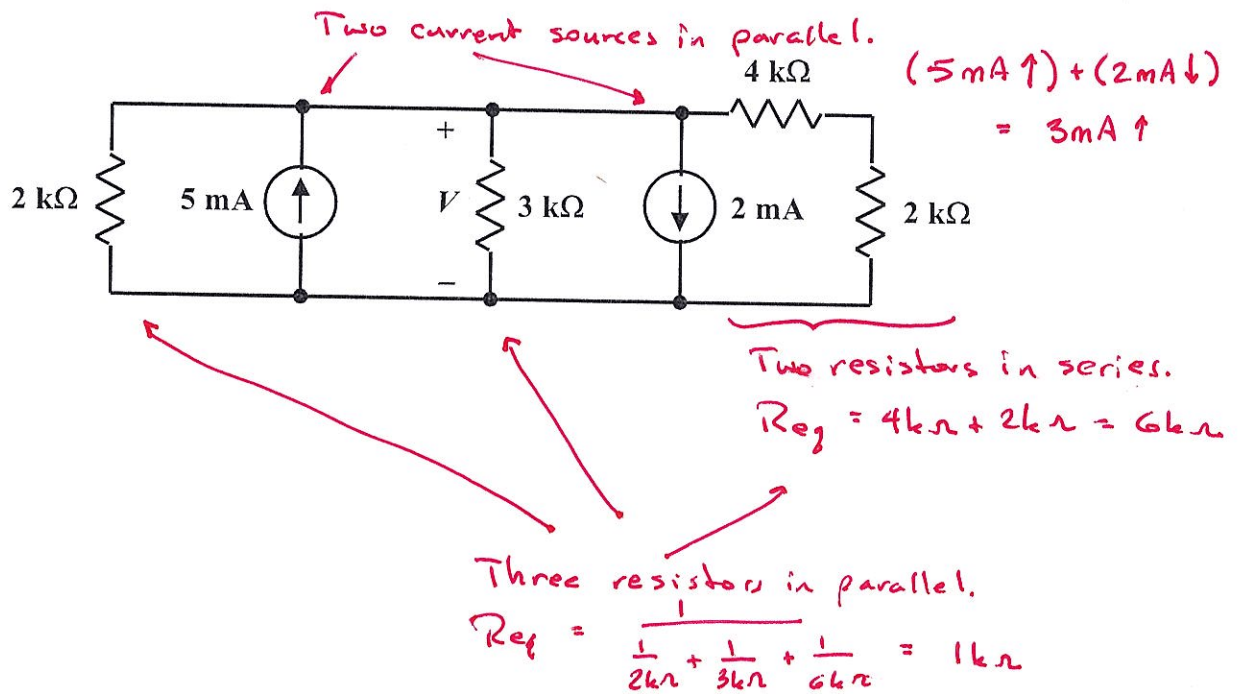1. Determine the value of the voltage,  $V$ . **SHOW YOUR WORK**, and include units and proper signs with your answers.




Equivalent Circuit:

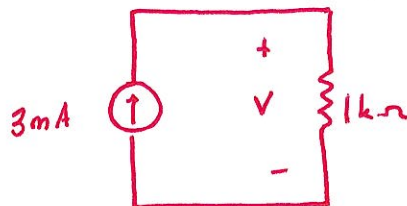

$$V = (1 \text{ k}\Omega) (3 \text{ mA}) = 3 \text{ V}$$

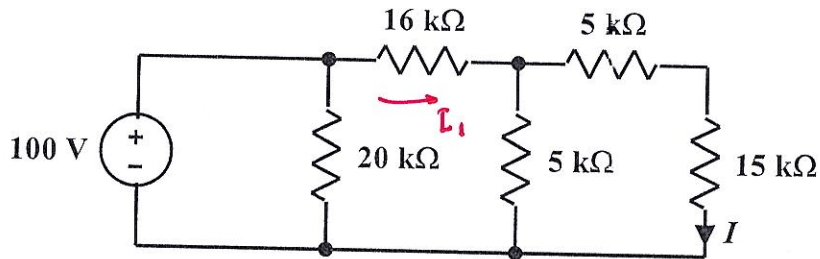2. Determine the value of the current,  $I$ . **SHOW YOUR WORK**, and include units and proper signs with your answers.



Two resistors in series.  
 $R_{eq1} = 5k\Omega + 15k\Omega = 20k\Omega$

Two resistors in parallel.

$$R_{eq2} = \frac{(5k\Omega)(R_{eq1})}{5k\Omega + R_{eq1}} = 4k\Omega$$

Two resistors in series.

$$R_{eq3} = 16k\Omega + R_{eq2} = 20k\Omega$$


From Ohm's Law:

$$I_1 = \frac{100V}{R_{eq3}} = 5mA$$

From the Current Divider Rule:

$$I = \frac{\frac{1}{20k\Omega}}{\frac{1}{5k\Omega} + \frac{1}{20k\Omega}} \cdot I_1 = \frac{1}{5} (5mA) = 1mA$$

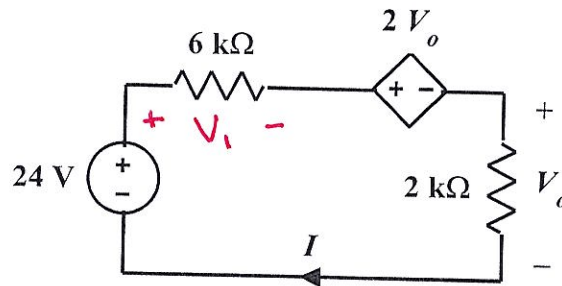3. Determine the value of the current,  $I$ . Then, determine whether the dependent source *delivers* or *absorbs* power, and how much. **SHOW YOUR WORK**, and include units and proper sign with your answer.



$$V_1 = (6\text{ k}\Omega) I \quad (\text{Ohm's Law})$$

$$V_1 + 2V_o + V_o = 24\text{ V} \quad (\text{KVL})$$

$$V_o = (2\text{ k}\Omega) I \quad (\text{Ohm's Law})$$

Substituting:  $(6\text{ k}\Omega) I + 2(2\text{ k}\Omega) I + (2\text{ k}\Omega) I = 24\text{ V}$

or  $(12\text{ k}\Omega) I = 24\text{ V}$

$$\rightarrow I = 2\text{ mA}$$


The voltage of the VCVS is  $2(2\text{ k}\Omega) I = 8\text{ V}$ .

Checking signs and reference directions, we see that the VCVS's voltage and current satisfy the Passive Sign Convention. Therefore, it absorbs

$$P = (8\text{ V})(2\text{ mA}) = 16\text{ mW}$$

4. Use the *nodal analysis method* to formulate a system of simultaneous linear equations representing the circuit shown below. Express the equations in the standard matrix form discussed in class. **SHOW YOUR WORK.**

*Do not attempt to solve the equations.*

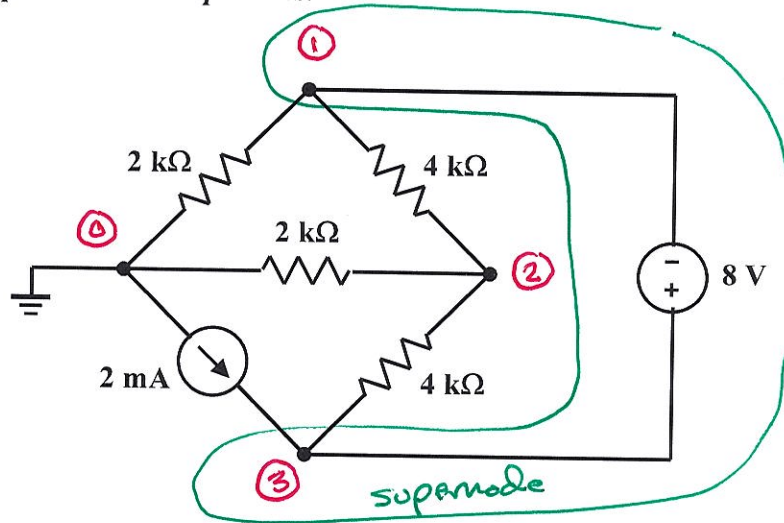

$$V_3 - V_1 = 8 \text{ V} \quad (\text{constraint equation for supernode})$$

$$\frac{V_2 - V_1}{4 \text{ k}\Omega} + \frac{V_2}{2 \text{ k}\Omega} + \frac{V_2 - V_3}{4 \text{ k}\Omega} = 0 \quad (\text{KCL for node 2})$$

$$\frac{V_1}{2 \text{ k}\Omega} + \frac{V_1 - V_2}{4 \text{ k}\Omega} + \frac{V_3 - V_2}{4 \text{ k}\Omega} - 2 \text{ mA} = 0 \quad (\text{KCL for the supernode})$$

In matrix form:

$$\begin{bmatrix} -1 & 0 & 1 \\ -\frac{1}{4000} & \frac{1}{4000} + \frac{1}{2000} + \frac{1}{4000} & -\frac{1}{4000} \\ \frac{1}{2000} + \frac{1}{4000} & -\frac{1}{4000} - \frac{1}{4000} & \frac{1}{4000} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ \frac{2}{1000} \end{bmatrix}$$

or

$$\begin{bmatrix} -1 & 0 & 1 \\ -\frac{1}{4000} & \frac{1}{1000} & -\frac{1}{4000} \\ \frac{3}{4000} & -\frac{1}{2000} & \frac{1}{4000} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ \frac{1}{500} \end{bmatrix}$$