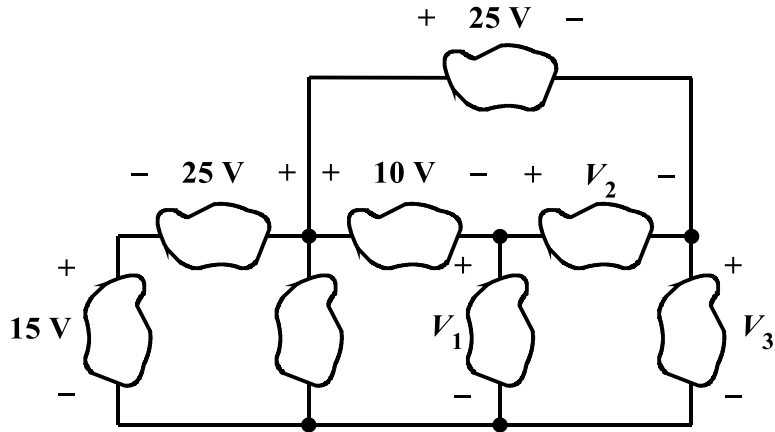


EE/EET 2240
Homework Problem #003

Determine the specified voltages in each circuit.

a. Find V_1 , V_2 and V_3 .



b. Find V_1 and V_2 .

