

EE/EET 2240

Homework Problem 011

Without making any simplifications, develop node equations and express them in the matrix form discussed in class. Note that the resistors are specified in conductance units.

