

Homework Problem #013

Develop node equations and express them in the matrix form discussed in class. Then, using a method of your choosing, solve for V_x .

