

**Homework Problem 015**

Use the nodal analysis method to write nodal equations and express them in the matrix form discussed in class. Then solve the equations to determine  $V_a$ .

