

Homework Problem #015

Use the nodal analysis method to write nodal equations and express them in the matrix form discussed in class. Then solve the equations to determine V_a .

