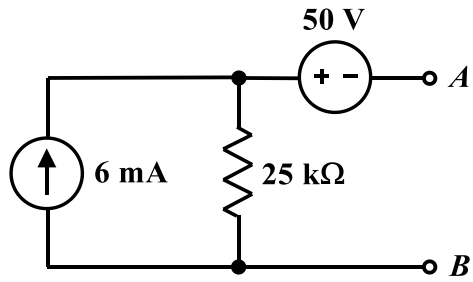


EE/EET 2240  
**Homework Problem #025**



Find the Thévenin equivalent circuit with respect to terminals *A* and *B*.