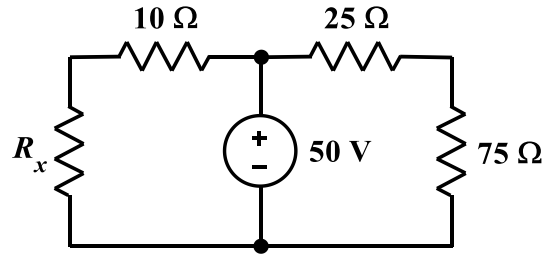


EE/EET 2240
Homework Problem #028



(a) What value of R_x will absorb maximum power from the remainder of the circuit?

(b) How much power will it absorb?