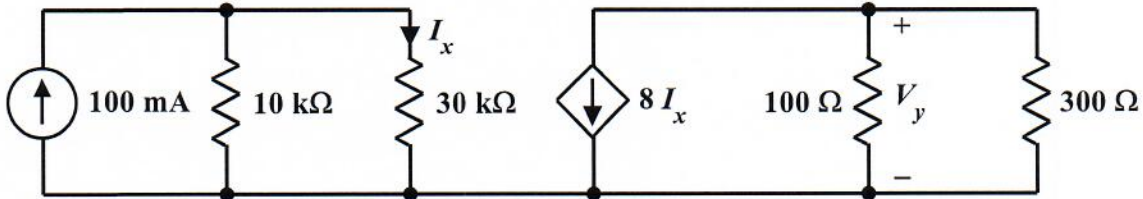


EE/EET 2240
Homework Problem #029



(a) Determine the value of V_y .

$$I_x = \frac{10\text{k}\Omega}{10\text{k}\Omega + 30\text{k}\Omega} \cdot 100\text{mA} = 25\text{mA}$$

$$8I_x = 200\text{mA}$$

$$V_y = - (100\Omega \parallel 300\Omega) (8I_x) = -15\text{V}$$

(b) Does the CCCS *absorb* or *deliver* power? How much?

The CCCS satisfies the PSC, so it

absorbs

$$(8I_x)(|V_y|) = (200\text{mA})(15\text{V}) = 3\text{W}$$