
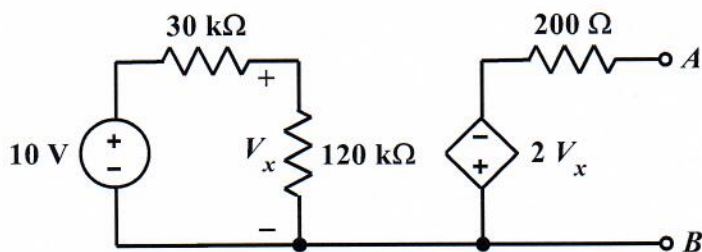


EE/EET 2240  
**Homework Problem 030**

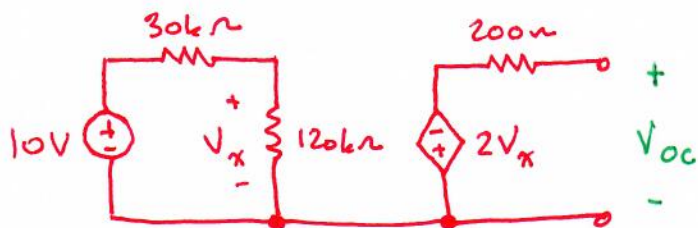


Determine and sketch the Norton equivalent circuit with respect to terminals *A* and *B*.



$$V_x = \frac{120\text{ k}\Omega}{30\text{ k}\Omega + 120\text{ k}\Omega} \cdot 10\text{ V} = 8\text{ V}$$

$$V_{oc} = -2V_x = -16\text{ V}$$

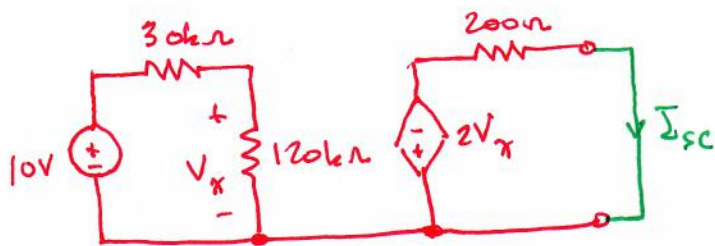

$$V_x = \frac{120\text{ k}\Omega}{30\text{ k}\Omega + 120\text{ k}\Omega} \cdot 10\text{ V} = 8\text{ V}$$

$$I_{sc} = -\frac{2V_x}{200\ \Omega} = -80\text{ mA}$$

$$I_N = I_{sc} = -8\text{ mA}$$

$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{-16\text{ V}}{-80\text{ mA}} = 200\ \Omega$$

