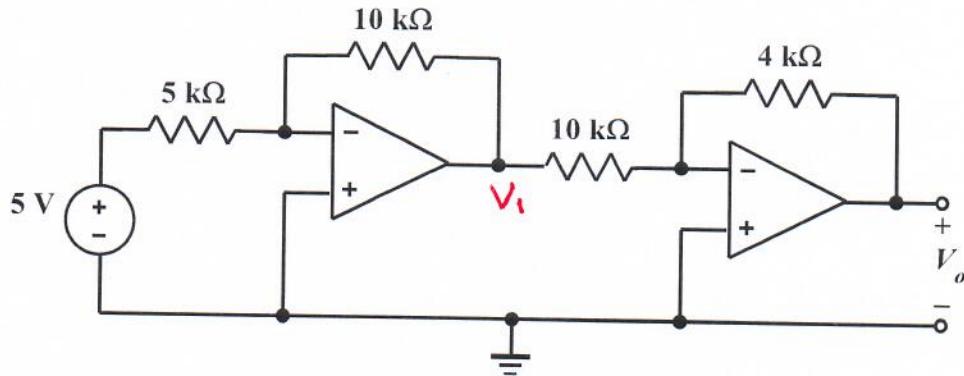


EE/EET 2240  
**Homework Problem #037**



The OpAmps are ideal. Determine the value of  $V_o$ .

$$V_1 = - \frac{10k\Omega}{5k\Omega} \cdot (5V) = -10V$$

$$V_o = - \frac{4k\Omega}{10k\Omega} \cdot V_1 = 4V$$