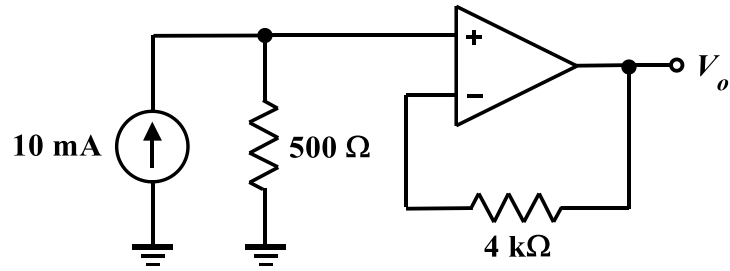


EE/EET 2240  
**Homework Problem #038**



The OpAmp is ideal. Determine the value of  $V_o$ .