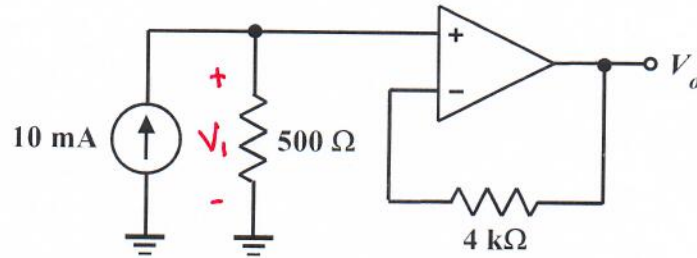


EE/EET 2240  
Homework Problem #038



The OpAmp is ideal. Determine the value of  $V_o$ .

$$V_i = (10\text{mA})(500\Omega) = 5\text{V}$$

$$V_o = V_i = 5\text{V}$$