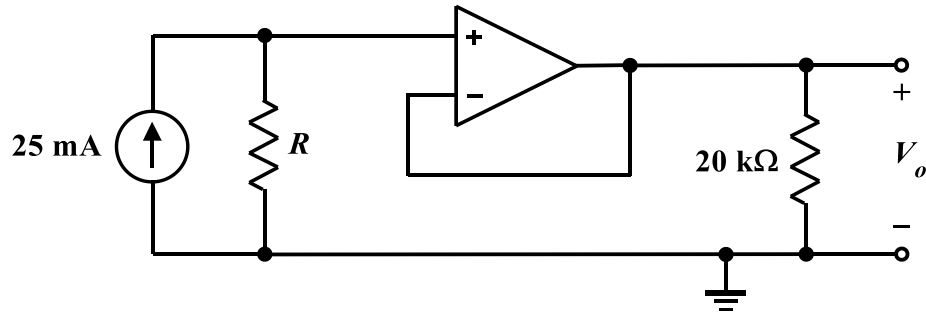


EE/EET 2240
Homework Problem #039



The OpAmp is ideal. Determine the value of R required to make $V_o = 20\text{ V}$.