
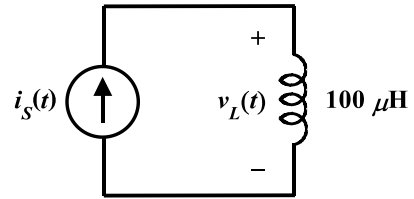


EE/EET 2240
Homework Problem #042

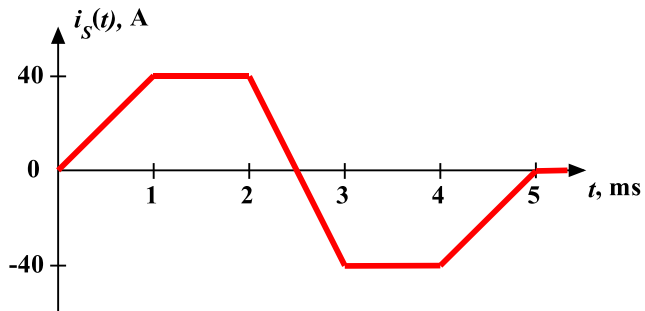

The independent current source is described by the plot shown.

a. Accurately sketch the waveform for the voltage, $v_L(t)$.

b. Accurately sketch the waveform for the power delivered by the independent current source.