
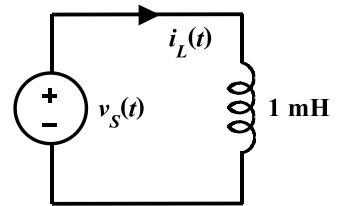


EE/EET 2240
Homework Problem #043

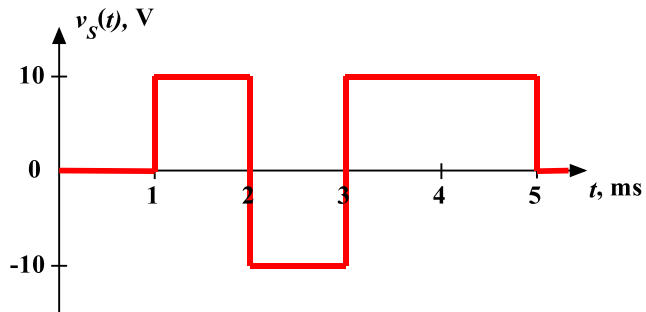

The independent voltage source is described by the plot shown. Given $i_L(0) = 0$ A, accurately sketch the waveform for the current $i_L(t)$ for $0 < t$.