
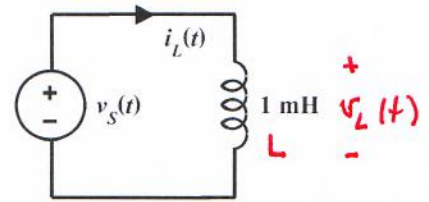


EE/EET 2240
Homework Problem #043

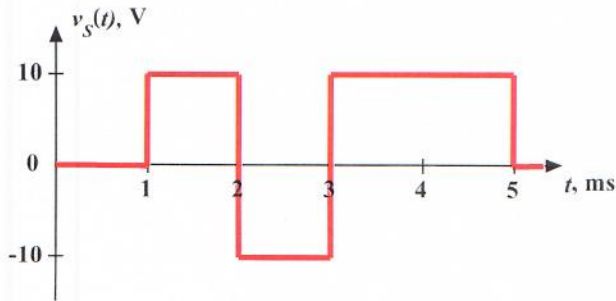

The independent voltage source is described by the plot shown. Given $i_L(0) = 0$ A, accurately sketch the waveform for the current $i_L(t)$ for $0 < t$.

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau = \overset{0}{i_L(0)} + \frac{1}{L} \int_0^t v_L(\tau) d\tau = 1000 \int_0^t v_s(\tau) d\tau$$

$$= \begin{cases} 1000 \int_0^t 0 d\tau = 0 & : 0 < t < 1\text{ms} \\ 0 + 1000 \int_{0.001}^t (10) d\tau = 10000(t - 0.001) \\ & = 10000t - 10 \text{ A} : 1\text{ms} < t < 2\text{ms} \\ 10 + 1000 \int_{0.002}^t (-10) d\tau = 10 - 10000(t - 0.002) \\ & = 30 - 10000t \text{ A} : 2\text{ms} < t < 3\text{ms} \\ 0 + 1000 \int_{0.003}^t (10) d\tau = 10000(t - 0.003) \\ & = 10000t - 30 \text{ A} : 3\text{ms} < t < 5\text{ms} \\ 20 \text{ A} : 5\text{ms} < t \end{cases}$$

