

EE/EET 2240  
**Homework Problem #044**

Determine the equivalent capacitance.

