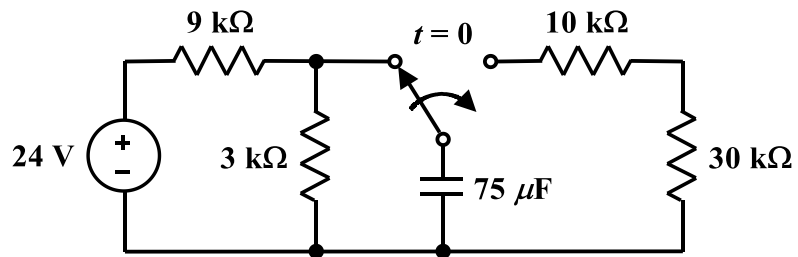


EE/EET 2240
Homework Problem #053



The circuit has reached the DC steady state prior to $t = 0$. Determine the power absorbed by the 10 kΩ resistor for $t \geq 0$.