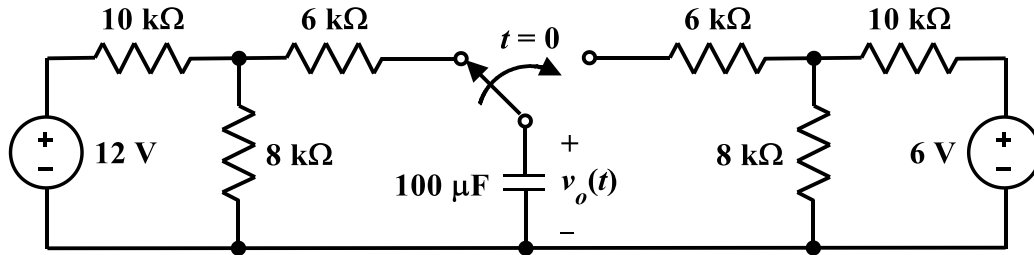


EE/EET 2240  
Problem #054

The circuit is in a DC steady-state condition before the switch is thrown at  $t = 0$ .

- a. Find  $v_o(t)$  for  $t \geq 0$ .



- b. Use PSpice and PROBE to verify your result.