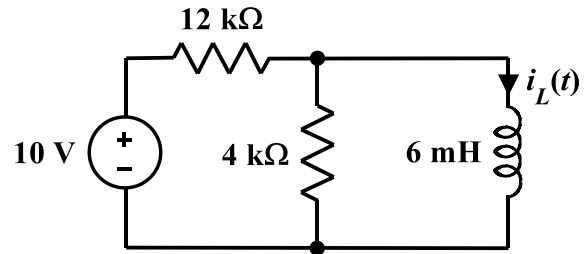


EE/EET 2240  
Problem #055

- a. Given  $i_L(0) = 3 \text{ mA}$ , find  $i_L(t)$  for  $t \geq 0$ .



- b. Use PSpice and PROBE to verify your result.