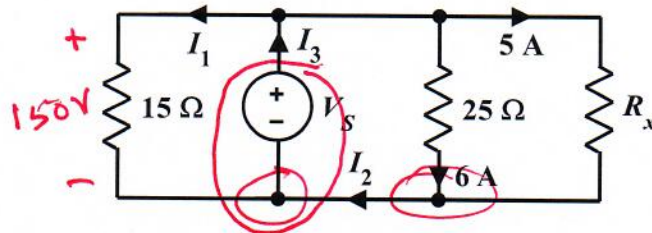


EE/EET 2240
Homework Problem #006

For the circuit shown below:



a. Determine the value of V_s .

150 V

b. Determine the value of I_1 .

10 A

c. Determine the value of I_2 .

11 A

d. Determine the value of I_3 .

21 A

e. Determine the value of R_x .

30 Ω

f. How much power does the 15Ω resistor absorb?

1500 W

g. How much power does the 25Ω resistor absorb?

900 W

h. How much power does R_x absorb?

750 W


i. How much power does the independent voltage source deliver?

3150 W


j. Verify that power is conserved.




$1500 + 900 + 750 = 3150$

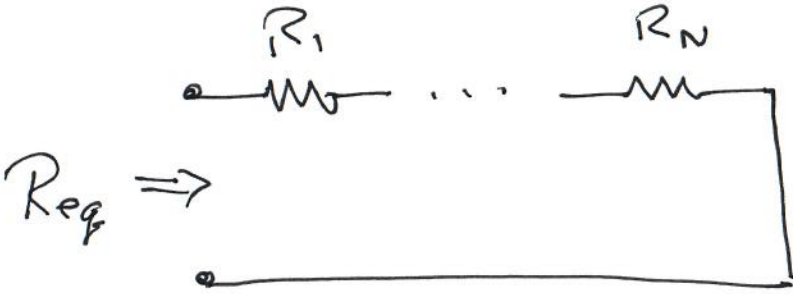

$$R_{eq} = R_1 + \dots + R_N$$

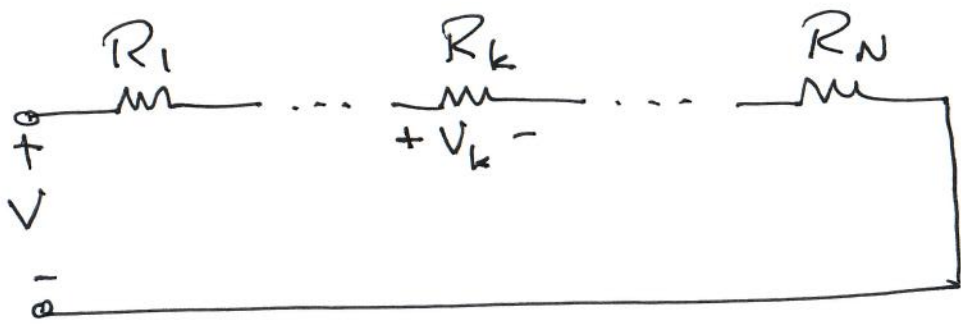
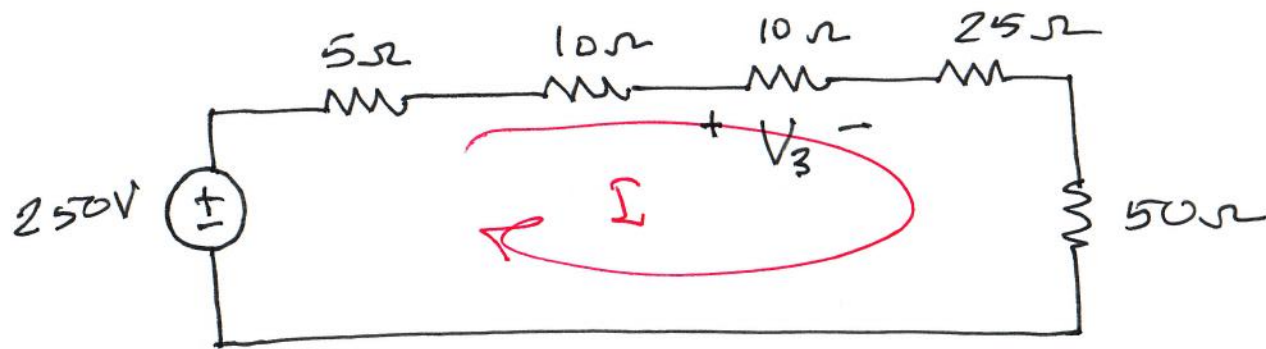
$$\frac{V_k}{V} = \frac{R_k}{R_1 + \dots + R_N} \leftarrow R_{eq}$$




$$\frac{V_3}{250V} = \frac{10\Omega}{5\Omega + 10\Omega + 10\Omega + 25\Omega + 50\Omega} = \frac{10}{100} = \frac{1}{10}$$

$$V_3 = \frac{1}{10} 250 = 25V$$

$$I = \frac{250V}{100\Omega} = 2.5A$$

$$V_3 = (10\Omega) I = 25V$$

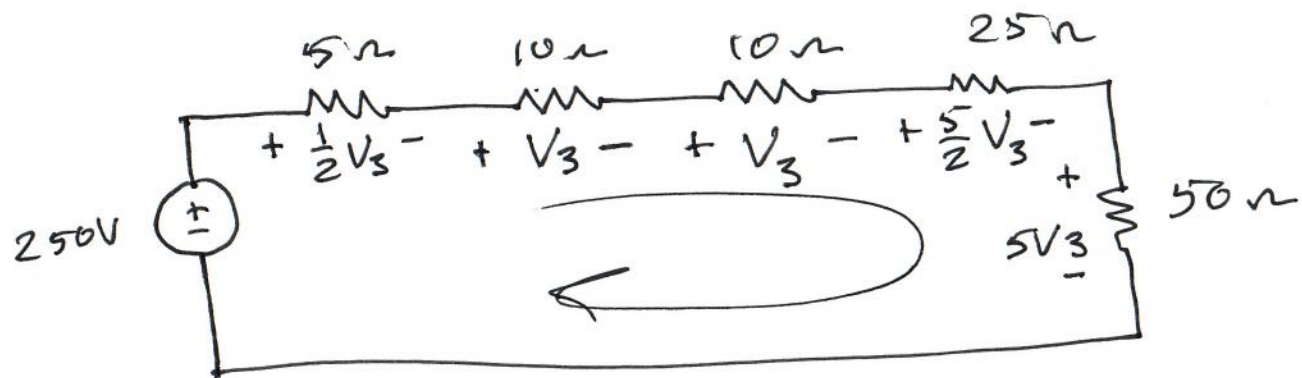


$$\text{KVL: } \frac{1}{2} V_3 + V_3 + V_3 + \frac{5}{2} V_3 + 5V_3 = 250$$

$$10V_3 = 250$$

$$V_3 = 25V$$

Parallel Resistors

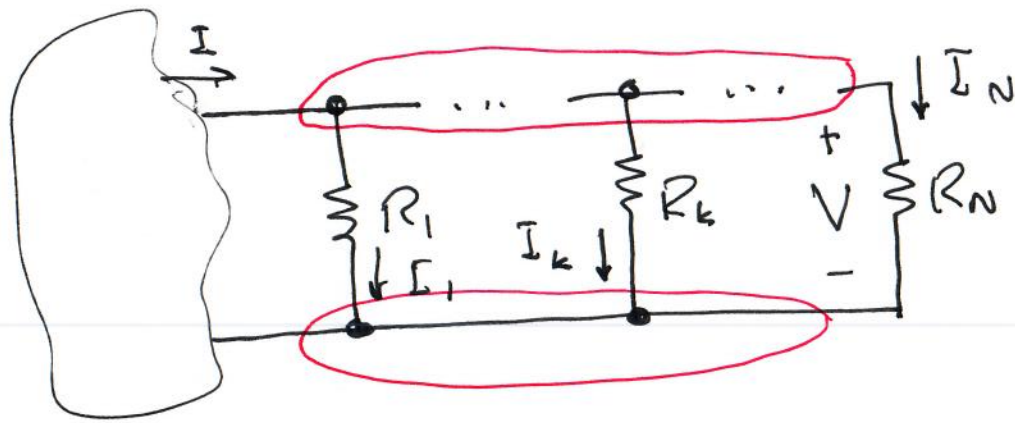

$$I_N = \frac{V}{R_N}$$

$$\vdots$$

$$I_k = \frac{V}{R_k}$$

$$\vdots$$

$$I_1 = \frac{V}{R_1}$$

$$I_1 + \dots + I_k + \dots + I_N = I$$

$$\frac{V}{R_1} + \dots + \frac{V}{R_k} + \dots + \frac{V}{R_N} = I$$

$$\left(\frac{1}{R_1} + \dots + \frac{1}{R_k} + \dots + \frac{1}{R_N} \right) V = I$$

$$V = \frac{I}{\left(\frac{1}{R_1} + \dots + \frac{1}{R_k} + \dots + \frac{1}{R_N} \right)}$$

$$V = \frac{I}{\left(\frac{1}{R_{eq}} \right)}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \dots + \frac{1}{R_k} + \dots + \frac{1}{R_N}$$

equivalent
conductance

$$\frac{I_k}{I} = \frac{\frac{1}{R_k}}{\left(\frac{1}{R_1} + \dots + \frac{1}{R_k} + \dots + \frac{1}{R_N}\right)}$$

current divider


For resistors connected in series:
values add

$$R_{eq} = R_1 + \dots + R_N$$

For resistors connected in parallel:


inverse values add to
give inverse resistance
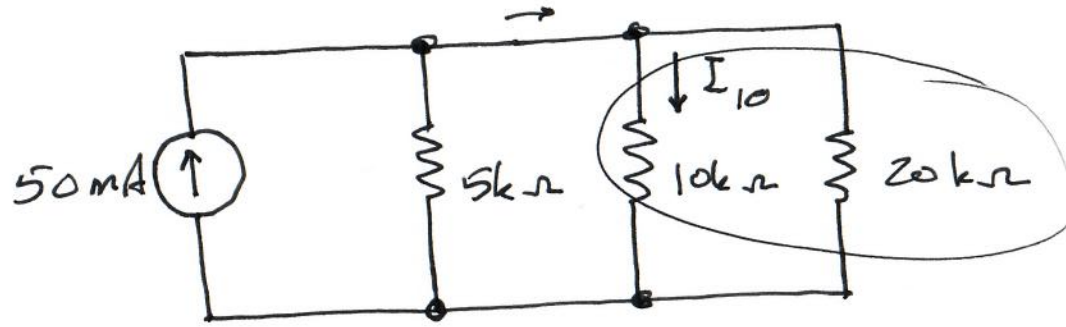
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \dots + \frac{1}{R_N}$$



$$\frac{I_{10}}{50 \text{ mA}} = \frac{\frac{1}{10 \text{ k}\Omega}}{\frac{1}{5 \text{ k}\Omega} + \frac{1}{10 \text{ k}\Omega} + \frac{1}{20 \text{ k}\Omega}} = \frac{2}{7}$$



$$I_{10} = \frac{100}{7} \text{ mA}$$

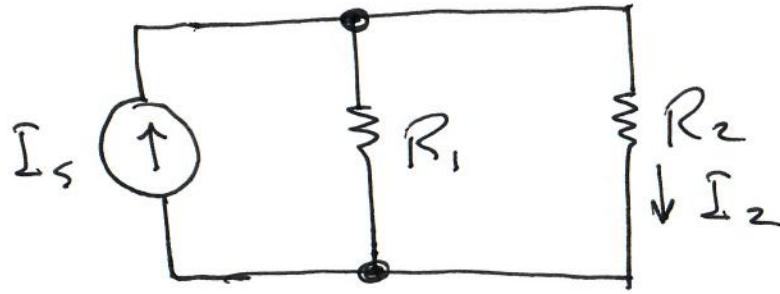

$$\frac{I_2}{I_s} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} \cdot \frac{R_2}{R_2} = \frac{1}{\frac{R_2}{R_1} + 1}$$

$$\frac{I_2}{I_s} = \frac{R_1}{R_1 + R_2}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

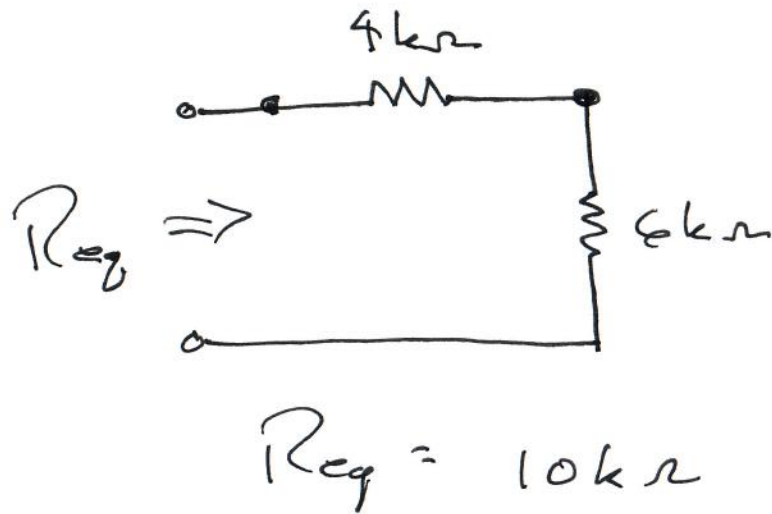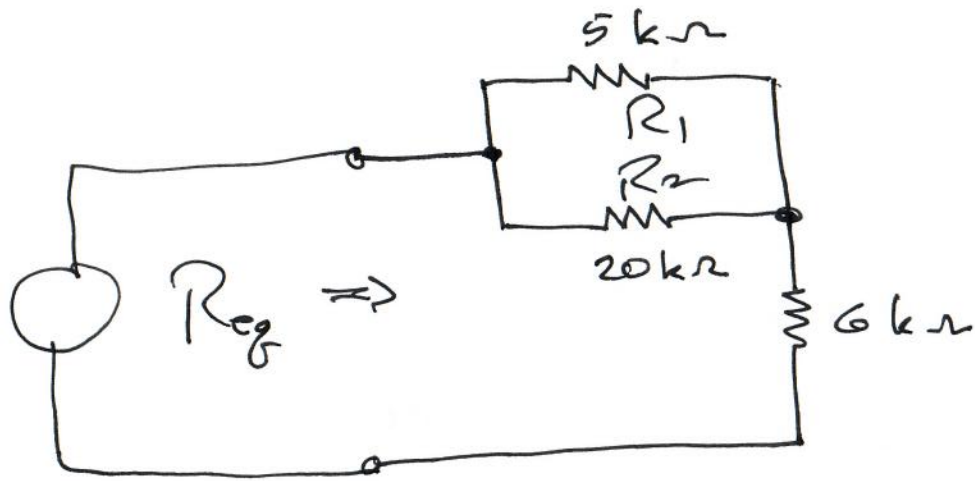

$$\frac{1}{R_g} = \frac{1}{5k\Omega} + \frac{1}{20k\Omega}$$

$$\frac{1}{R_{eq}} = \frac{5}{20k\Omega} = \frac{1}{4k\Omega}$$



$$R_{eq} = 4k\Omega$$

$$\frac{1}{R_g} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_2 + R_1}$$
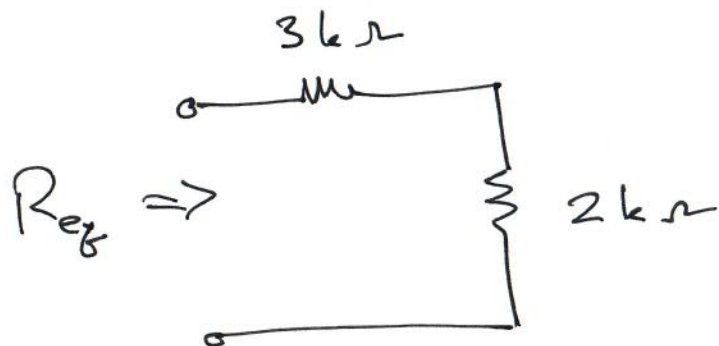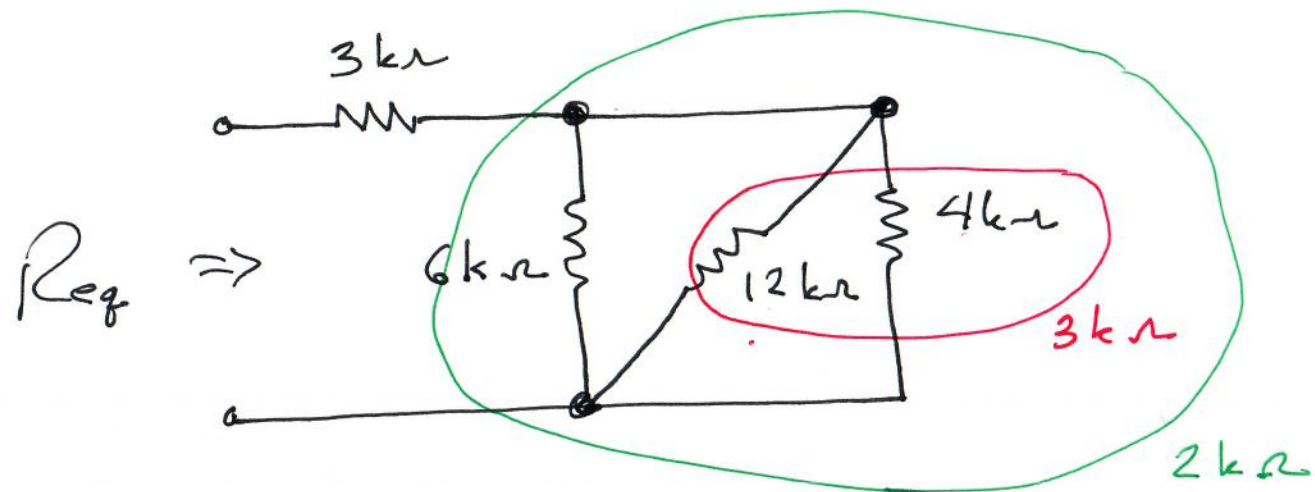
$$\begin{aligned} R_{eq} &= \frac{(5k\Omega)(20k\Omega)}{5k\Omega + 20k\Omega} \\ &= \frac{100k^2\Omega^2}{25k\Omega} \\ &= 4k\Omega \end{aligned}$$




$$R_{eq} = 5k\Omega$$

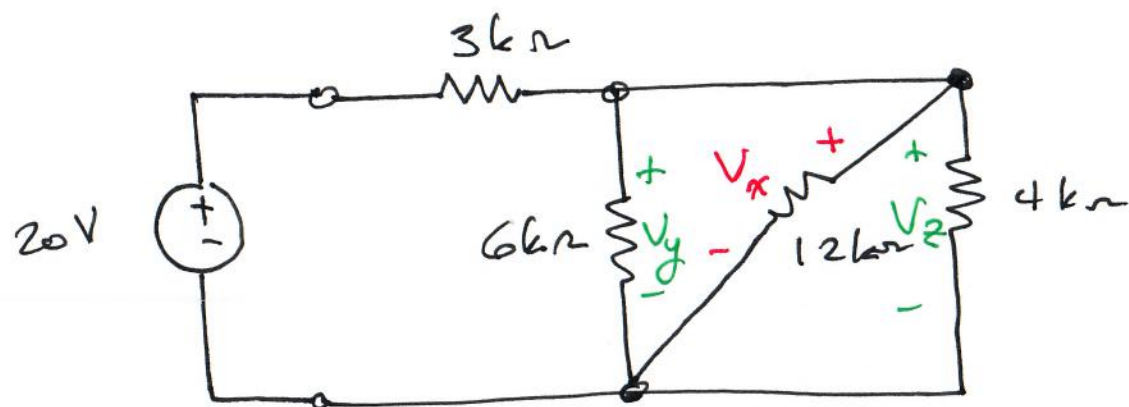

$$V_x = V$$


$$V_y = V$$

$$V_z = V$$

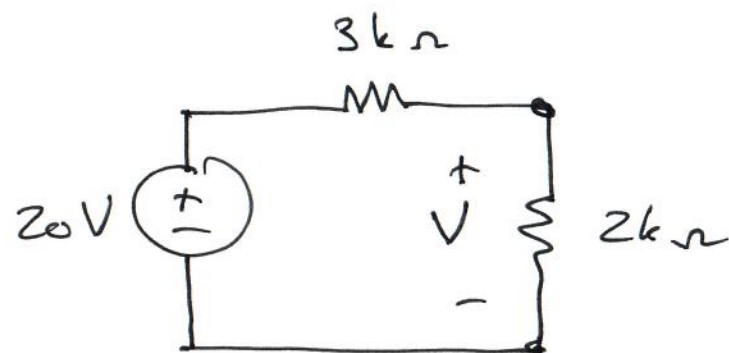

$$V = \frac{2k\Omega}{3k\Omega + 2k\Omega} \cdot 20V$$
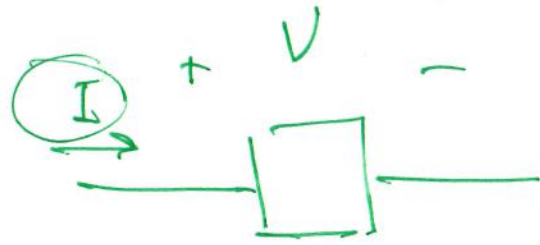
$$P_{4k\Omega} = \frac{V_z^2}{4k\Omega} = \frac{(8V)^2}{4k\Omega} = 16mW$$



absorbs