
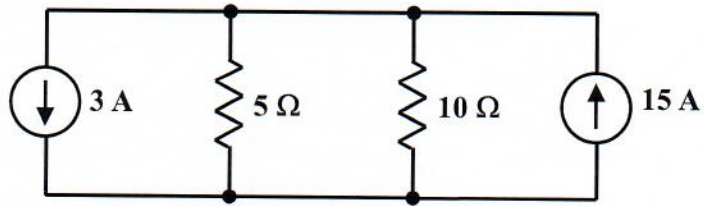


EE/EET 2240
Homework Problem #017

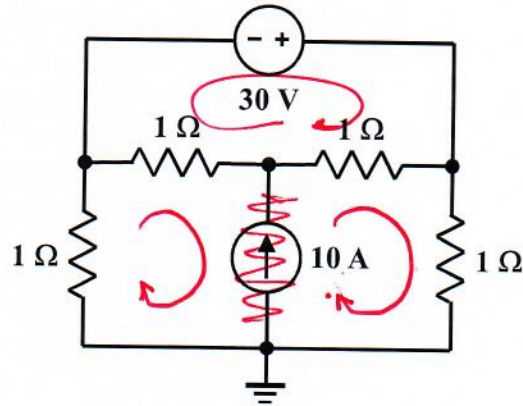
Express mesh equations in the matrix form discussed in class.



EE/EET 2240
Homework Problem #018



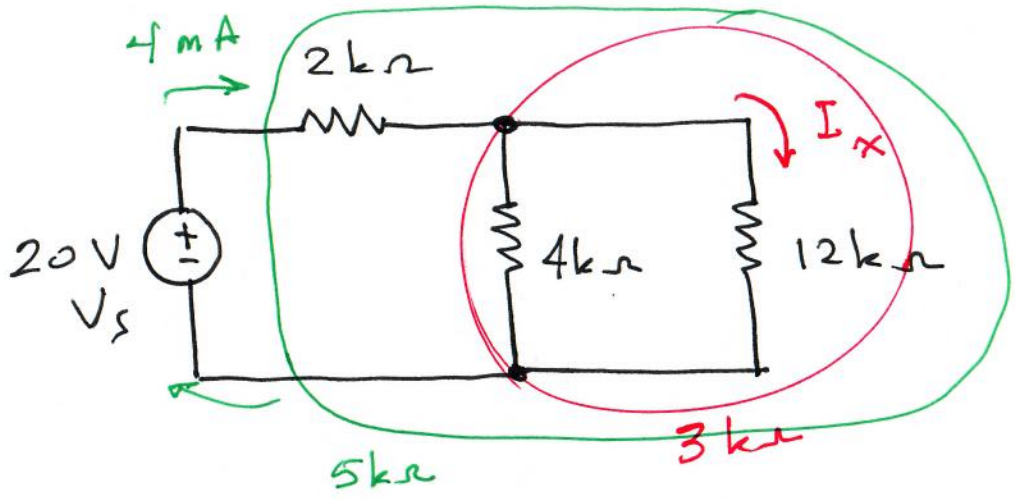- a. Express mesh equations in the matrix form discussed in class.
- b. Solve the equations.
- c. Is the 30 V source *delivering power* or *absorbing power*? How much?



$$I_x = \frac{4k\Omega}{4k\Omega + 12k\Omega} \cdot 4mA$$

$$= \frac{16}{16k} = 1mA$$

$$P_{2k\Omega} = I_x^2 (12k\Omega)$$


$$= 12mW$$

$$I_x = C \cdot V_s$$


$$= \frac{4k\Omega}{4k\Omega + 12k\Omega} \cdot \frac{V_s}{5k\Omega}$$

$$= \frac{4k\Omega}{16k\Omega \cdot 5k\Omega} \cdot V_s \quad (2k\Omega + (4k\Omega || 12k\Omega))$$

$$= \frac{1}{20} \times 10^{-3} V_s$$

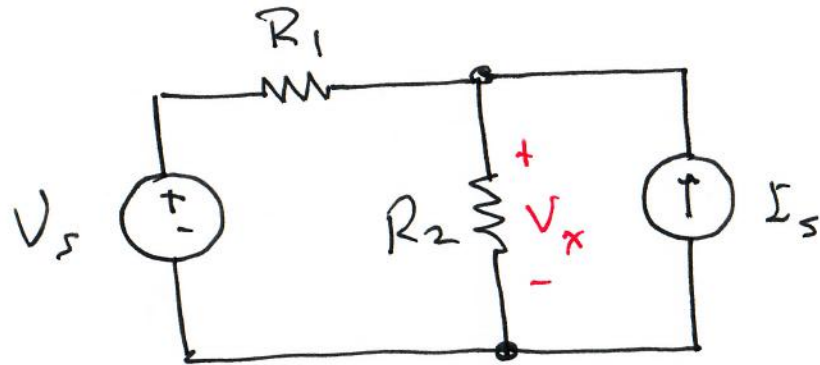


Superposition:

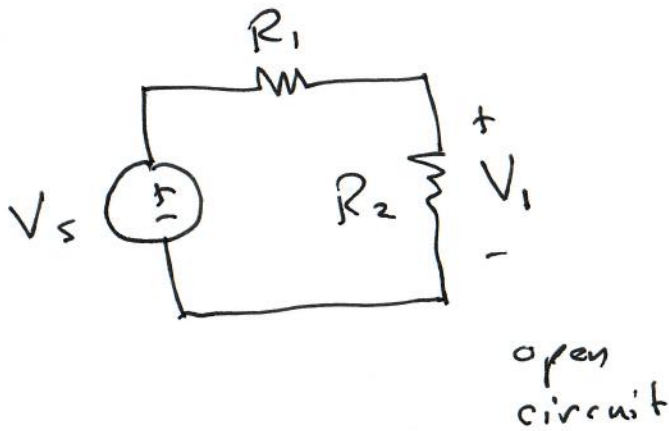

Contribution to V_x
from the V_s source.

$$V_1 = \frac{R_2}{R_1 + R_2} V_s$$

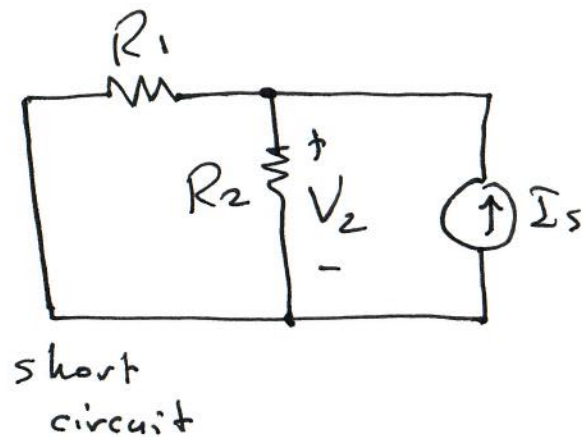


Contribution to V_x
from the I_s source.

$$V_2 = \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$\begin{aligned}
 V_x &= V_1 + V_2 \\
 &= \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} I_s
 \end{aligned}$$

Is this true?

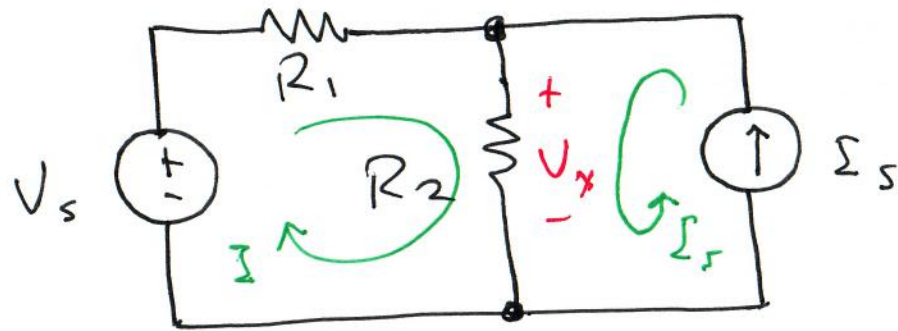


$$-V_s + R_1 I + R_2 (I + I_s) = 0$$


$$I = \frac{V_s - R_2 I_s}{R_1 + R_2}$$

$$V_x = R_2 (I + I_s) = \frac{R_2 V_s - R_2^2 I_s}{R_1 + R_2} + R_2 I_s$$
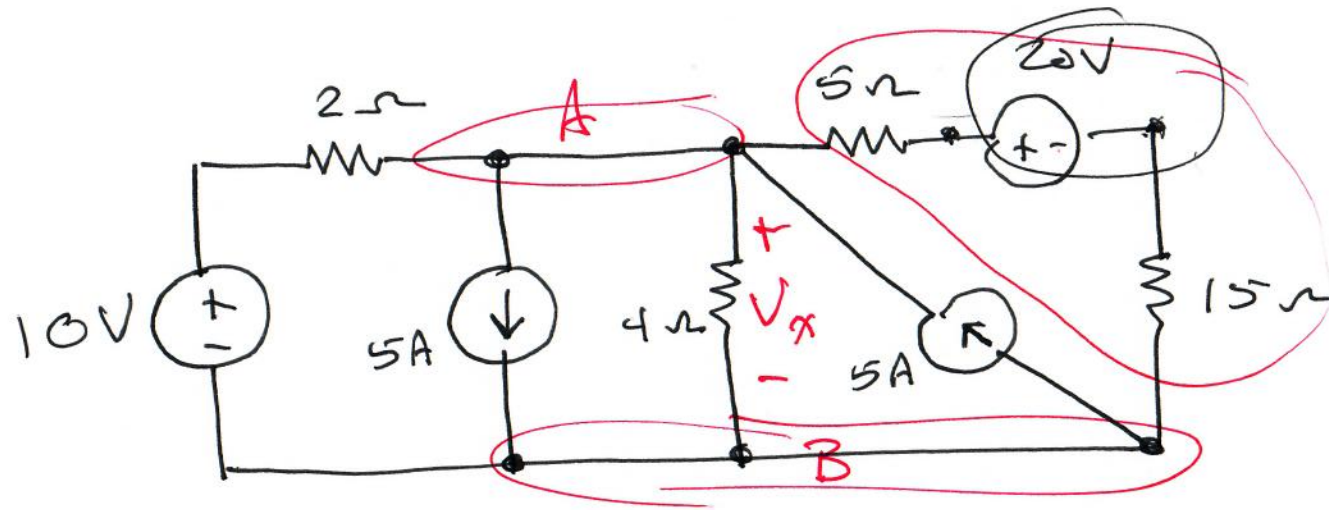
$$V_A = \frac{R_2 V_S - \cancel{R_2^2} \hat{I}_S + R_2 R_1 \hat{I}_S + \cancel{R_2^2} \hat{I}_S}{R_1 + R_2}$$
$$= \frac{R_2}{R_1 + R_2} V_S + \frac{R_2 R_1}{R_1 + R_2} \hat{I}_S$$




For the 10V source:

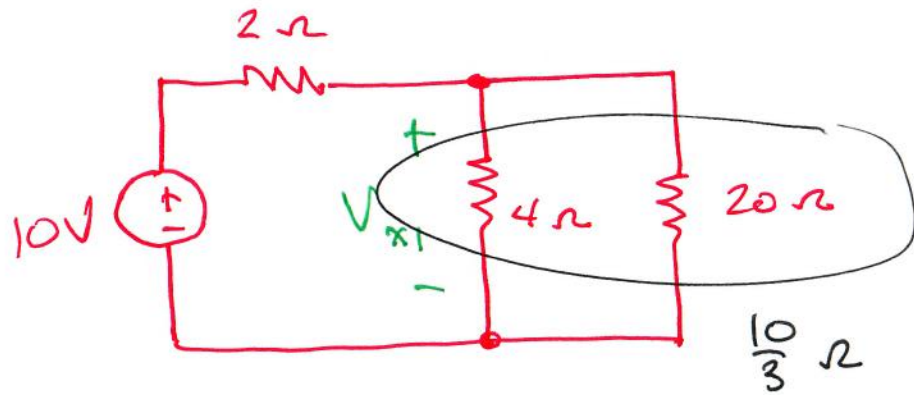

$$V_{x1} = \frac{\frac{10}{3}}{2 + \frac{10}{3}} \cdot 10V$$

$$= \frac{8\sqrt{3}}{8\sqrt{3}} \cdot 10V = \frac{25}{4} V$$


For the left 5A source:

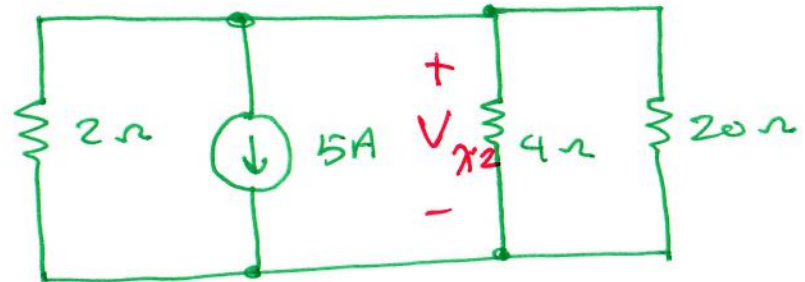


$$R_{eq} = \frac{\frac{10}{3} \times 2}{\frac{10}{3} + 2} = \frac{10}{4} \Omega$$

$$V_{x2} = - \frac{5}{4} \cdot 5A = - \frac{25}{4} V$$

For the right 5A source:

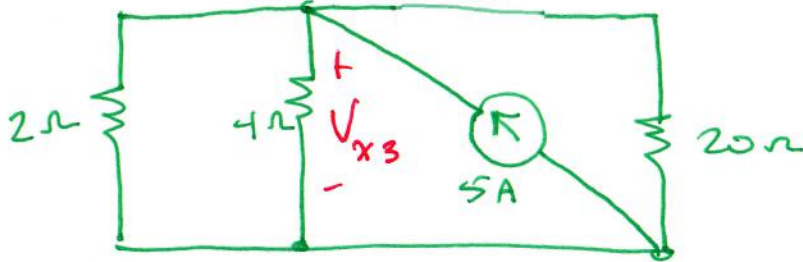

For the 20V source:

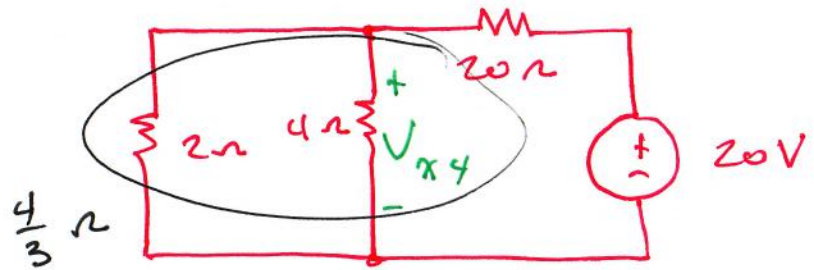


$$V_x = V_{x1} + V_{x2} + V_{x3} + V_{x4} \quad ?$$

$$V_{x3} = \frac{25}{4} \text{ V}$$



$$V_{x4} = \frac{\frac{4}{3} \cdot 20}{\frac{5}{3} + 20} \text{ V}$$

$$= \frac{15}{4} \text{ V}$$
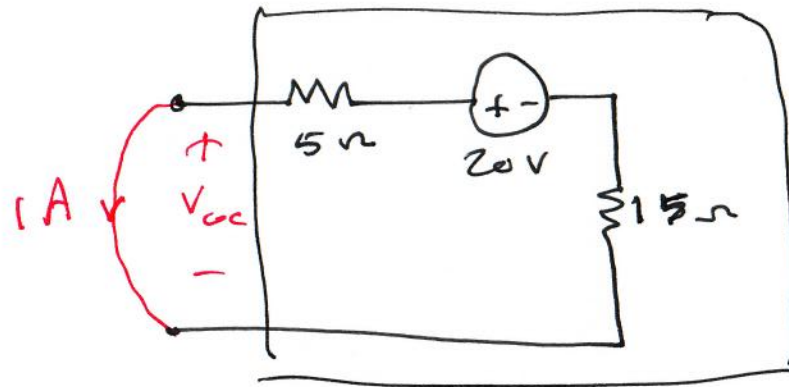
$$V_x = \frac{25}{4} - \frac{25}{4} + \frac{25}{4} + \frac{15}{4} = \frac{15}{2} \text{ V}$$



$$V_{oc} = 20V$$

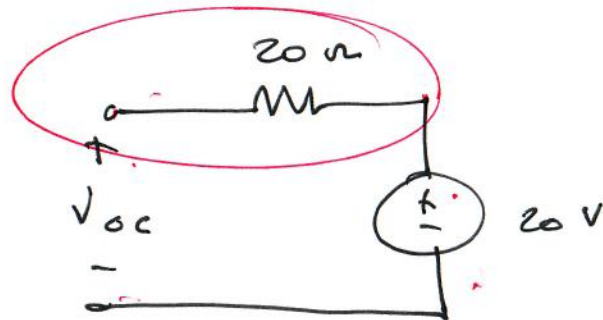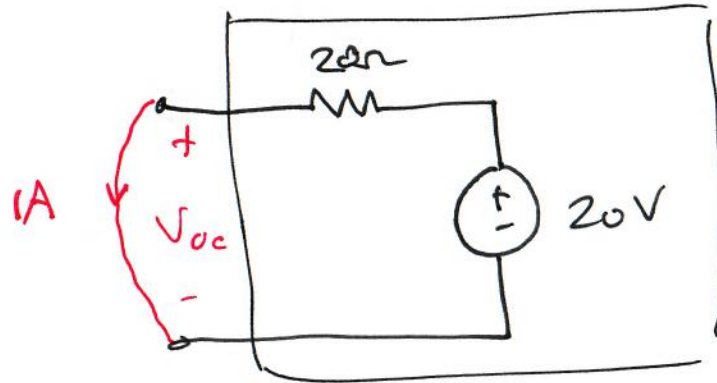

$$-V_{oc} + \cancel{R(1A)} + 20 = 0$$

$$V_{oc} = 20V$$

