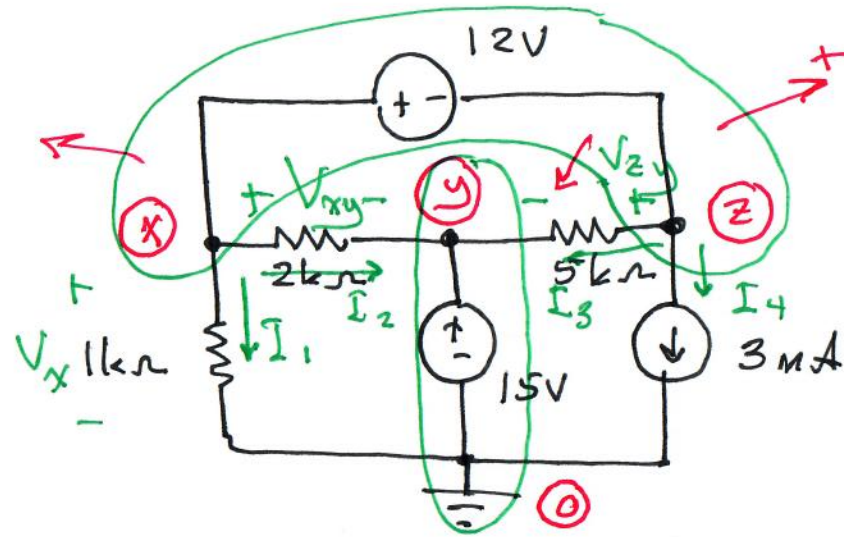


$$V_1 = 6V$$

$$V_1 - V_2 = 10V$$

$$\begin{bmatrix} 1 & 0 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 6 \\ 10 \end{bmatrix}$$




$$1. \quad V_y = 15V$$

$$2. \quad V_x - V_z = 12V$$

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$3. \quad + \frac{V_x}{1k\Omega} + \frac{V_x - V_y}{2k\Omega} + \frac{V_z - V_y}{5k\Omega} + 3mA = 0 \quad (\text{KCL})$$
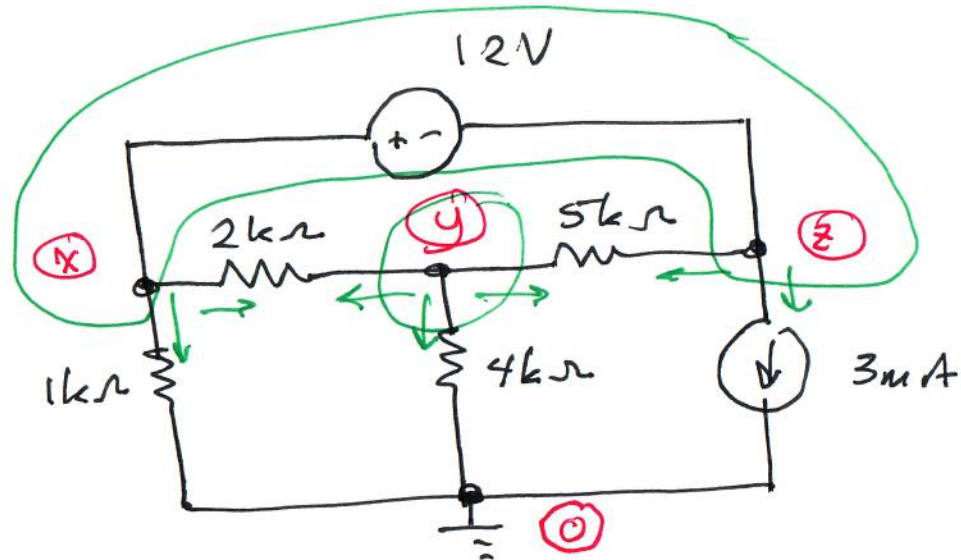
$$\begin{bmatrix} 0 & 1 & 0 \\ 1 & 0 & -1 \\ \frac{3}{2000} & -\frac{7}{10000} & \frac{1}{5000} \end{bmatrix} \begin{bmatrix} V_x \\ V_y \\ V_z \end{bmatrix} = \begin{bmatrix} 15 \\ 12 \\ -\frac{3}{1000} \end{bmatrix}$$




$$\frac{V_x - V_y}{2k\Omega} - \frac{V_y - V_x}{2k\Omega}$$

$$V_x - V_z = 12V$$



$$\frac{V_x}{1000} + \frac{V_x - V_y}{2000} + \frac{V_z - V_y}{5000} + \frac{3}{1000} = 0$$


$$\frac{V_y - V_x}{2k\Omega} + \frac{V_y}{4k\Omega} + \frac{V_y - V_z}{5k\Omega} = 0$$

EE/EET 2240
Homework Problem #007


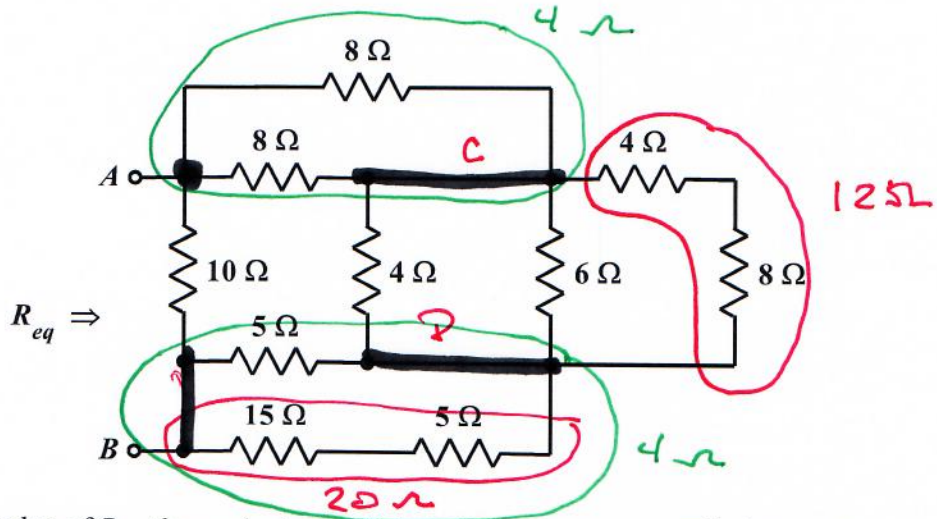


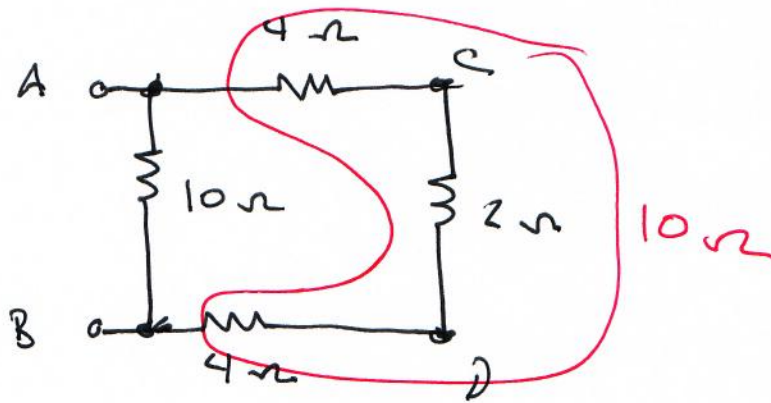
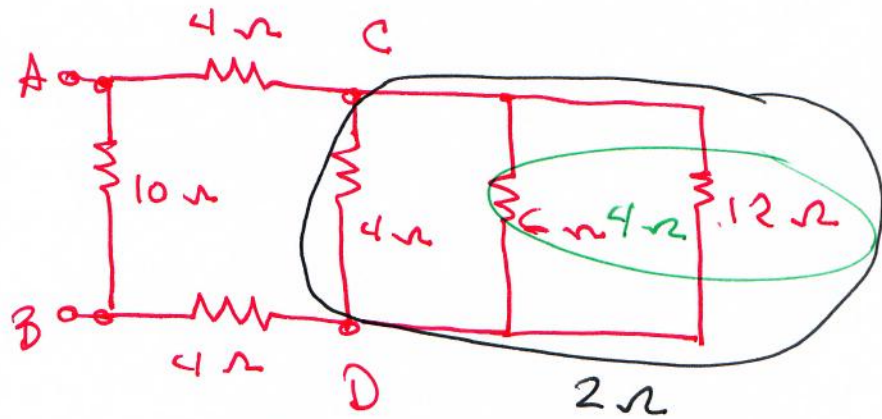
Determine the value of R_{eq} , the equivalent resistance with respect to terminal pair A-B.




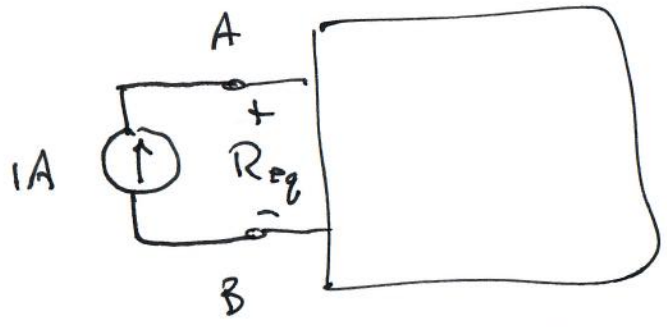


Current Divider

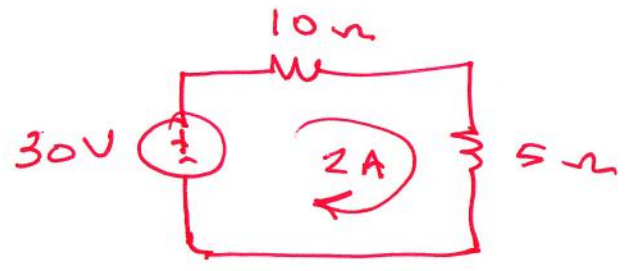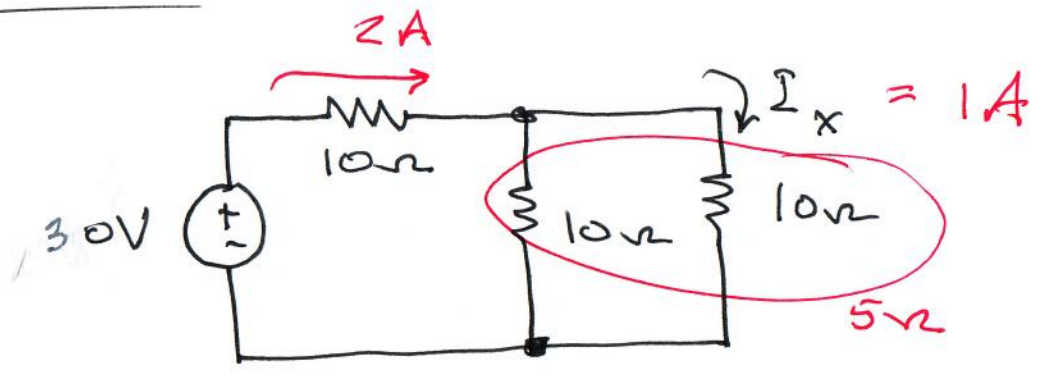

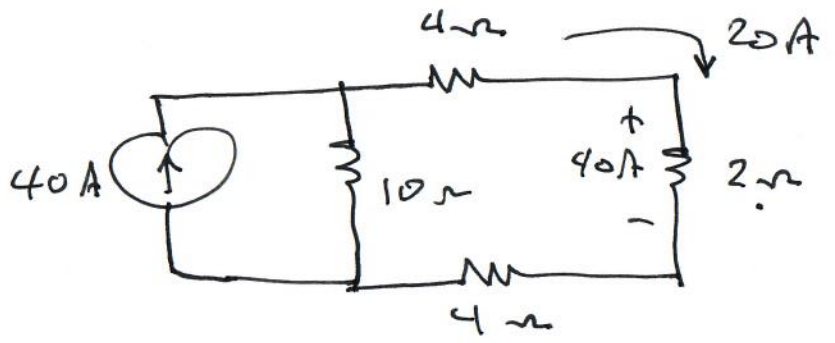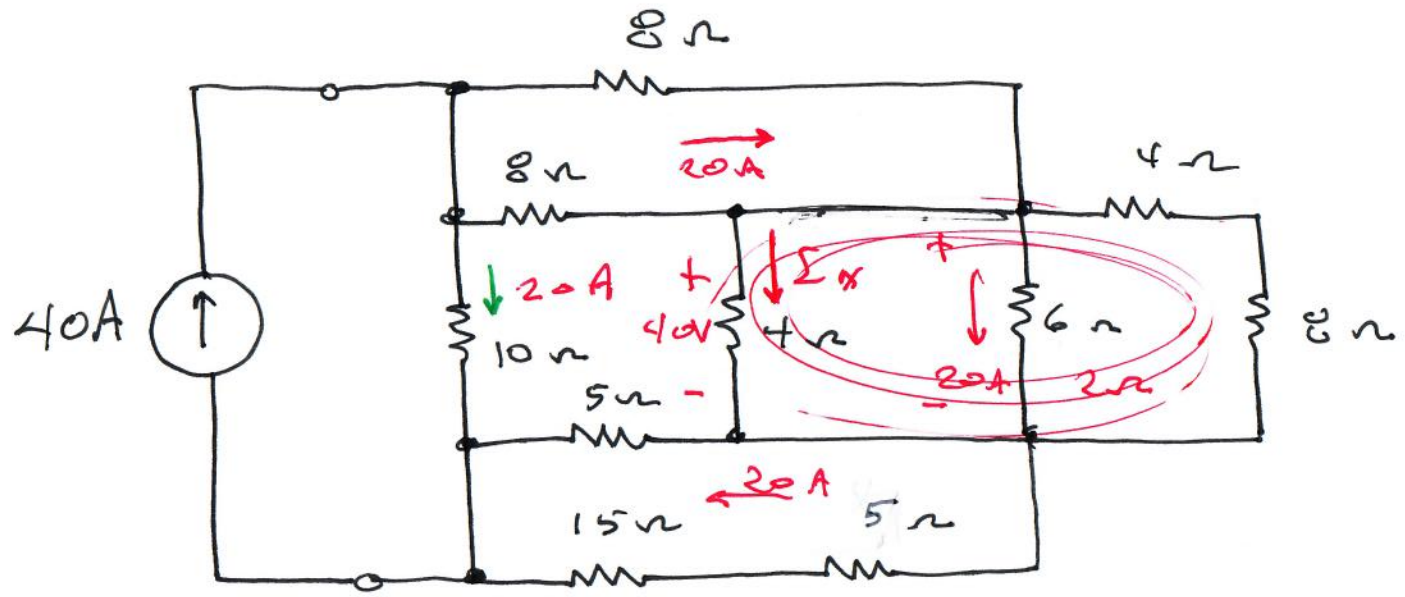

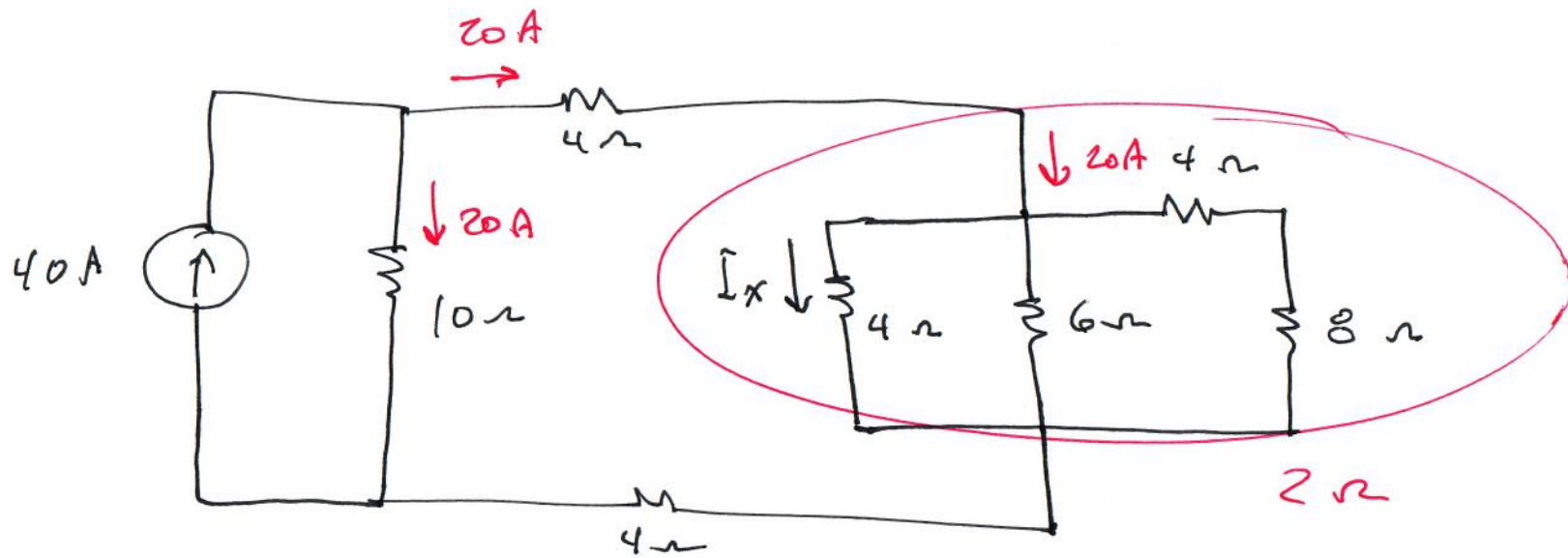
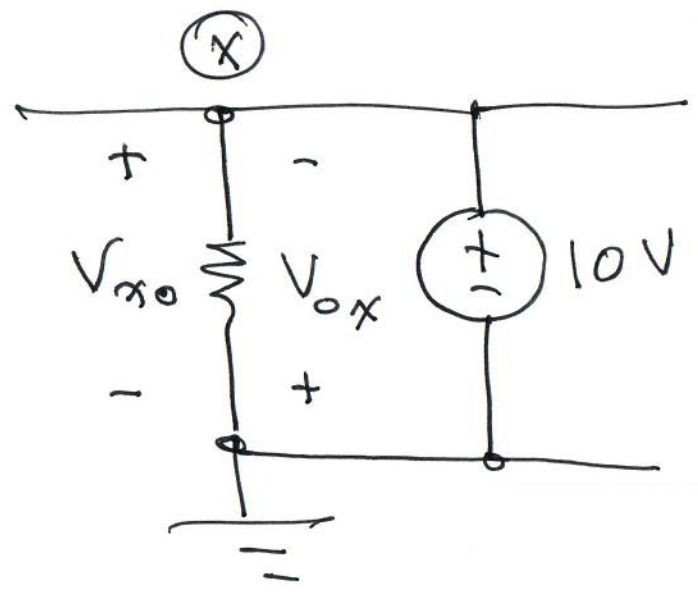
$$\begin{aligned}
 I_x &= \frac{\frac{1}{4}}{\frac{1}{4} + \frac{1}{6} + \frac{1}{12}} \cdot 20A \\
 &= \frac{\frac{6}{24}}{\frac{6+4+2}{24}} \cdot 20 \\
 &= \frac{1}{2} \cdot 20 = 10A
 \end{aligned}$$



$$V_{x0} = V_x - V_o$$

↑
o

$$= V_x$$

$$V_{ox} = V_o - V_x$$

↑
o

$$= -V_x$$