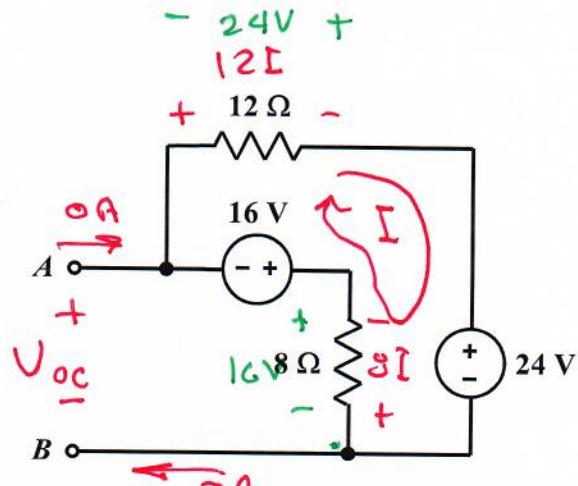


EE/EET 2240
Homework Problem #027




Find the Thévenin equivalent circuit with respect to terminals A and B .

$$\text{KVL: } 12I + 24 + 8I + 16 = 0$$


$$20I = -40$$

$$I = -2A$$

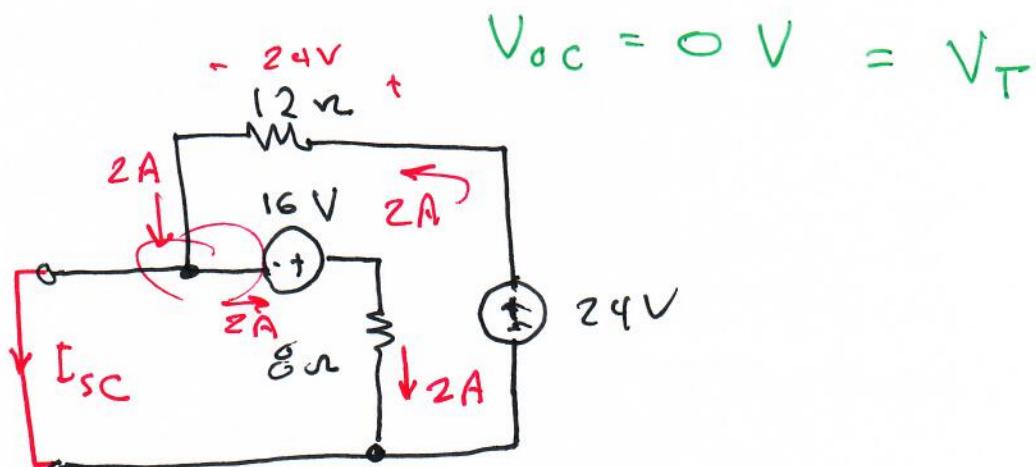


$$I_{sc} = 0A$$


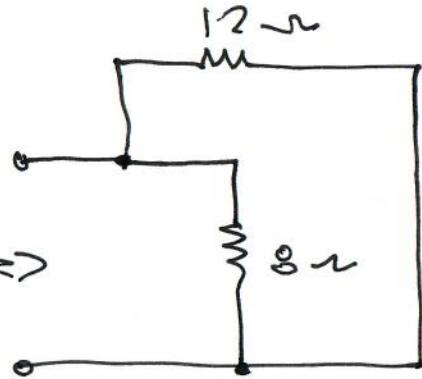
$$R_T = \frac{V_{oc}}{I_{sc}} = \frac{0}{0} = ?$$




$R_T \Rightarrow$



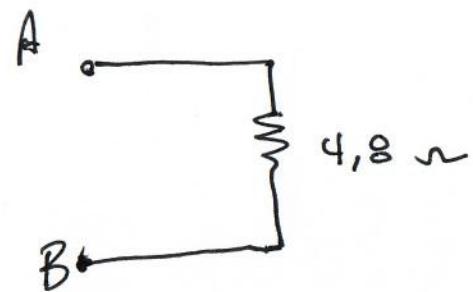
$$R_T = 8\Omega \parallel 12\Omega = 4.8\Omega$$




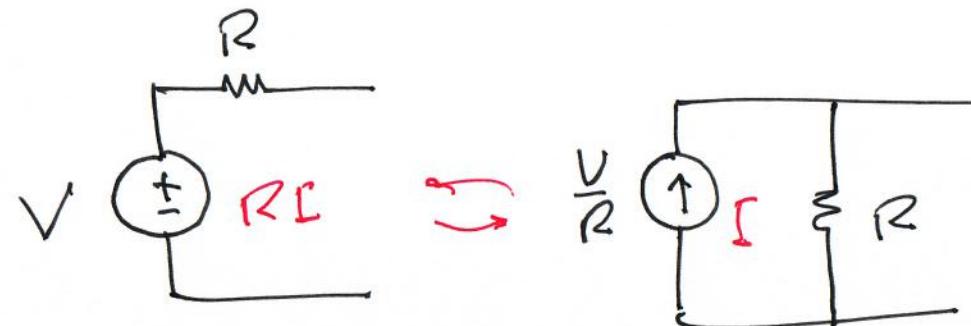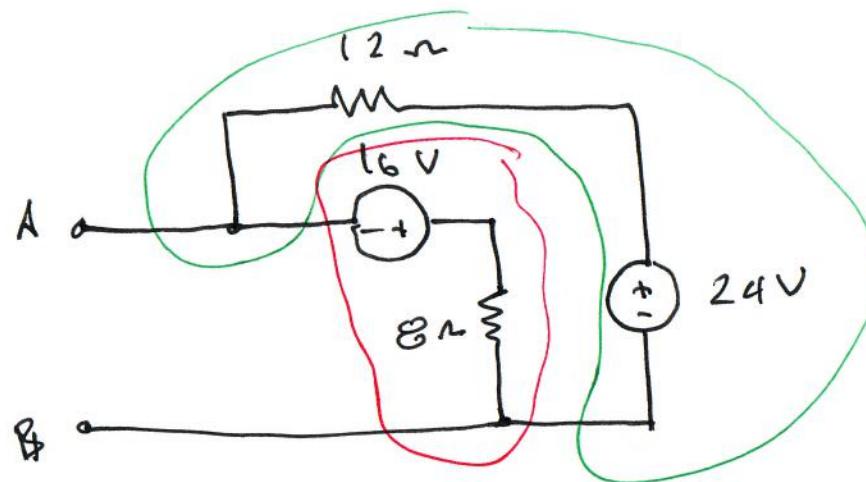

Source Transformation

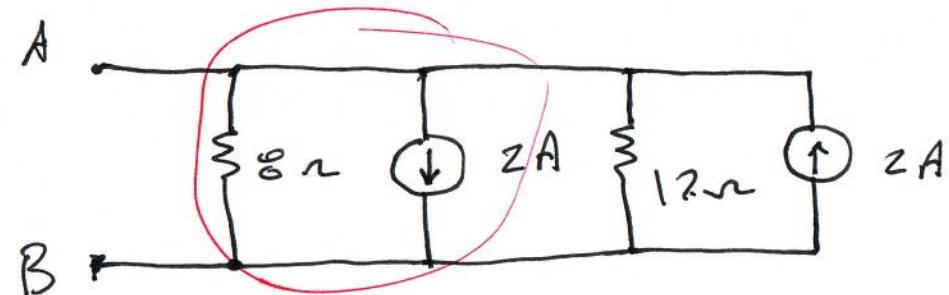

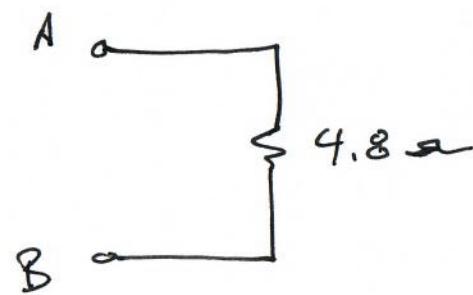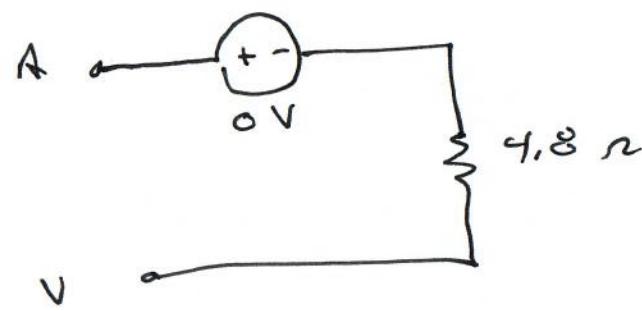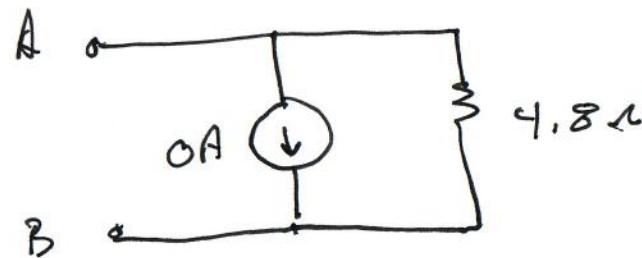

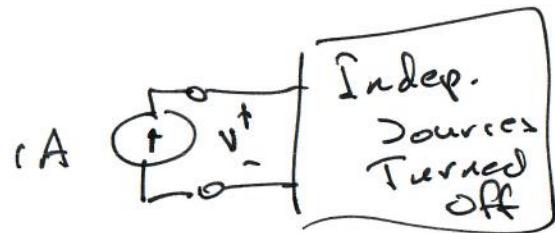


$$V = R_T = R_N$$

SC \Rightarrow Short Circuit

OC \Rightarrow Open Circuit


EE/EET 2240
Homework Problem #026

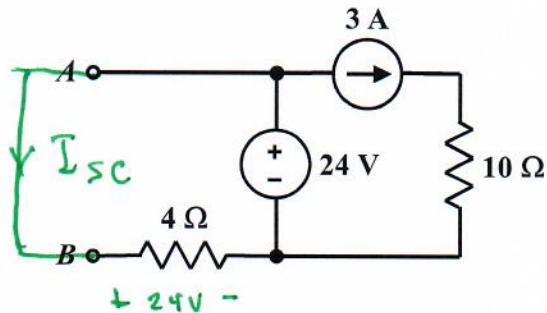


Find the Norton equivalent circuit with respect to terminals A and B.

$$R_T = R_N = 4 \Omega$$



$$I_{SC} = 6 A$$

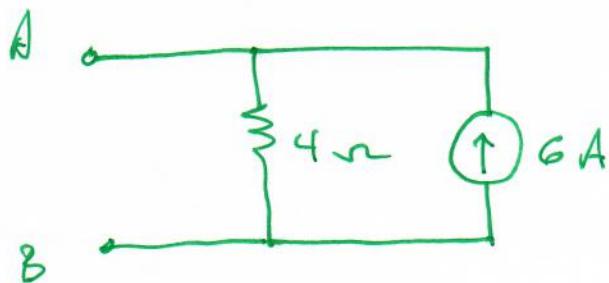


EE/EET 2240
Homework Problem #025

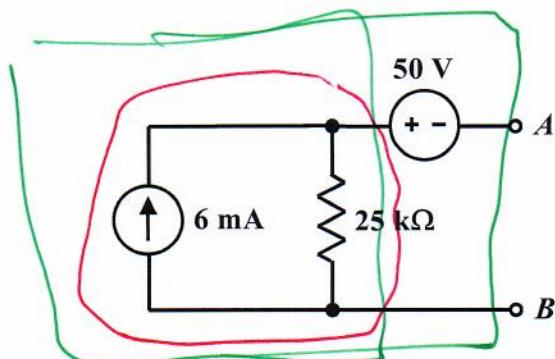

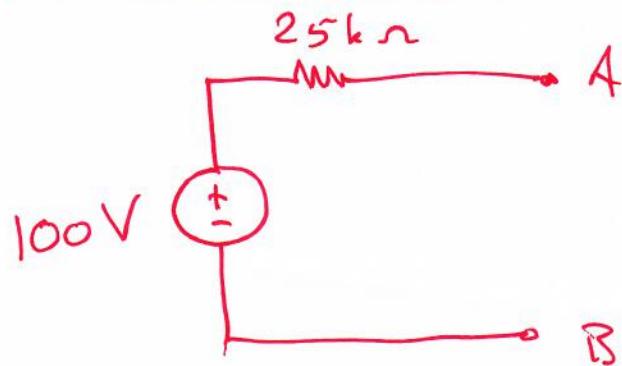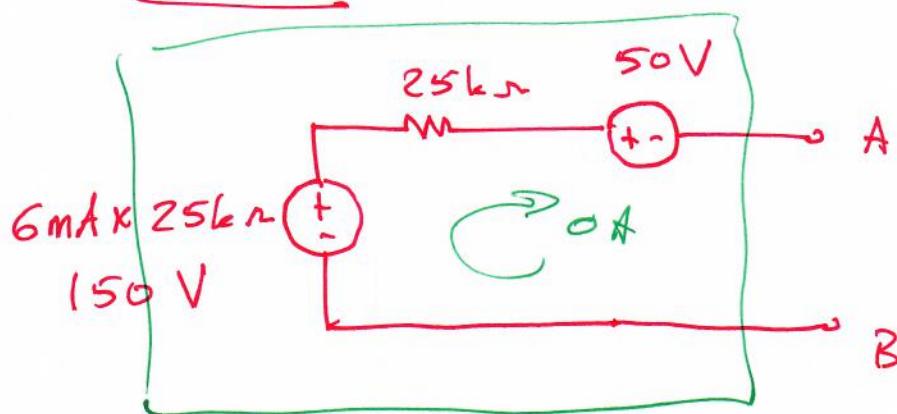Find the Thévenin equivalent circuit with respect to terminals A and B.



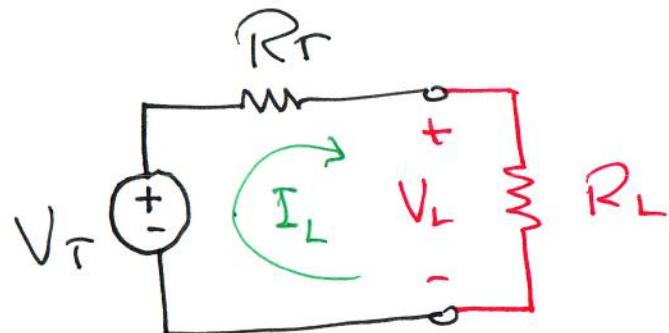

What value of R_L will absorb maximum power from the circuit?

$$V_L = \frac{R_L}{R_T + R_L} \cdot V_T$$

$$I_L = \frac{V_T}{R_T + R_L}$$

$$P_L = V_L I_L = \frac{R_L V_T^2}{(R_T + R_L)^2}$$

Maximize P_L w.r.t. R_L


Q

$$\frac{dP_L}{dR_L} = \frac{(R_T + R_L)^2 V_T^2 - R_L V_T^2 2(R_T + R_L)}{(R_T + R_L)^2}$$

$$(R_T + R_L) \cancel{V_T^2} - R_L \cancel{V_T^2} 2(\cancel{R_T + R_L}) = 0$$


$$R_T + R_L - 2R_L = 0$$

$$R_L = R_T$$

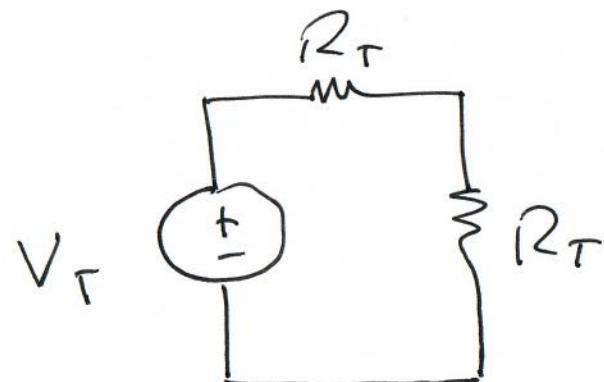


Maximum Power
Transfer Theorem



$$R_L = R_T \text{ (or } R_n\text{)}$$

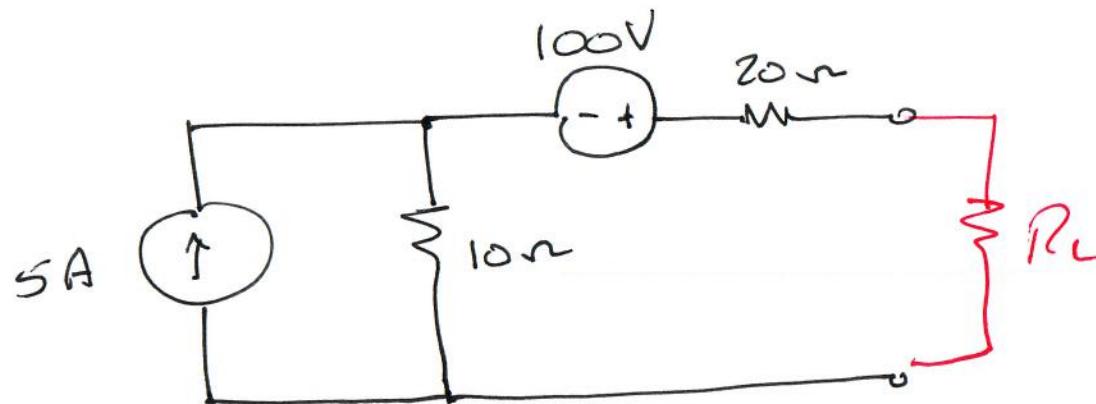

What R_L
will absorb
max. power?

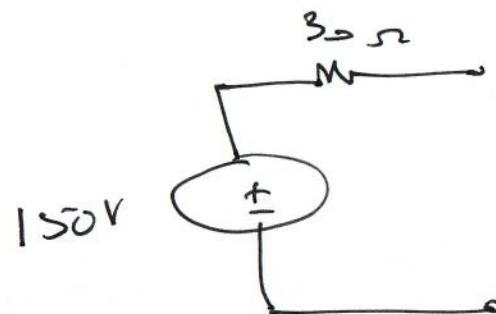


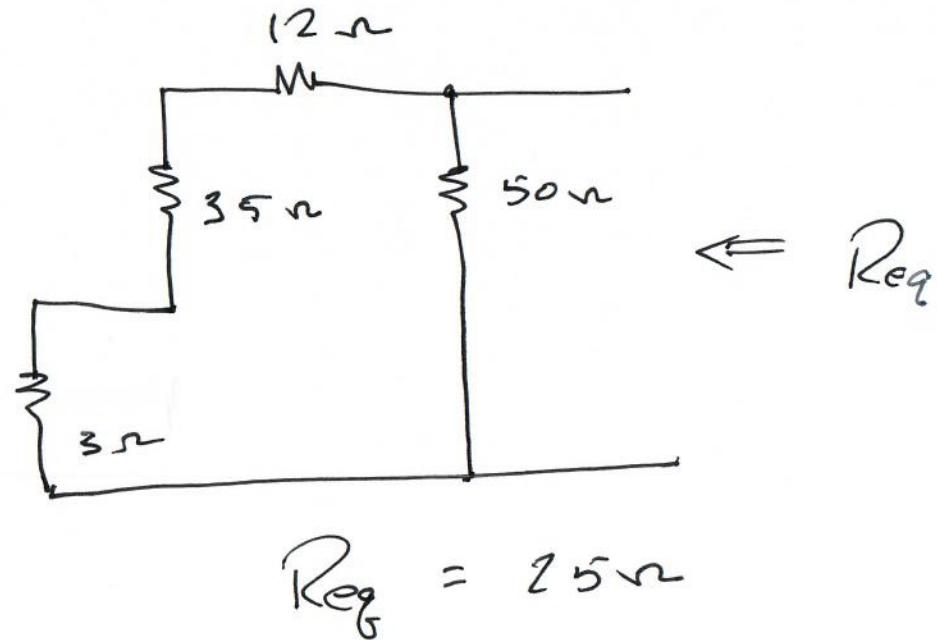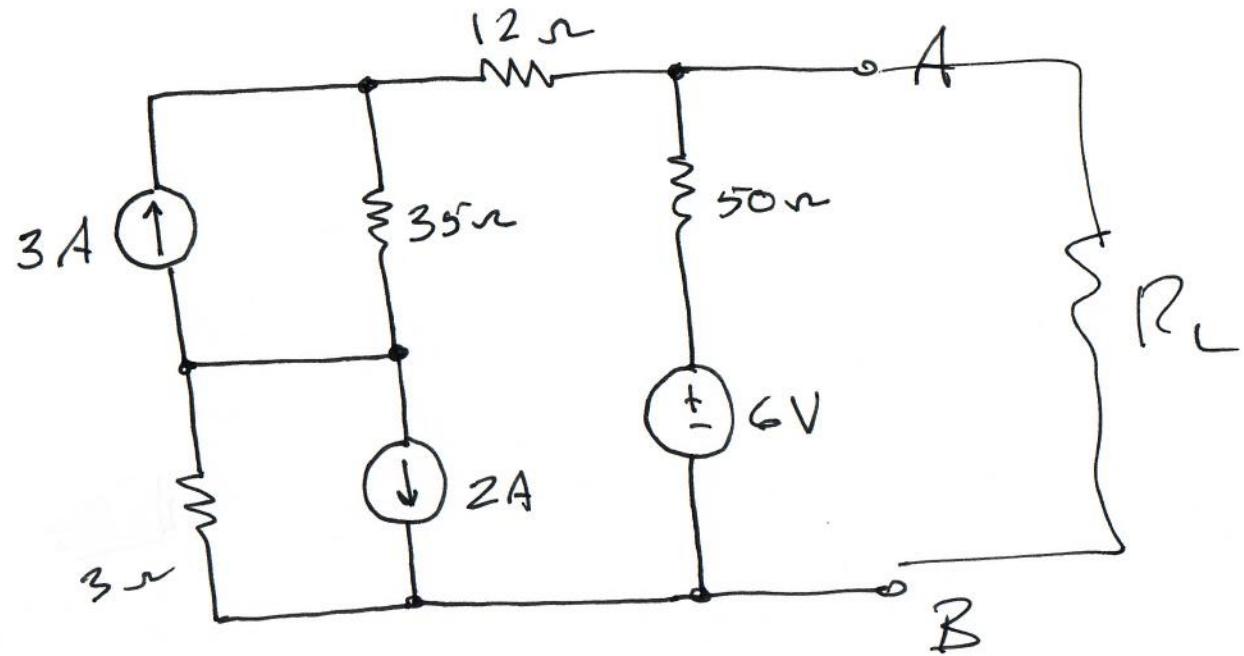'choose' $R_L = 30\Omega$
for max. power.






Independent Sources


12

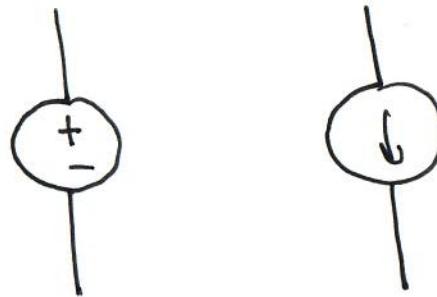

Dependent Sources (Controlled Sources)

$\rightarrow E$

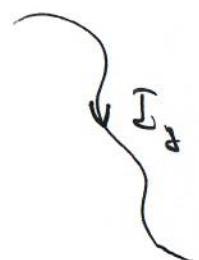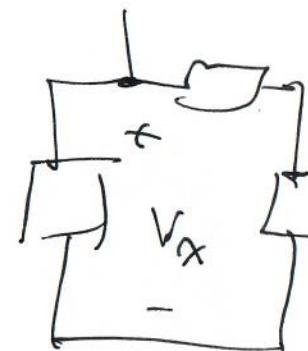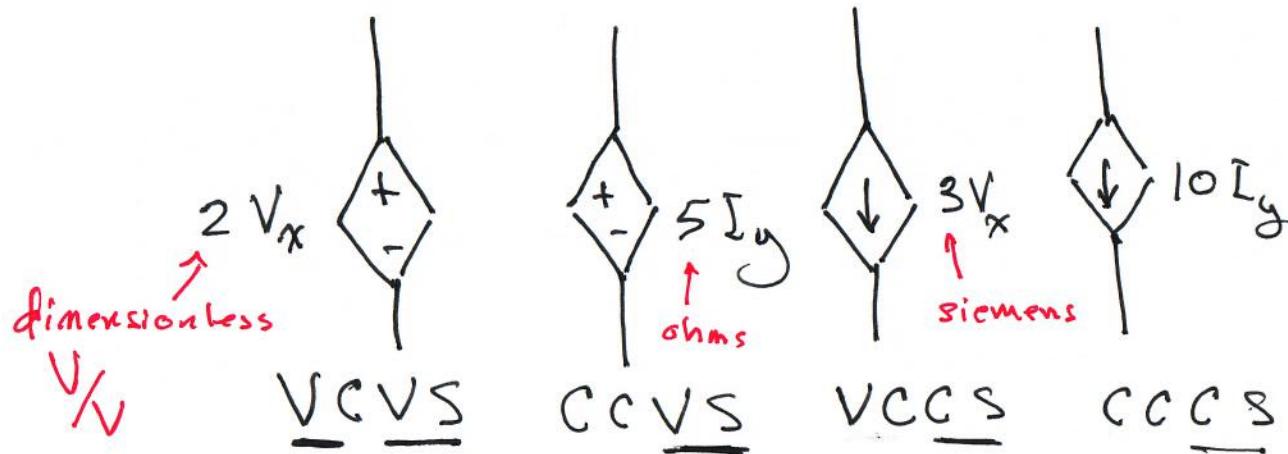

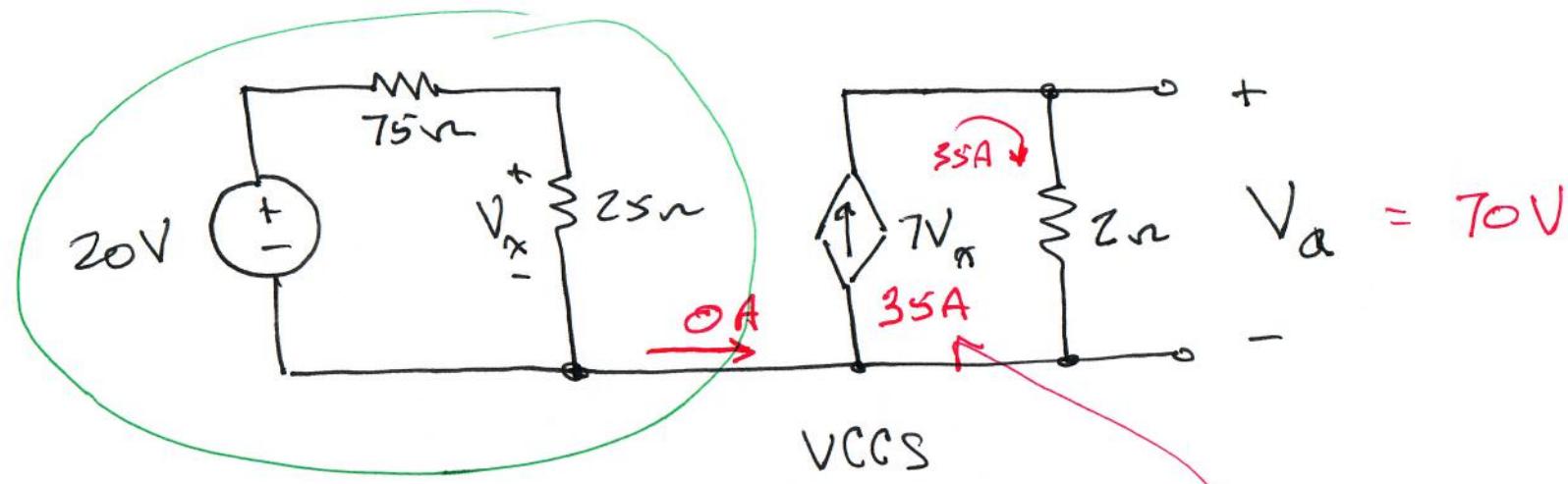

$$V_x = \frac{25}{100} \cdot 20 = 5V$$