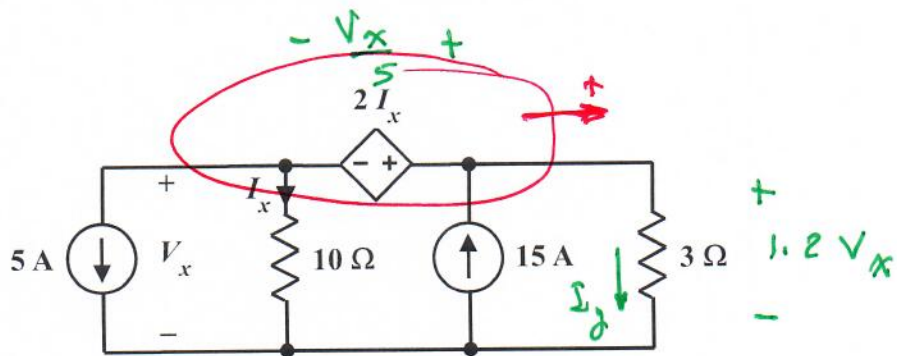


EE/EET 2240
Homework Problem #031



Determine the value of V_x .

$$I_x = \frac{V_x}{10\Omega}$$


$$I_y = \frac{1.2V_x}{3\Omega} = 0.4V_x$$

$$5A + \frac{V_x}{10\Omega} - 15A + \frac{4}{10}V_x = 0$$

$$\frac{1}{2}V_x = 10$$

$$V_x = 20V$$

EE/EET 2240
Homework Problem #033

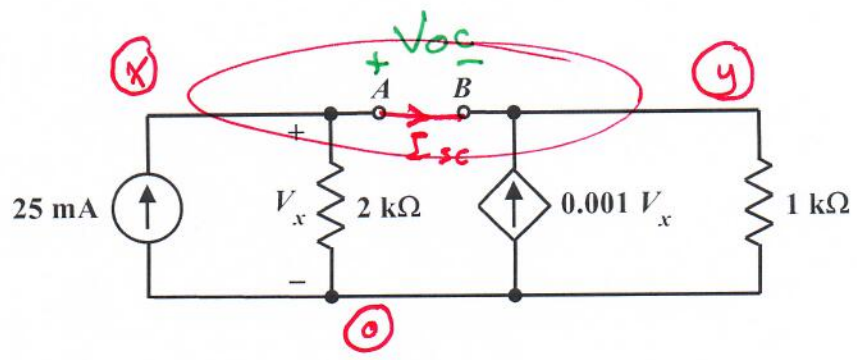

(a) Find the Thévenin equivalent circuit with respect to terminals A and B.

$$-25 \text{ mA} + \frac{V_x}{2 \text{ k}\Omega} = 0 \Rightarrow V_x = 50 \text{ V}$$

$$\frac{V_y}{1 \text{ k}\Omega} - \frac{V_x}{1000} = 0 \Rightarrow V_y = V_x = 50 \text{ V}$$


$$V_{oc} = V_x - V_y = 0 \equiv V_T$$

$$-25 \text{ mA} + \frac{V_x}{2 \text{ k}\Omega} - \frac{V_x}{1000} + \frac{V_x}{1000} = 0$$

$$\Rightarrow V_x = 50 \text{ V}$$


$$I_{sc} = 0 \text{ A} \Rightarrow R_T = \frac{0 \text{ V}}{0 \text{ A}}$$

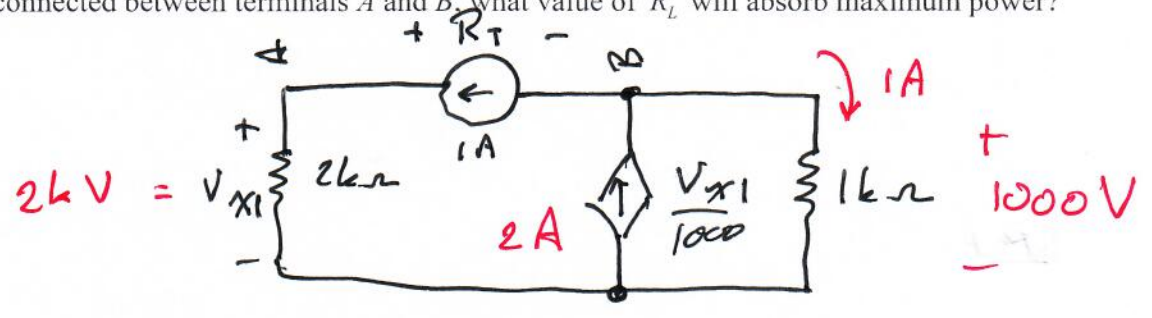
(b) If connected between terminals A and B, what value of R_L will absorb maximum power?



$$R_T + 1000 - 2000 \text{ V} = 0$$


$$R_T = 1000 \Omega$$

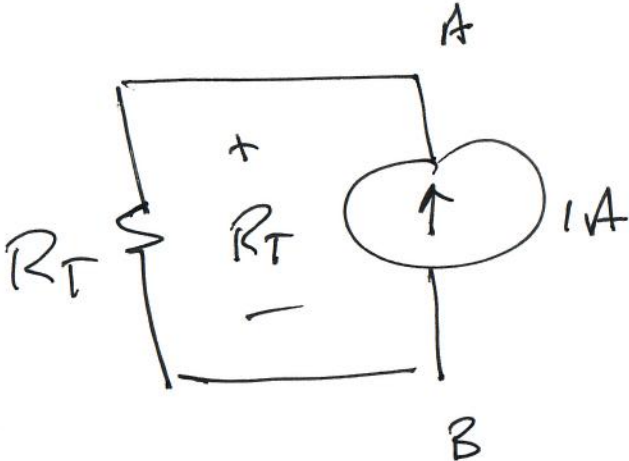

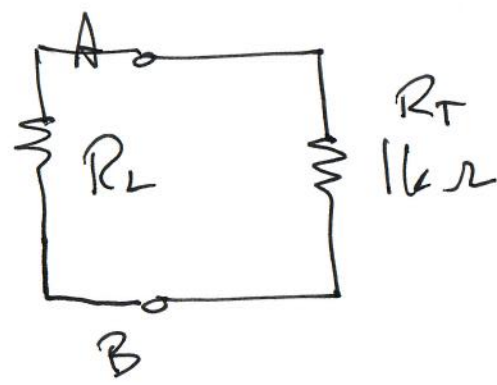

R_L will not absorb power or deliver power.

EE/EET 2240
Homework Problem #032

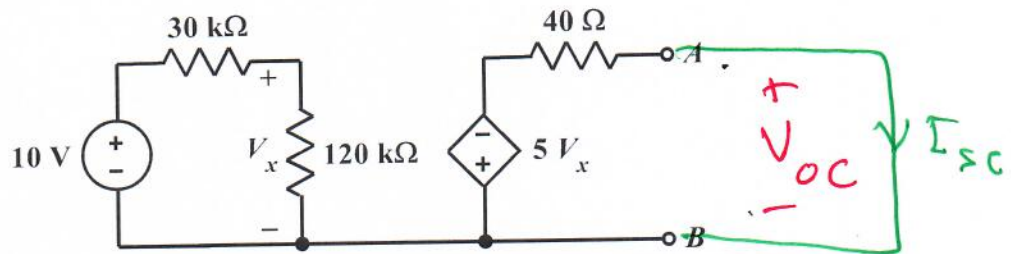

Find the Norton equivalent circuit with respect to terminals A and B .



$$V_x = \frac{120 \text{ k}\Omega}{150 \text{ k}\Omega} \cdot 10 \text{ V} = 8 \text{ V}$$


$$V_{oc} = -5V_x = -40 \text{ V}$$

$$I_{sc} = -\frac{40 \text{ V}}{40 \Omega} = -1 \text{ A}$$


$$I_N = -1 \text{ A}$$
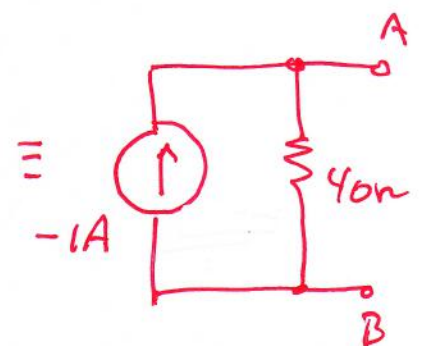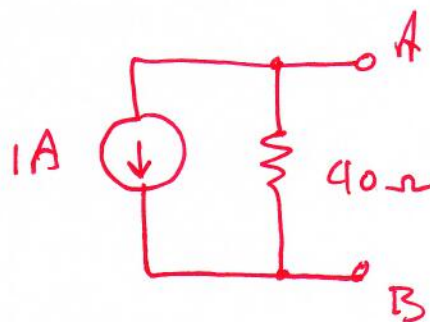
$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{-40 \text{ V}}{-1 \text{ A}} = 40 \Omega$$




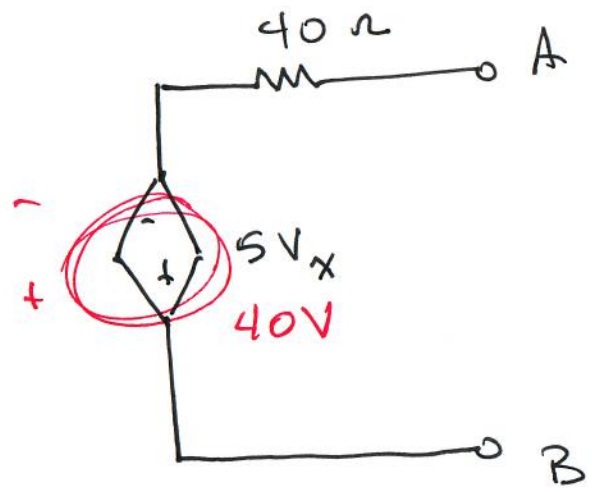


\Rightarrow

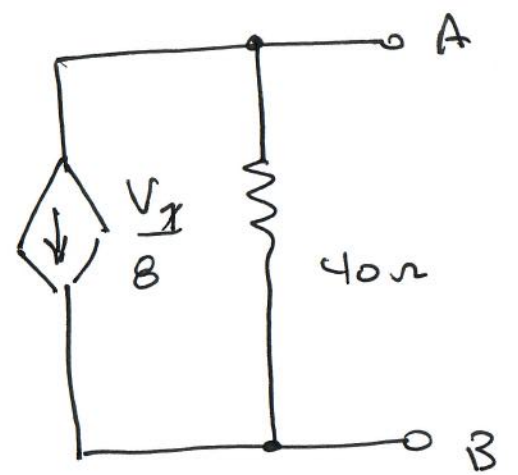


|||

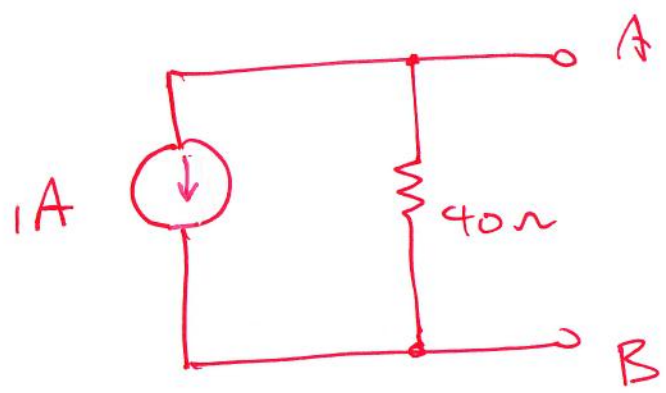

Operational Amplifier (OpAmp)

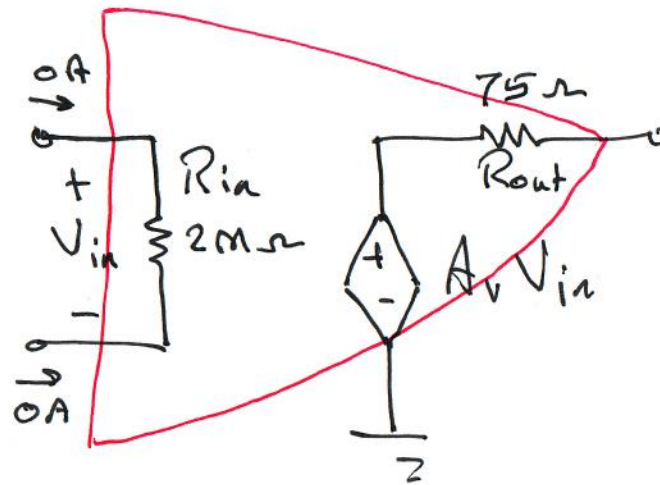

$$A_v \approx 100,000$$

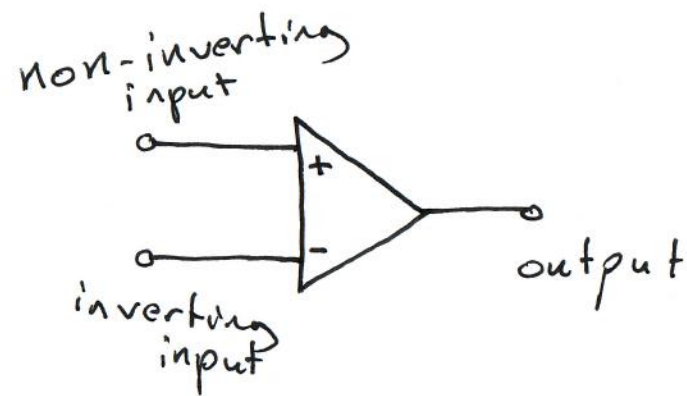



For an ideal OpAmp

$$R_{in} \approx \infty \Omega$$

$$R_{out} \approx 0 \Omega$$

$$V_{in} \approx 0 V$$


$$A_v \approx \infty V/V$$

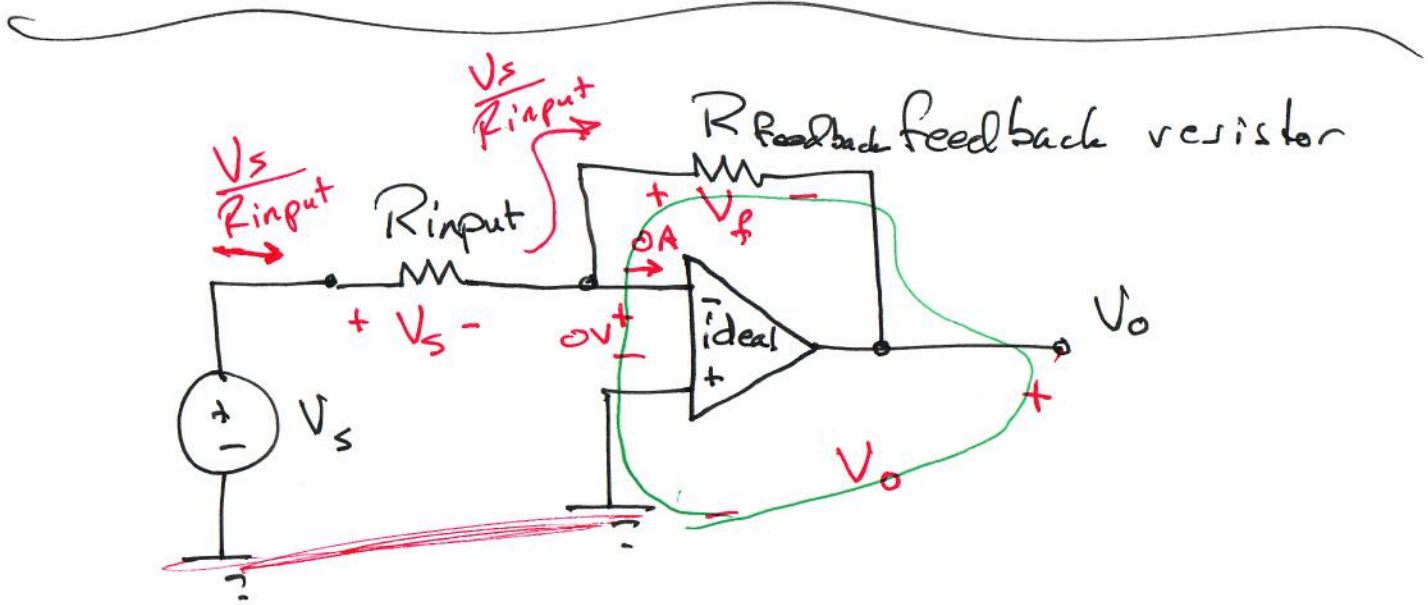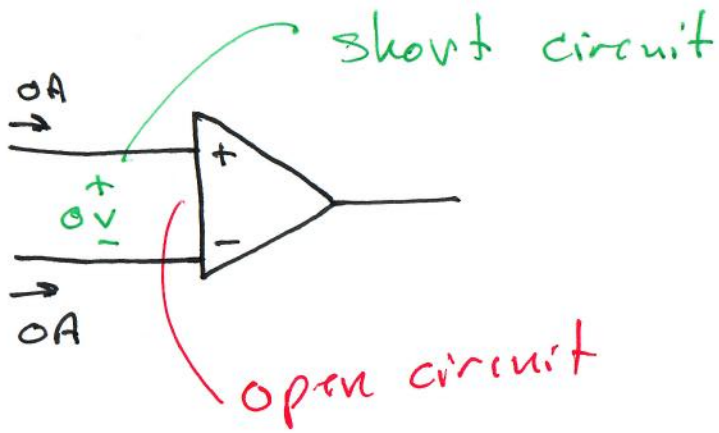

$$V_f = R_{feedback} \times \frac{V_s}{R_{input}}$$


$$V_o = -V_f = -\frac{R_f}{R_i} V_s$$

Inverting Amplifier

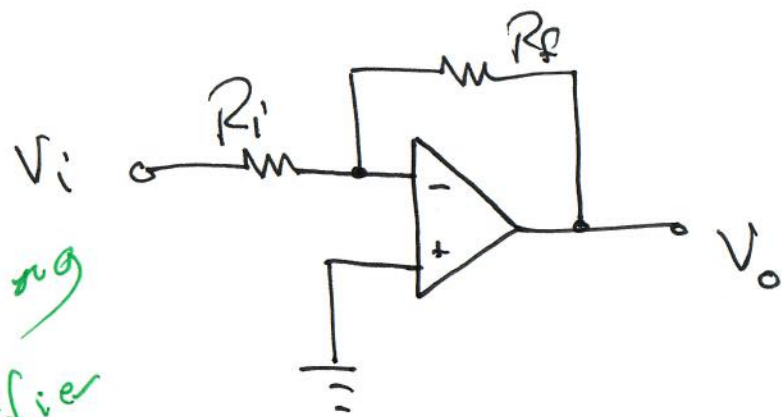



$$V_o = - \frac{R_f}{R_i} V_i$$

↑
amplifier
inverting

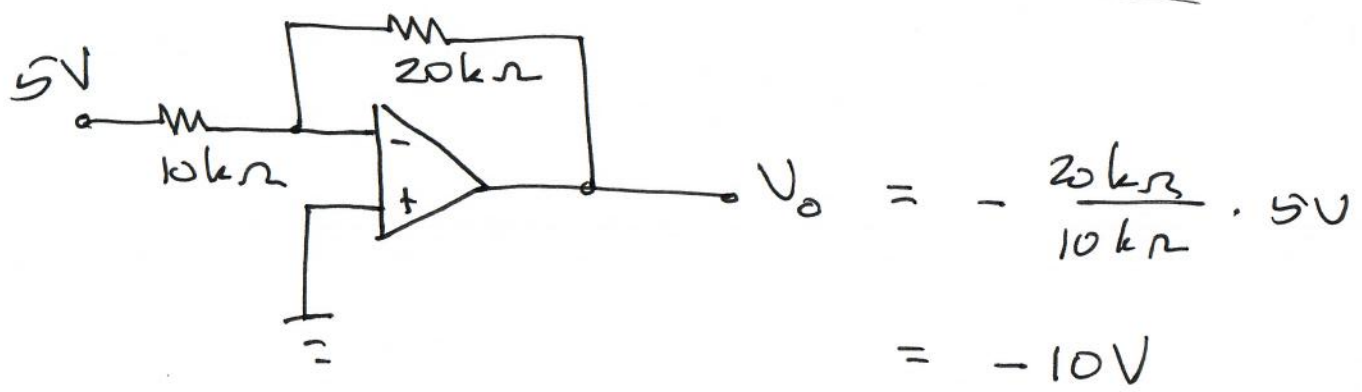

$$V_o = - \frac{20k\Omega}{10k\Omega} \cdot 5V$$

$$= -10V$$

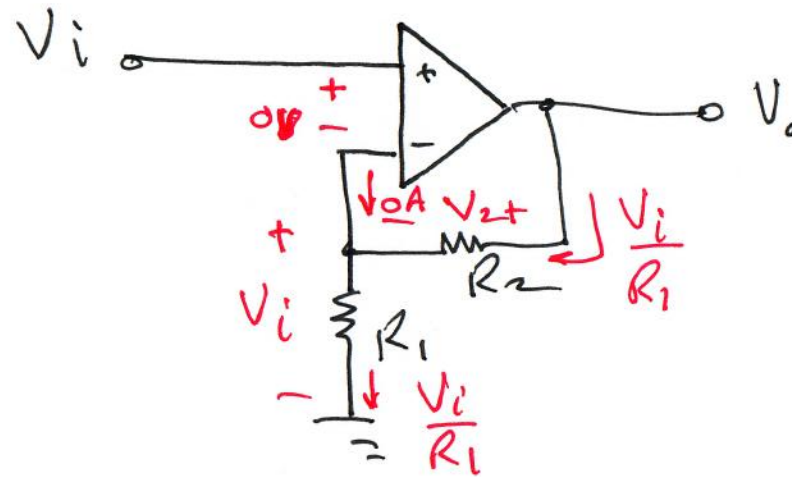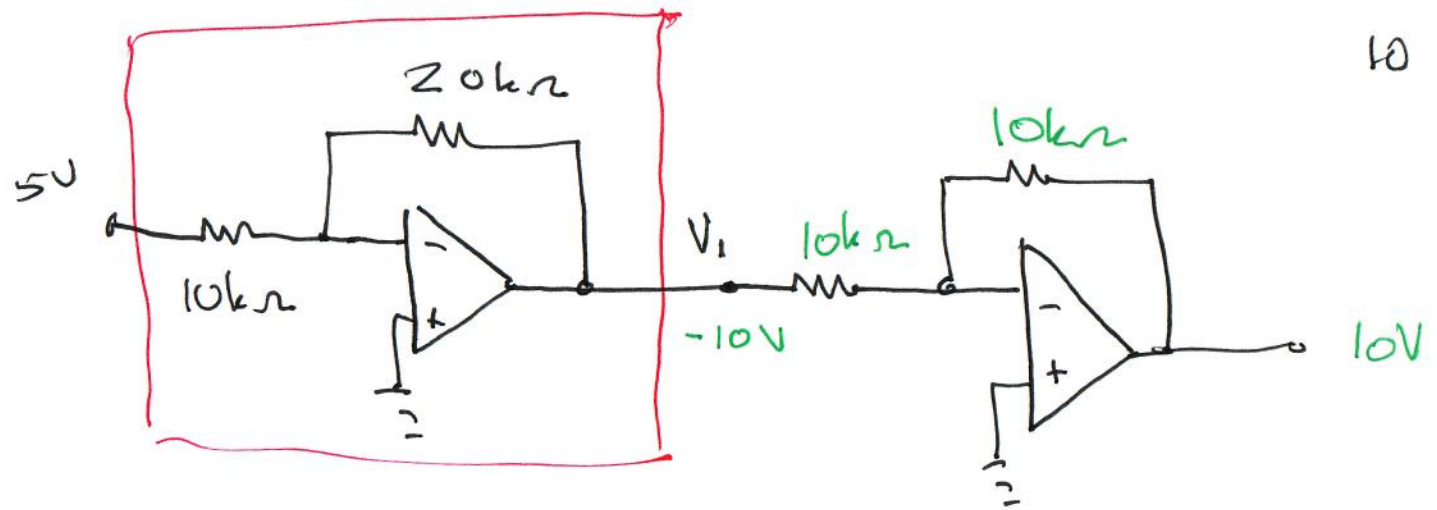


$$V_2 = R_2 \frac{V_i}{R_1}$$

$$= \frac{R_2}{R_1} V_i$$

$$V_o = V_2 + V_i$$

$$= \left(1 + \frac{R_2}{R_1}\right) V_i$$

Amplifier

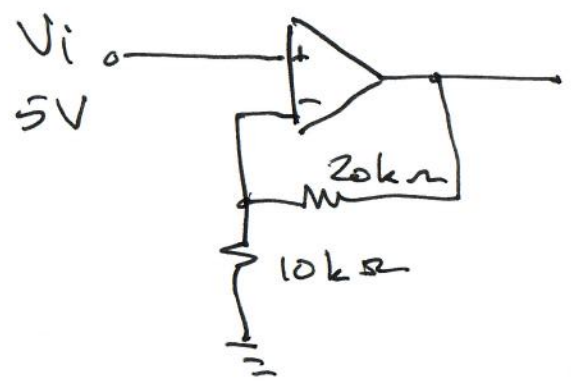

$$V_o = \left(1 + \frac{20k\Omega}{10k\Omega}\right) 5V$$
$$= 15V$$