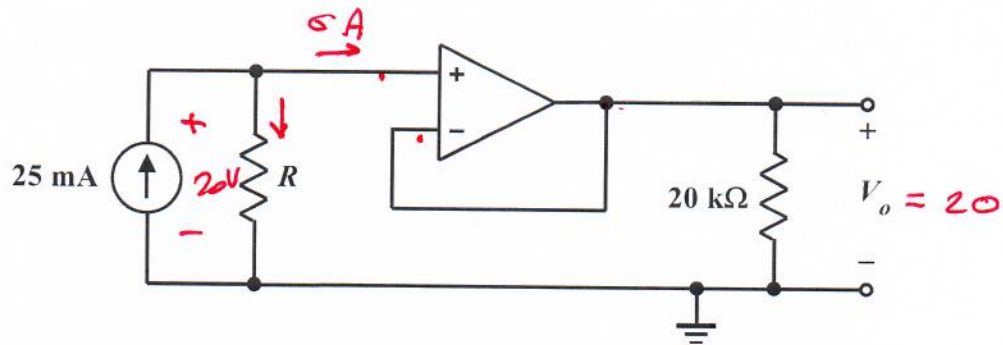



EE/EET 2240  
Homework Problem #039




The OpAmp is ideal. Determine the value of  $R$  required to make  $V_o = 20\text{ V}$ .

$$R(25\text{ mA}) = 20\text{ V}$$

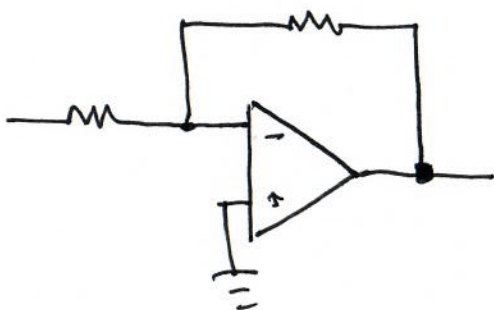
$$R = \frac{20}{25} \text{ k}\Omega$$
$$= 800 \Omega$$




Inverting  
Amplifier

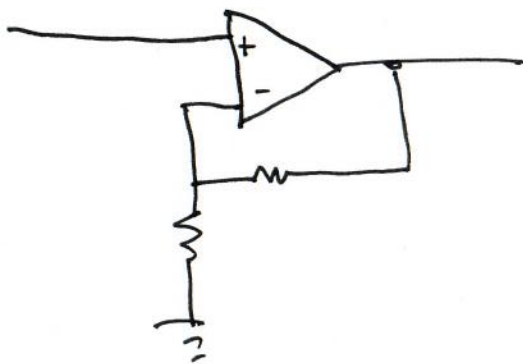


Non - Inverting  
Amplifier

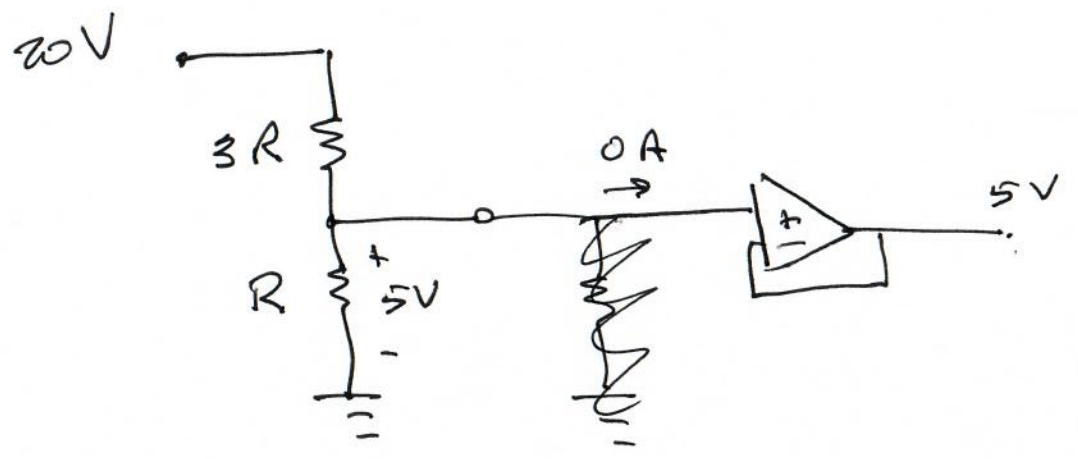

Buffer or Voltage Follower

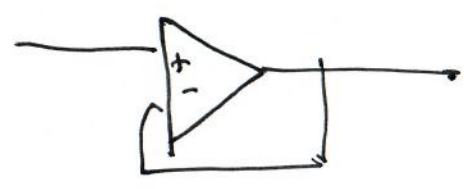

EE/EET 2240  
 Homework Problem #038

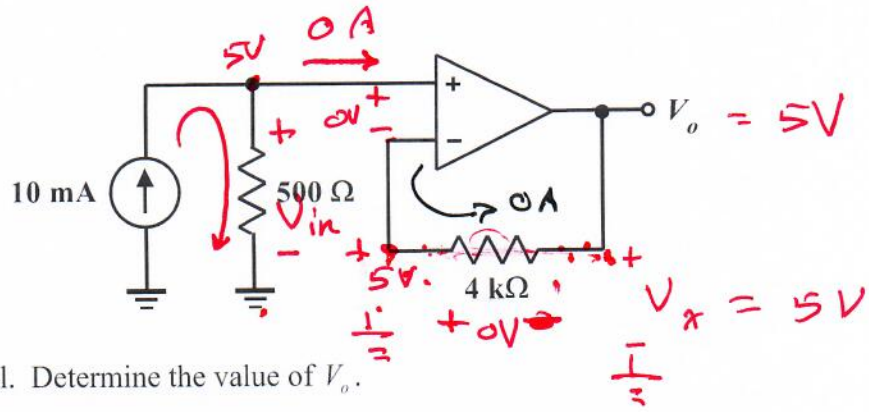

The OpAmp is ideal. Determine the value of  $V_o$ .

$$V_{in} = (10\text{mA})(500\Omega) = 5V$$



## Exam #2

Next Thursday, 10/25

9:30 AM - 10:45 AM

LIBR 3A in Pocatello

TAB 115 in IF

2. Mesh Analysis

\* 4. Linearity / Superposition w/o Controlled Sources


F.E. [ Thévenin / Norton / ST / Max. Power  
Controlled (or Dependent) Sources

\* 3. Op. Amps

1. Matrix Equation to Solve

$$\begin{bmatrix} 1 & 2 & 3 \\ 4 & 5 & 3 \\ 2 & 1 & 7 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 3 \end{bmatrix}$$

# Mesh Analysis

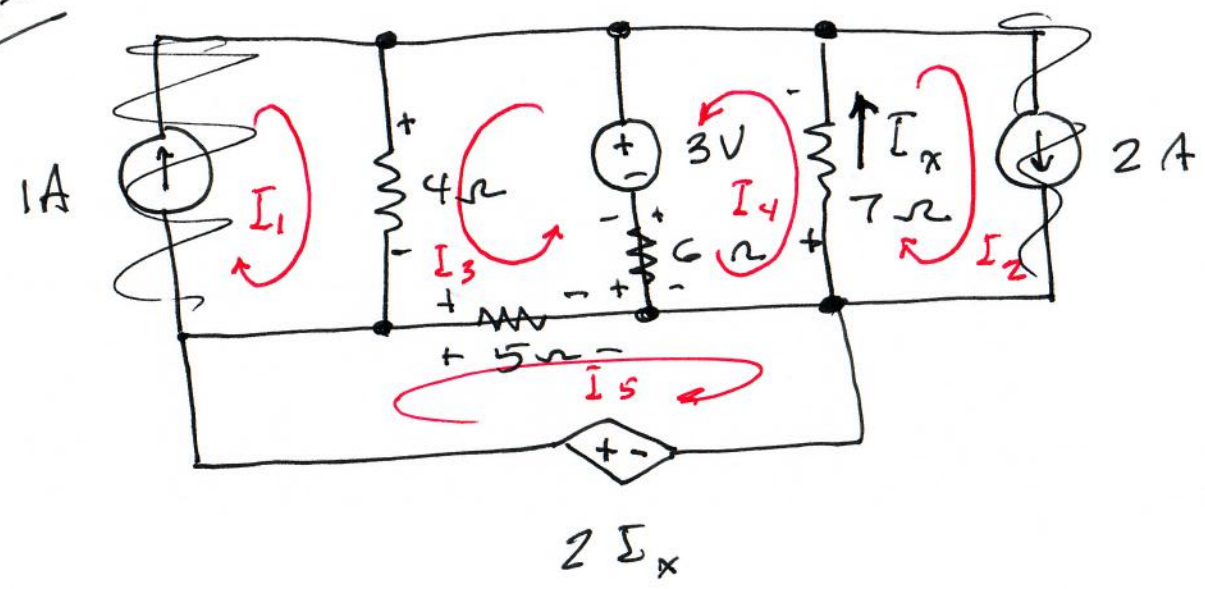

$$I_1 = 1 \quad (\text{constraint})$$

$$I_2 = 2 \quad (\text{constraint})$$

$$4(I_1 + I_3) + 5(I_3 + I_5) + 6(I_3 - I_4) - 3 = 0 \quad (\text{KVL for mesh 3})$$


$$+ 3 + 6(I_4 - I_3) + 7(I_2 + I_4) = 0 \quad (\text{KVL for mesh 4})$$

$$5(I_3 + I_5) - 2I_x = 0 \quad (\text{KVL for mesh 5})$$

$$I_x = I_2 + I_4 \quad (\text{definition})$$
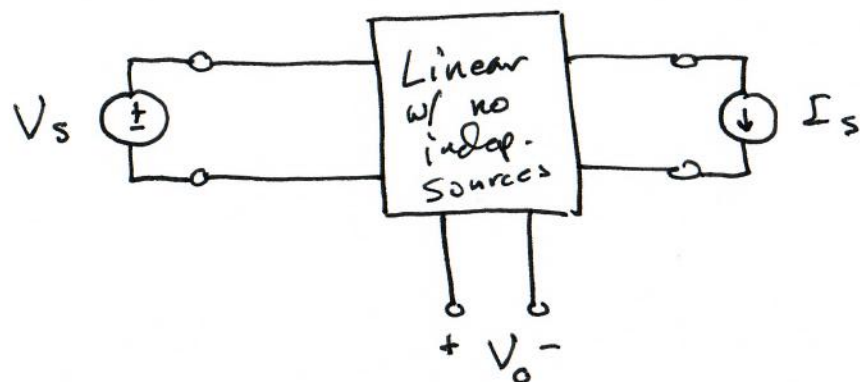
$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 4 & 0 & 15 & -6 & 5 & 0 \\ 0 & 7 & -6 & 13 & 0 & 0 \\ 0 & 0 & 5 & 0 & 5 & -2 \\ 0 & \cancel{0} & 0 & \cancel{0} & 0 & 1 \\ & -1 & & -1 & & \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \\ 3 \\ -3 \\ 0 \\ 0 \end{bmatrix}$$





For  $V_s = 2V$  and  $I_s = 5A$ ,  $V_o = 10V$

For  $V_s = 5V$  and  $I_s = 6A$ ,  $V_o = 15V$

For  $V_s = 3V$  and  $I_s = 4A$ ,  $V_o = ?$

Assume

$$V_o = \underline{K_1} V_s + K_2 I_s$$

$$2K_1 + 5K_2 = 10$$

$$5K_1 + 6K_2 = 15$$

$$\begin{bmatrix} 2 & 5 \\ 5 & 6 \end{bmatrix} \begin{bmatrix} K_1 \\ K_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 15 \end{bmatrix}$$

Solve for  $K_1 = \frac{15}{13}$

$$K_2 = \frac{20}{13}$$

$$V_o = \frac{15}{13} V_s + \frac{20}{13} \hat{I}_s$$

$$V_o = \frac{15}{13} (3) + \frac{20}{13} (4) = \frac{125}{13} \text{ V}$$