

# Exam # 2 Results

Highest: 100 (5)

Lowest: 33

Median: 85

Average: 82.9

---

91-100: 8


81-90: 11

71-80: 4

61-70: 3



0-60:  $\frac{2}{28}$

# Capacitor

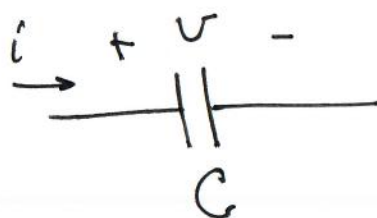

$$i = C \frac{dv}{dt}$$

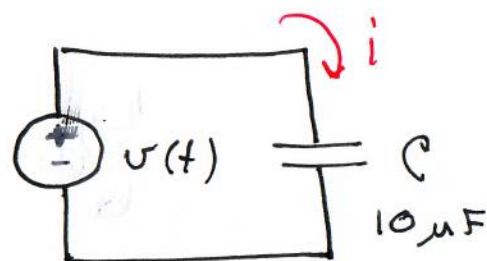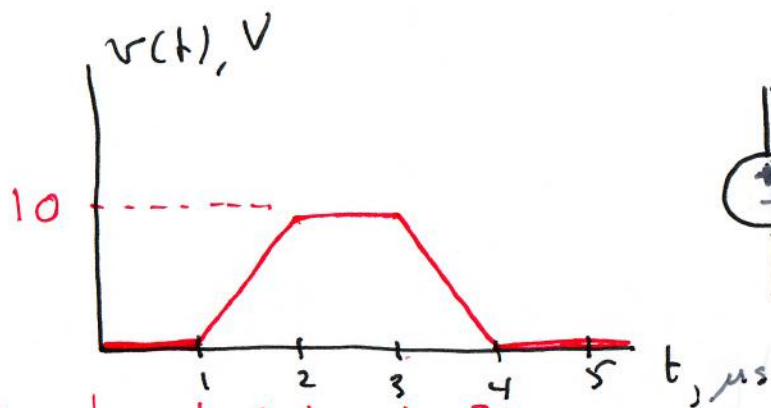
$$\text{or } v = \frac{1}{C} \int_{-\infty}^t i d\tau = \underbrace{\frac{1}{C} \int_{-\infty}^0 i d\tau}_{v(0) \text{ initial value}} + \frac{1}{C} \int_0^t i d\tau$$




Determine and sketch  $i(t)$ ,

$$i = C \frac{dv}{dt}$$

$\frac{dv}{dt}$	0	$10^7$	0	$-10^7$	0
$i$	0	100	0	-100	0

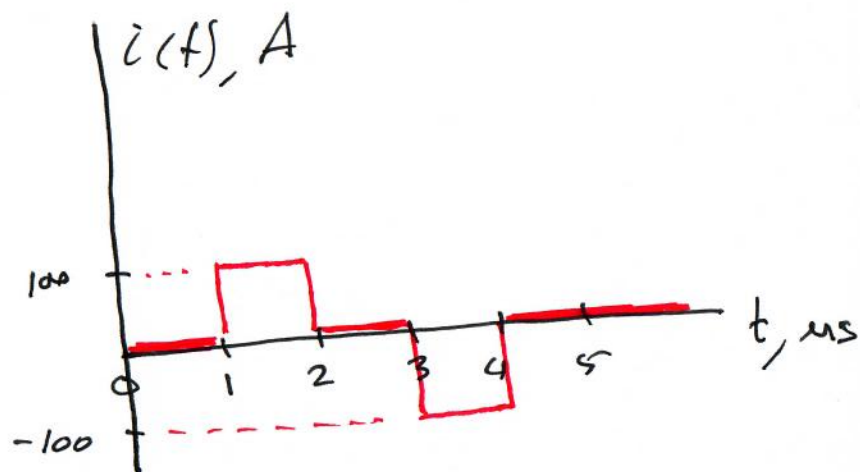

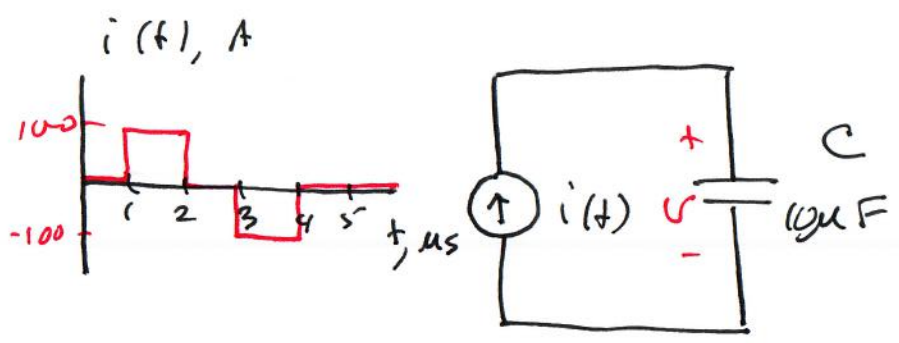


Find and sketch  $v(t)$ ,

The capacitor is initially uncharged.

$$Q = C V, \quad Q = 0 \Rightarrow V = 0$$

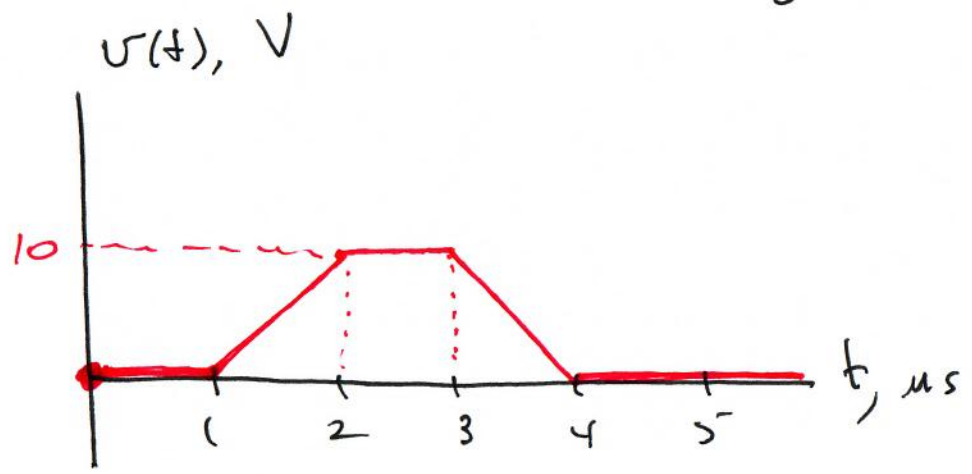
$$\begin{aligned}
 v(t) &= \frac{1}{C} \int_{-\infty}^0 i d\tau + \frac{1}{C} \int_0^t i d\tau \\
 &= \frac{1}{C} \int_0^t i dt \\
 &= 10^5 \int_0^t i dt
 \end{aligned}$$


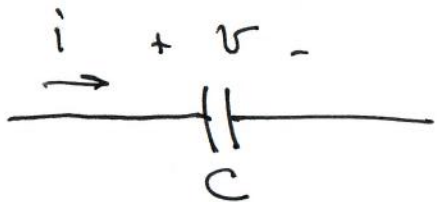
# Capacitor

$$i(t) = C \frac{dv}{dt}$$

$$v(t) = v(0) + \frac{1}{C} \int_0^t i \, dt$$



$$Q = CV$$

$$\frac{dQ}{dt} = i$$

$$i = C \frac{dv}{dt}$$

$$w_c = \frac{1}{2} C v^2$$

# Inductor

$$v(t) = L \frac{di}{dt}$$

$$i(t) = i(0) + \frac{1}{L} \int_0^t v \, dt$$



$v$  and  $i$  must satisfy the PSC



$$\lambda = Li$$

$$\frac{d\lambda}{dt} = v(t) \Rightarrow v(t) = L \frac{di}{dt}$$

$$w_L = \frac{1}{2} Li^2$$

# Spring

$$w_s = \frac{1}{2} k x^2$$

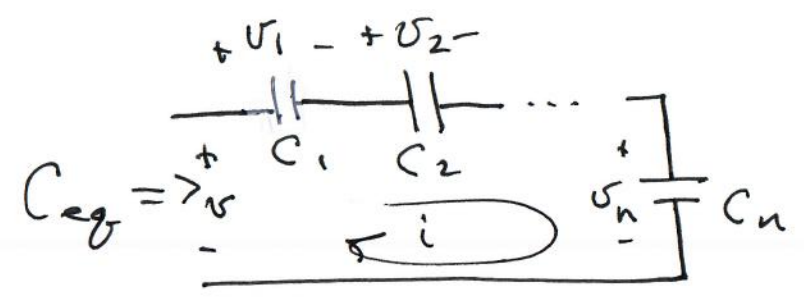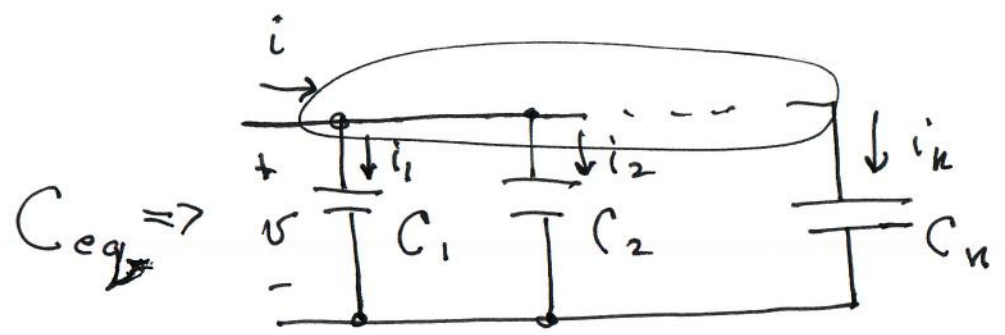

$$i_1 = C_1 \frac{dv}{dt}, \quad i_2 = C_2 \frac{dv}{dt}$$

$$\dots \quad i_n = C_n \frac{dv}{dt}$$

$$i = i_1 + i_2 + \dots + i_n$$

$$= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt}$$

$$i = \boxed{C_1 + C_2 + \dots + C_n} \frac{dv}{dt}$$

$$C_{eq}$$

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

Assume all capacitors are initially uncharged

$$v_1 = \frac{1}{C_1} \int_0^t i dt$$

$$v_2 = \frac{1}{C_2} \int_0^t i dt$$

⋮

$$v_n = \frac{1}{C_n} \int_0^t i dt$$

$$v = v_1 + v_2 + \dots + v_n$$

$$= \frac{1}{C_1} \int_0^t i dt + \frac{1}{C_2} \int_0^t i dt$$


$$+ \dots + \frac{1}{C_n} \int_0^t i dt$$

$$v = \boxed{\left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)} \int_0^t i dt$$

$\frac{1}{C_{eq}}$

$L_{eq}$

$\Rightarrow$

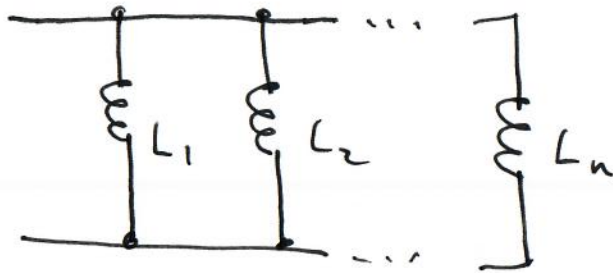

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \dots + \frac{1}{L_n}$$

$L_{eq} \Rightarrow$



$$L_{eq} = L_1 + L_2 + \dots + L_n$$

## Series

resistance  $R_{eq} = R_1 + \dots + R_n$

inductance  $L_{eq} = L_1 + \dots + L_n$

capacitance  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \dots + \frac{1}{C_n}$

conductance  $\frac{1}{G_{eq}} = \frac{1}{G_1} + \dots + \frac{1}{G_n}$

## Parallel


7

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

$$G_{eq} = G_1 + G_2 + \dots + G_n$$

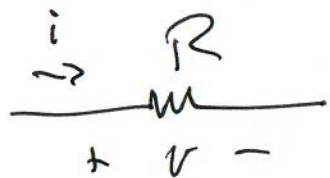

$$v = Ri$$

$$i = \frac{1}{R} v$$

G

$$G \triangleq \frac{1}{R}$$


units of  
conductance

are  $\Omega^{-1}$  or S


Siemens




Resistance units are ohms,  $\Omega$  

Inductance units are henrys, H 

Capacitance " " farads, F 

Conductance " " siemens, S 

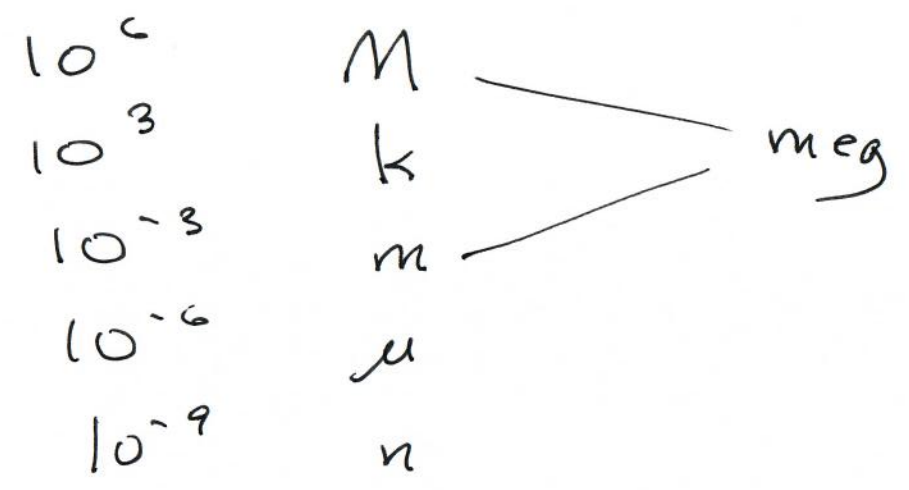



cadence.com

P Spice download