
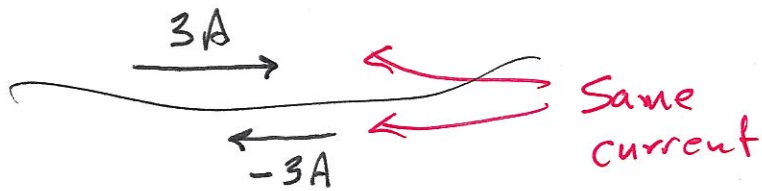


# Resistors

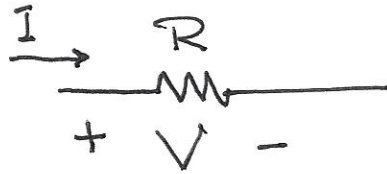

Passive Sign

Convention


$\Rightarrow$  always absorb  
power

$$P = VI$$


$V$  and  $I$  satisfy

Ohm's Law

$$V = R \cdot I$$

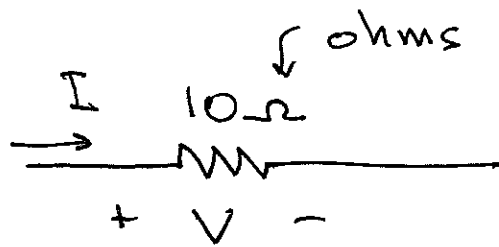

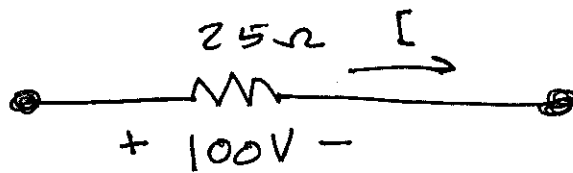If  $I = 3\text{ A}$ , then  $V = R \cdot I = 10 \cdot 3 = 30\text{ V}$



$$V = RI \Rightarrow I = \frac{V}{R} = \frac{100}{25} = 4\text{ A}$$

Alternately,

For this problem:

$$G = \frac{1}{R} = \frac{1}{25} = .04\text{ S}$$


$$= 40\text{ mS}$$

$$I = G V$$


↑  
conductance

$$G = \frac{1}{R}$$

mhos  
or  
Siemens  
S

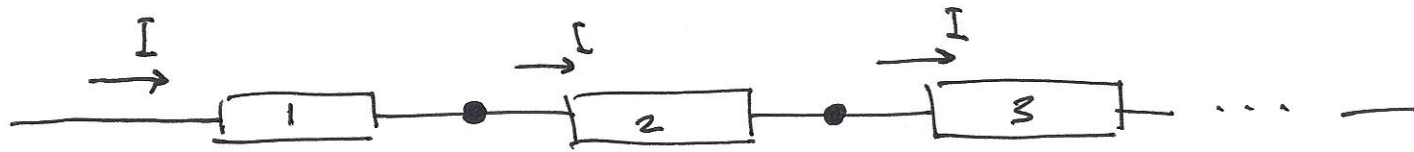

Connected in series

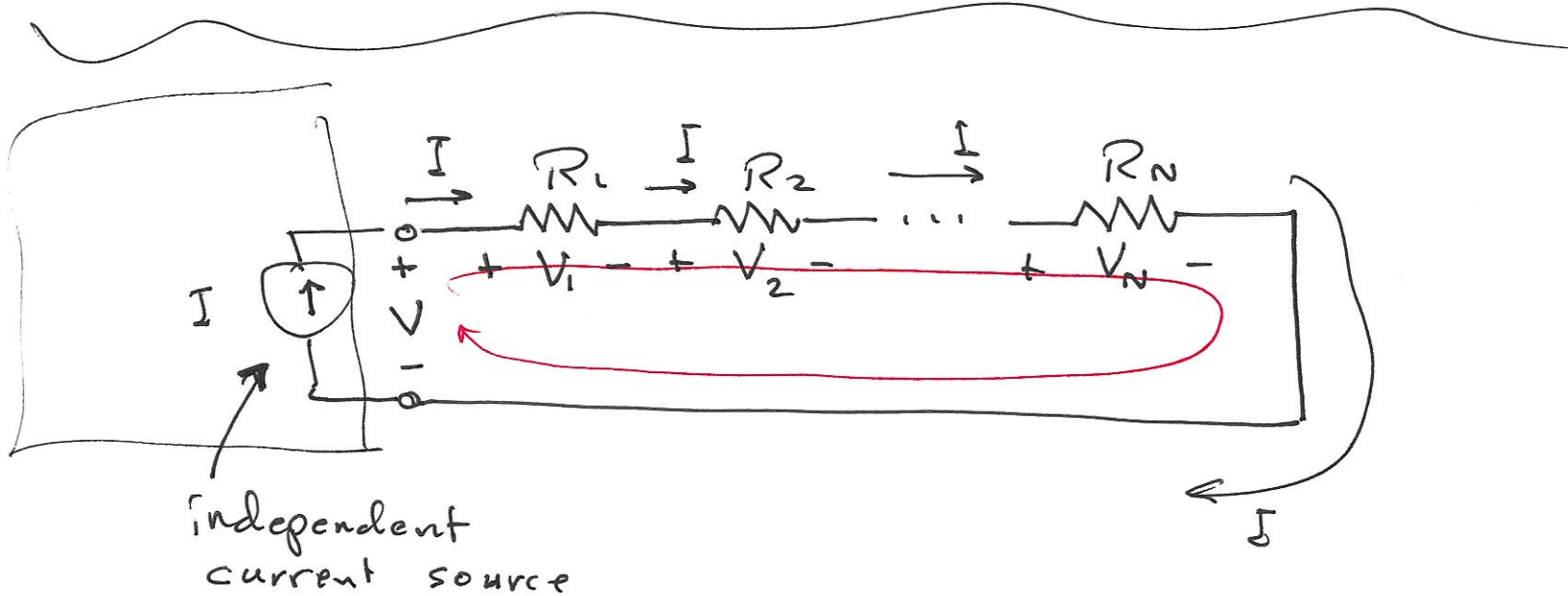


$$\text{KVL: } -V + V_1 + V_2 \dots + V_N = 0$$

$$V = V_1 + V_2 + \dots + V_N$$

$$V = R_1 I + R_2 I + \dots + R_N I$$



$$V = \underbrace{(R_1 + R_2 + \dots + R_N)}_{R_{eq}} I$$

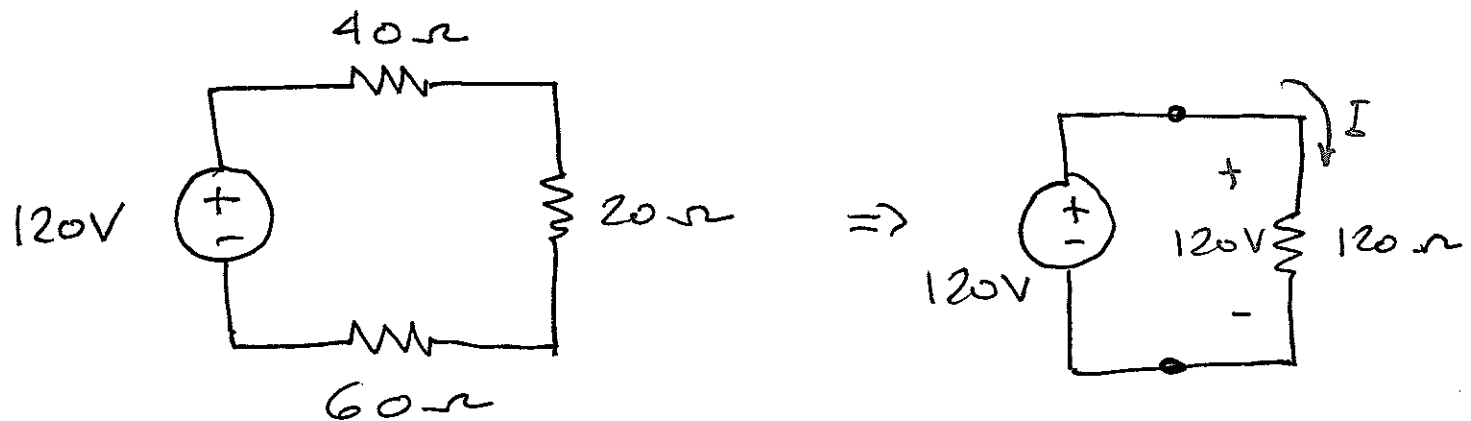For resistors in series,  $R_{eq} = R_1 + \dots + R_N$




$$R_{eq} = 40 + 20 + 60 = 120\Omega$$
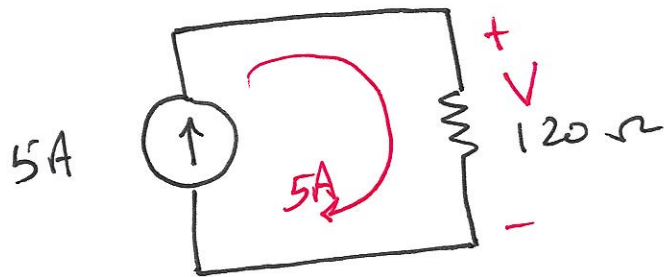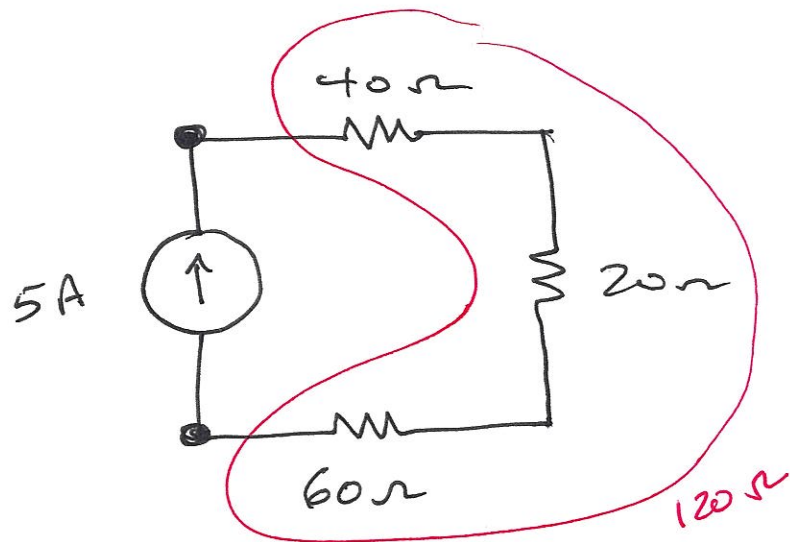
$$I = \frac{V}{R} = \frac{120}{120} = 1A$$


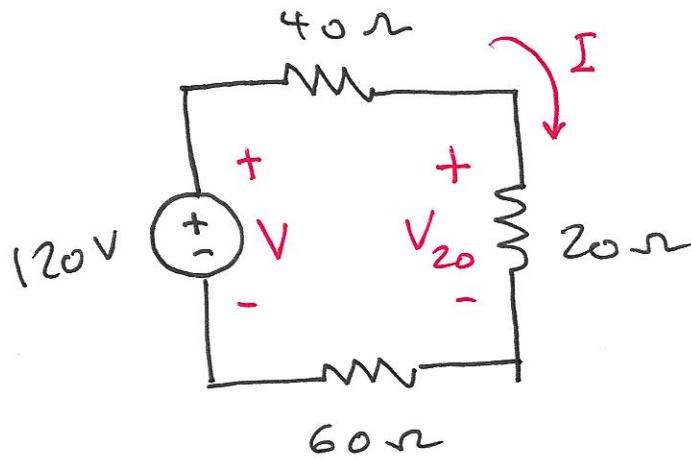
$$\begin{aligned} V &= RI \\ &= (120\ \Omega)(5A) \\ &= 600\ V \end{aligned}$$




$$V = \underbrace{(40 + 20 + 60)}_{R_{eq}} \text{ I}$$

$$V_{20} = 20 \text{ I}$$

$$\frac{V_{20}}{V} = \frac{20 \text{ I}}{(40 + 20 + 60) \text{ I}} = \frac{20}{40 + 20 + 60} = \frac{1}{6}$$

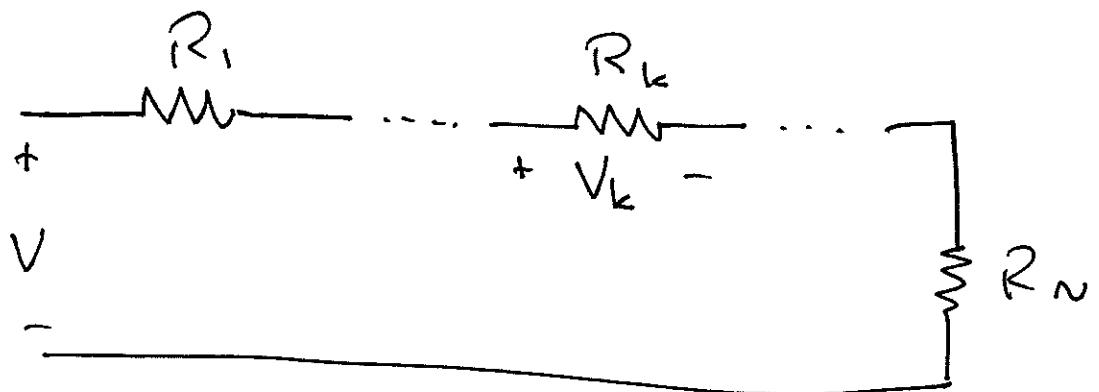
$$V_{20} = \frac{1}{6} V = \frac{1}{6} \cdot 120 \text{ V} = 20 \text{ V}$$




$$\frac{V_k}{V} = \frac{R_k}{R_1 + \dots + R_k + \dots + R_N}$$

Voltage Divider Equation

$$\frac{V_k}{V} = \frac{R_k}{R_{eq}}$$

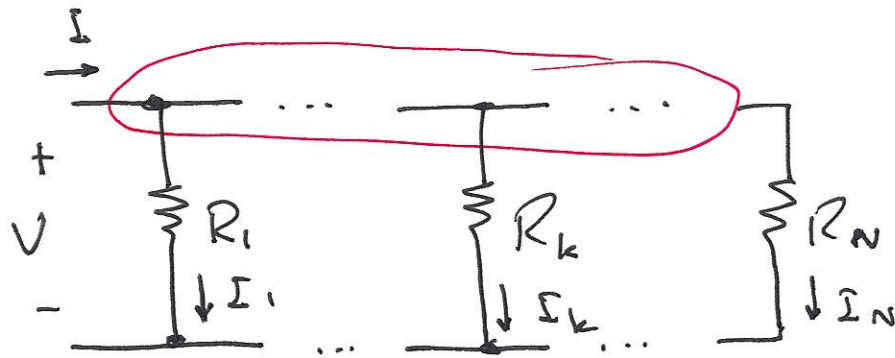

parallel connection

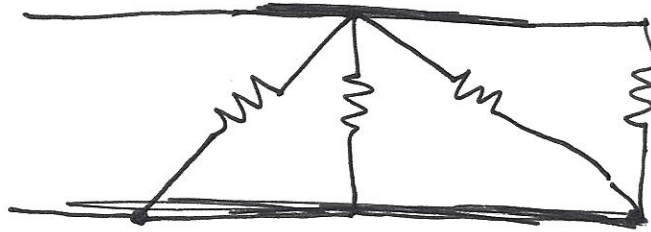

All are connected to the same pair of nodes

$$I_1 = \frac{V}{R_1} = G_1 V$$

$$\vdots$$

$$I_k = \frac{V}{R_k} = G_k V$$

$$\vdots$$

$$I_N = \frac{V}{R_N} = G_N V$$

$$\begin{aligned} I &= I_1 + \dots + I_k + \dots + I_N \\ &= G_1 V + \dots + G_k V + \dots + G_N V \\ &= \underbrace{(G_1 + \dots + G_k + \dots + G_N)}_{G_{eq}} V \end{aligned}$$




$$I = G_{eq} V$$

$$I_k = G_k V = \frac{1}{R_k} V$$

$$\frac{I_k}{I} = \frac{G_k V}{G_{eq} V} = \frac{G_k}{G_{eq}} = \frac{G_k}{\sum_{n=1}^N G_n}$$


$$\frac{I_k}{I} = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \dots + \frac{1}{R_k} + \dots + \frac{1}{R_N}}$$

Current  
Divider  
Equation

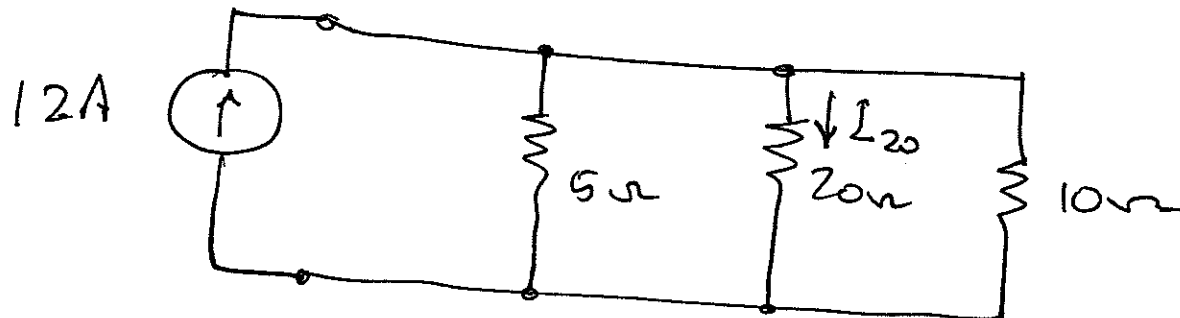

$$\frac{I_{20}}{12A} = \frac{\frac{1}{20}}{\frac{1}{5} + \frac{1}{20} + \frac{1}{10}} = \frac{1}{7}$$

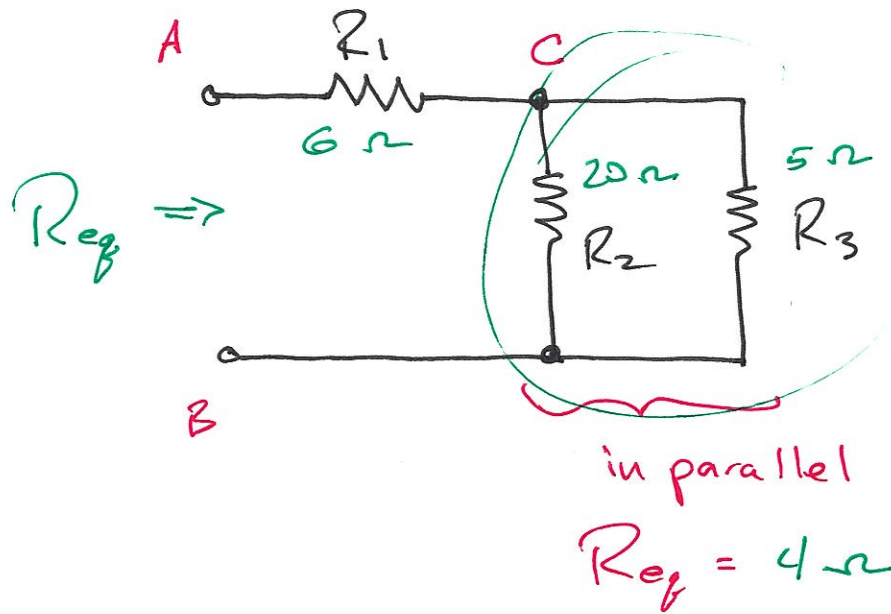
$$I_{20} = \frac{1}{7} (12A) = \frac{12}{7} A$$





$$\frac{1}{R_{eq}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} \cdot \frac{R_2 R_3}{R_2 R_3}$$

$$= \frac{R_2 R_3}{R_3 + R_2}$$

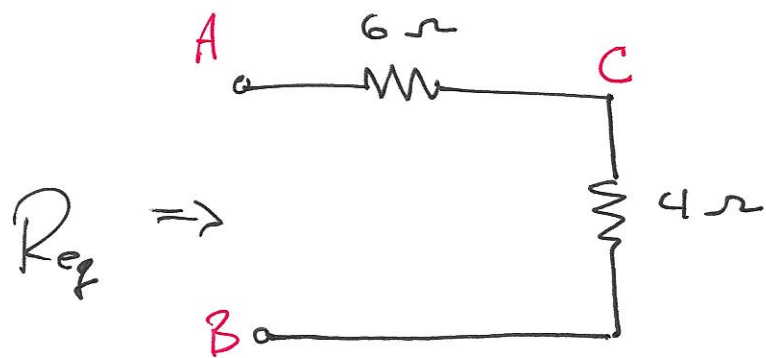


$$R_{eq} = 6 + 4 = 10 \Omega$$

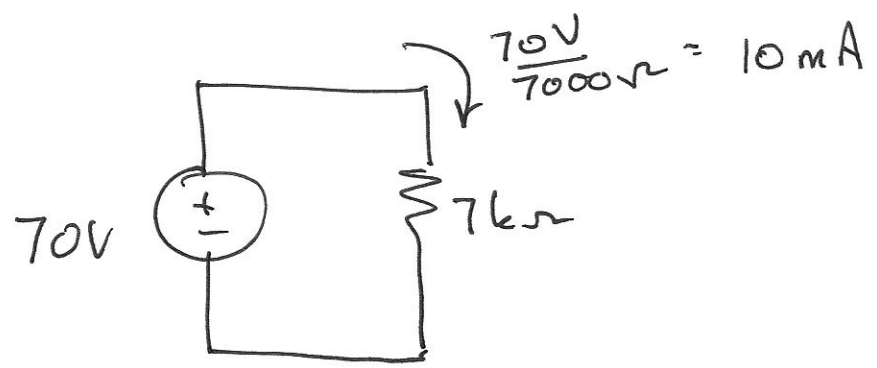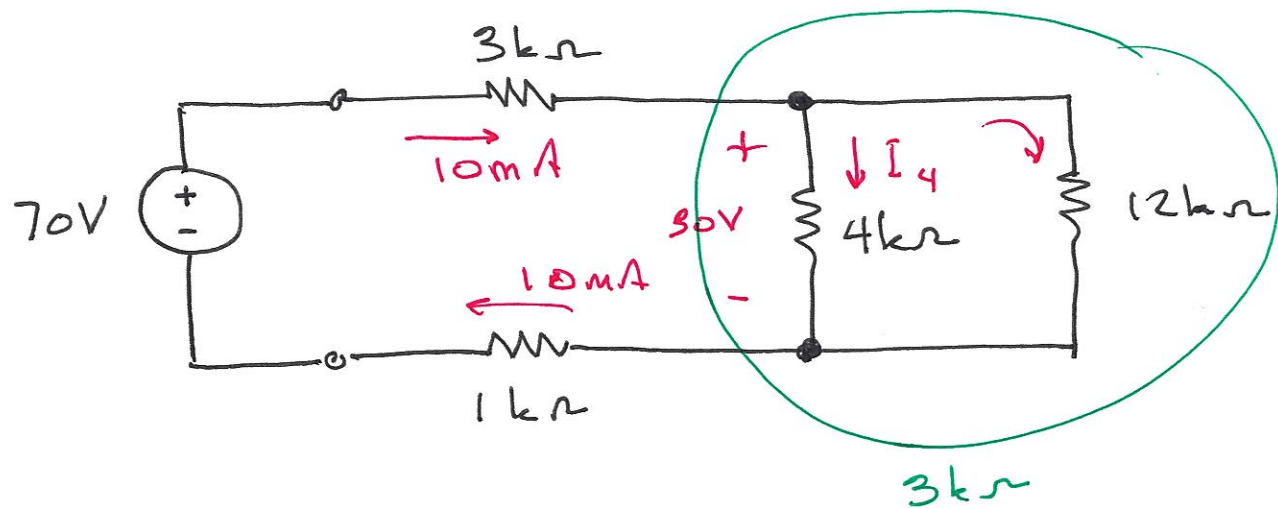


$$I_4 = \frac{30V}{4k\Omega} = 7.5mA$$

$$I_4 = \frac{1}{\frac{1}{4k\Omega} + \frac{1}{12k\Omega}} \cdot 10mA$$

$$= 7.5mA$$

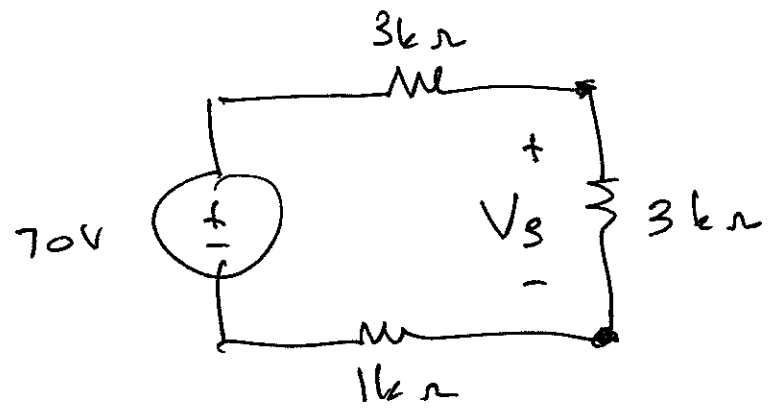
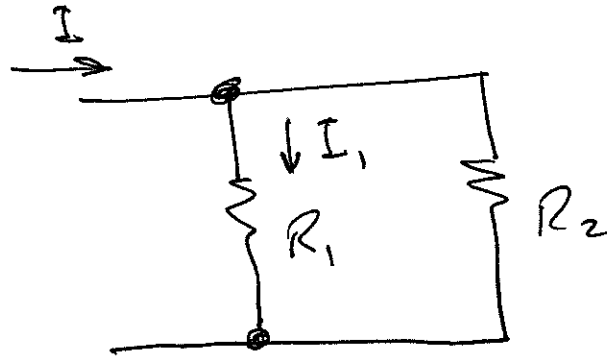
$$V_3 = \frac{3k}{3k + 3k + 1k} \cdot 70$$
$$= 30V$$



$$\frac{I_1}{I} = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} \cdot \frac{R_1 R_2}{R_1 R_2} = \frac{R_2}{R_1 + R_2}$$

For 2 resistors:

$$\boxed{\frac{I_1}{I} = \frac{R_2}{R_1 + R_2}}$$