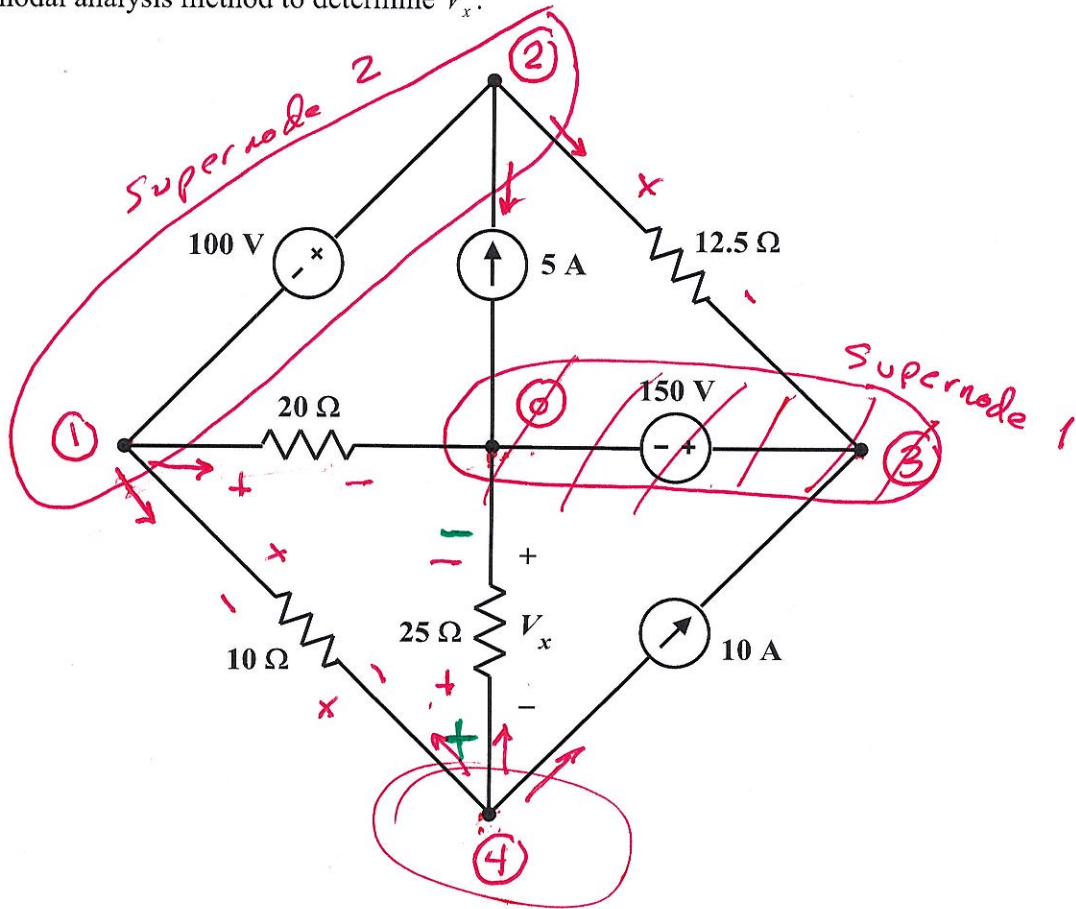


Use the nodal analysis method to determine V_x .



$$V_3 = 150 \quad (\text{constraint, supernode 1})$$

$$V_2 - V_1 = 100 \quad (\text{constraint, supernode 2})$$

$$\frac{V_2 - V_3}{12.5} - 5 + \frac{V_1}{20} + \frac{V_1 - V_4}{10} = 0 \quad (\text{KCL for supernode 2})$$

$$10 + \frac{V_4}{25} + \frac{V_4 - V_1}{10} = 0 \quad (\text{KCL for node 4})$$


$$V_x = -V_4$$

$$\begin{bmatrix} 0 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 \\ 3/20 & 1/12.5 & -1/12.5 & -1/10 \\ -1/10 & 0 & 0 & 1/50 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 150 \\ 100 \\ 5 \\ -10 \end{bmatrix}$$

Practice Problem 6 on Nodal Analysis

Use the nodal analysis method to determine V_x and I_y .

Practice
Problem 7
Nodal Analysis

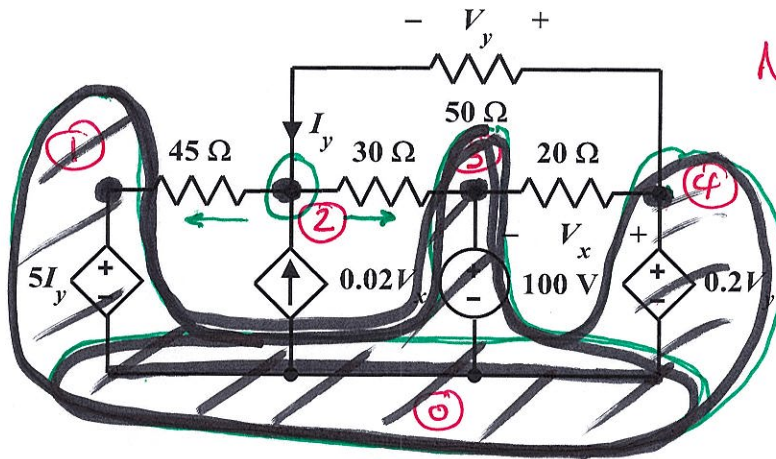

$$V_1 = 5I_y$$

$$V_4 = 0.2V_y$$

$$V_3 = 100$$

$$I_y + 0.02V_x = \left(\frac{V_2 - V_3}{30} \right) + \left(\frac{V_2 - V_1}{45} \right) = 0$$

$$V_y = V_4 - V_2$$

$$V_x = V_4 - V_3$$

$$I_y = \frac{V_4 - V_2}{50}$$

$$\begin{array}{c}
 v_1 \quad v_2 \quad v_3 \quad v_4 \quad v_x \quad v_y \quad I_y \\
 \left[\begin{array}{ccccccc}
 1 & 0 & 0 & 0 & 0 & 0 & -5 \\
 0 & 0 & 0 & 1 & 0 & -0.2 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 1/45 = 1/18 & 1/30 & 0 & 0.02 & 0 & 0 & 1 \\
 0 & -1 & 0 & 1 & 0 & -1 & 0 \\
 0 & 0 & 1 & -1 & 1 & 0 & 0 \\
 0 & 1/50 & 0 & -1/50 & 0 & 0 & 1
 \end{array} \right]
 \begin{array}{c}
 v_1 \\
 v_2 \\
 v_3 \\
 v_4 \\
 v_x \\
 v_y \\
 I_y
 \end{array}
 =
 \begin{array}{c}
 1 \\
 1 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{array}
 \end{array}$$