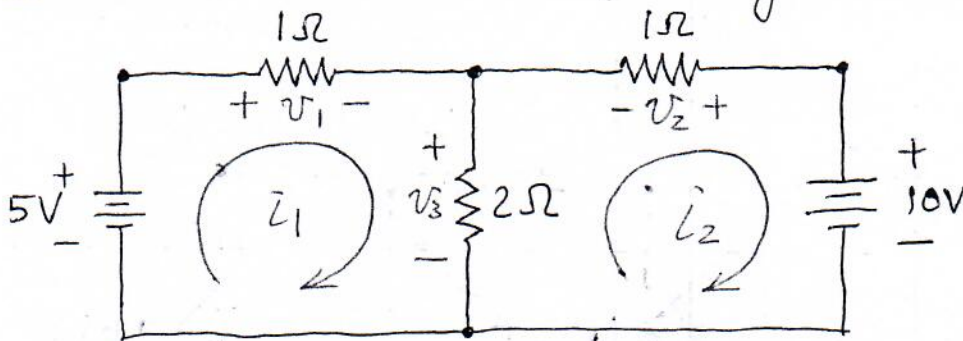


△ Mesh analysis -

A planar network partitions the plane into regions called "meshes".

The first step of mesh analysis is to use a "mesh current", around each mesh, either CW or CCW. To see this, consider the following circuit:



Two mesh currents, i_1 and i_2 , are set up for the two meshes. Based on this setup, $(i_1 - i_2)$ represents the current going down through the $2\text{-}\Omega$ resistor.

Now, use KVL to each mesh, :

$$\text{"Mesh } i_1\text{" : } v_1 + v_3 = 5$$

$$\text{By Ohm's Law : } \underbrace{1i_1}_{v_1} + \underbrace{2(i_1 - i_2)}_{v_3} = 5$$

$$\Rightarrow 3i_1 - 2i_2 = 5 \text{ ----- } (\alpha)$$

$$\text{"Mesh } i_2\text{" : } v_2 + v_3 = 10$$


$$\text{By Ohm's Law : } -1i_2 + 2(i_1 - i_2) = 10$$

$$\Rightarrow 2i_1 - 3i_2 = 10 \text{ ----- } (\beta)$$

Using (α) , (β) we can solve to get $i_1 = -1\text{A}$, $i_2 = -4\text{A}$.

Once all the mesh currents are found, we can find any current or voltage in the circuit. For example, $(i_1 - i_2) = 3A$;
 $v_1 = 1i_1 = -1V$, $v_2 = -1i_2 = 4V$, $v_3 = 2(i_1 - i_2) = 6V$.

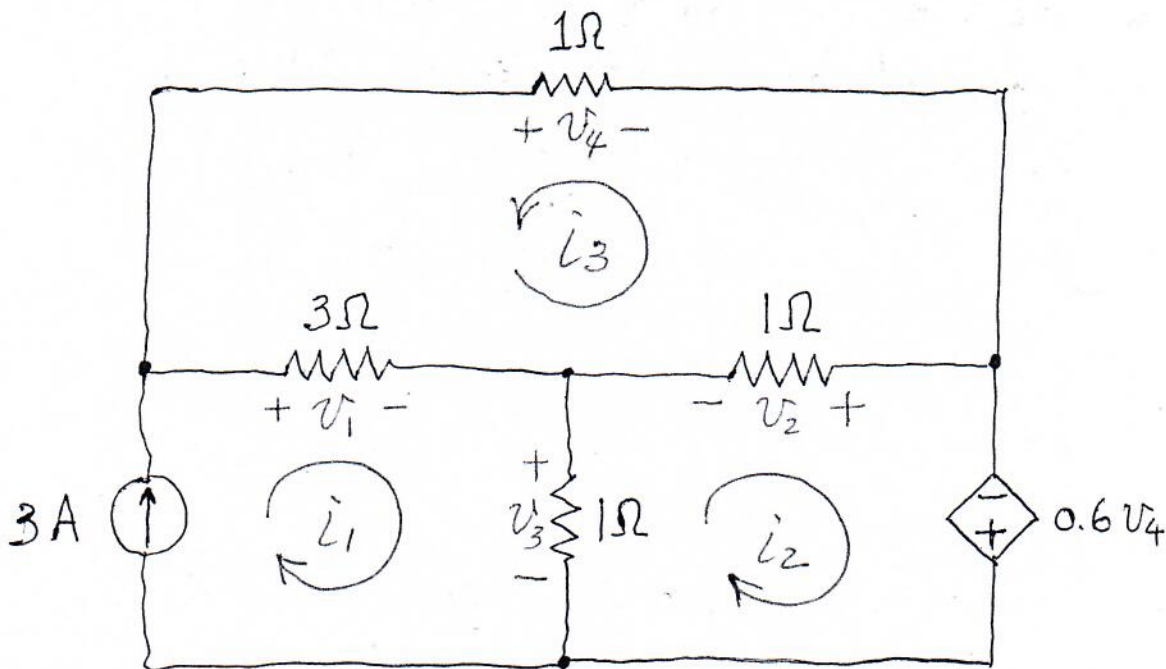△ Let's look at another more complex circuit:



Directions of mesh currents i_1, i_2, i_3 are arbitrarily chosen. By inspection, we see that $i_1 = 3A$.
 So, only i_2 and i_3 need to be found.

By KVL on "mesh i_2 ":

$$v_2 + v_3 + 0.6v_4 = 0$$

Ohm's law:

$$1(-i_2 - i_3) + 1(i_1 - i_2) + 0.6(-1i_3) = 0$$

$$\Rightarrow 10i_2 + 8i_3 = 5i_1 = 5(3A) = 15 \dots \dots \dots (\alpha)$$

By KVL on "mesh i_3 ":

$$v_1 - v_2 - v_4 = 0$$

$$3(i_1 + i_3) - 1(-i_2 - i_3) - (-1i_3) = 0$$

$$\Rightarrow i_2 + 5i_3 = -3i_1 = -9 \dots \dots \dots (\beta)$$

Solving (α) , (β) , we get $i_2 = 3.5A$, $i_3 = -2.5A$

By Ohm's law, since $i_1 = 3A$,

$$v_1 = 3(i_1 + i_3) = 1.5V$$

$$v_2 = 1(-i_2 - i_3) = -1V$$

$$v_3 = 1(i_1 - i_2) = -0.5V$$

$$v_4 = -1i_3 = 2.5V$$