

EE 2240  
**Problem #07**

The current through a  $10\ \mu\text{F}$  capacitor is given by the waveform shown. Accurately sketch the waveform for the voltage across the capacitor if it is initially uncharged.

