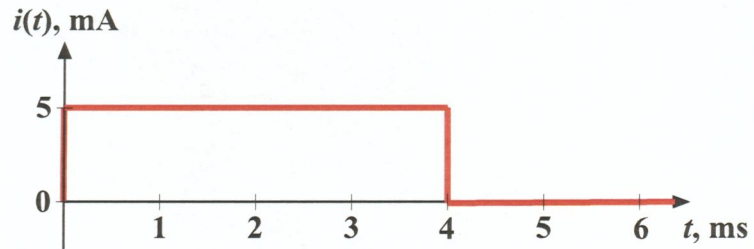


EE 2240
Problem #07

The current through a $10 \mu\text{F}$ capacitor is given by the waveform shown. Accurately sketch the waveform for the voltage across the capacitor if it is initially uncharged.



$$\begin{aligned} v(t) &= v(0) + \frac{1}{C} \int_0^t i(t) dt \\ &= 0 + 10^{-5} \int_0^t i(t) dt \\ &= \begin{cases} 0 & t = 0 \\ 10^{-5} \times 0.005t = 500t \text{ V} & 0 < t < 4 \text{ ms} \\ 10^{-5} \times 0.005 \times 0.004 = 2 \text{ V} & 4 \text{ ms} < t \end{cases} \end{aligned}$$

