

EE 2240  
**Problem #09**

The charge stored in a  $12 \mu\text{F}$  capacitor is shown below. Accurately sketch the waveform for the current through the capacitor.

