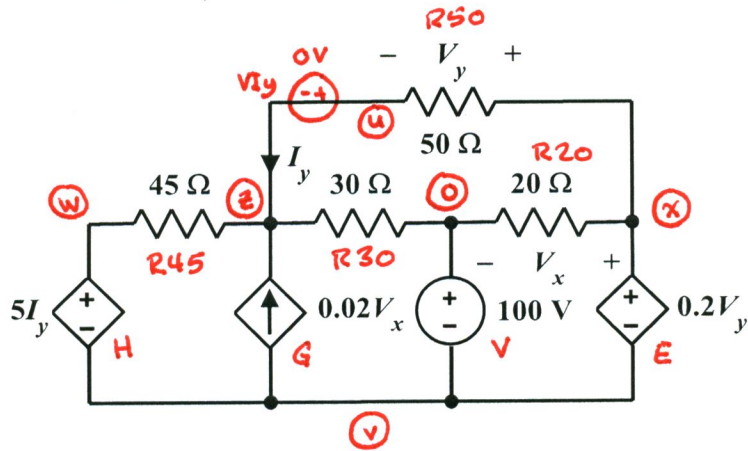


EE 2240
Problem #07

Use PSpice to determine V_x and I_y .



```
Problem #07
VIy u z dc 0
R50 x u 50
R45 w z 45
R30 z 0 30
R20 0 x 20
H w v VIy 5
G v z x 0 0.02
V 0 v dc 100
E x v x u 0.2
.end
```

**** 02/06/15 00:07:31 ***** PSpice Lite (October 2012) ***** ID# 10813 ****

Problem #07

**** CIRCUIT DESCRIPTION

```
VIy      u      z      dc      0
R50      x      u      50
R45      w      z      45
R30      z      0      30
R20      0      x      20
H        w      v      VIy     5
G        v      z      x      0      0.02
V        0      v      dc     100
E        x      v      x      u      0.2
.end
♀
```

**** 02/06/15 00:07:31 ***** PSpice Lite (October 2012) ***** ID# 10813 ****

Problem #07

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(u)	-84.9060	(v)	-100.0000	(w)	-101.8900	(x)	-103.7700
(z)	-84.9060						

This is V_x . (-103.77 V)

VOLTAGE SOURCE CURRENTS

NAME CURRENT

VIy -3.774E-01 ← This is I_y. (- 0.3774 A)
V -8.019E+00

TOTAL POWER DISSIPATION 8.02E+02 WATTS

JOB CONCLUDED

♀
**** 02/06/15 00:07:31 ***** PSpice Lite (October 2012) ***** ID# 10813 ****

Problem #07

**** JOB STATISTICS SUMMARY

♀ Total job time (using Solver 1) = 0.00