

EE 2240  
Problem #01

Find the value of  $L_{eq}$ .

