

EE 2240
Problem #02

Determine the equivalent inductance.

