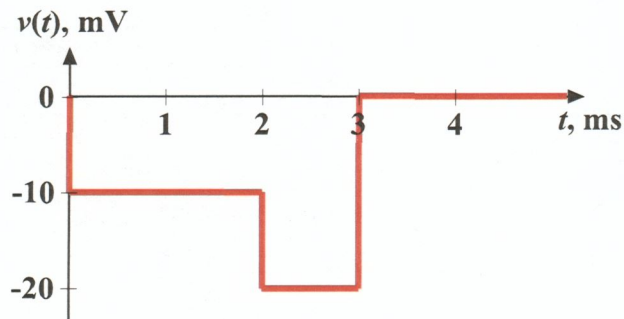


EE 2240  
**Problem #04**

The waveform for the voltage across a  $20 \mu\text{H}$  inductor is shown. Determine, and accurately sketch, the waveform for the inductor current if  $v(t) = 0$  for  $t < 0$ .



$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^0 v(\tau) d\tau + \frac{1}{L} \int_0^t v(\tau) d\tau = 5 \times 10^4 \int_0^t v(\tau) d\tau$$

For  $0 < t < 2 \text{ ms}$ :  $v(t) = -10 \text{ mV}$

$$i(t) = 5 \times 10^4 \int_0^t (-10 \times 10^{-3}) d\tau = -500 \tau \Big|_0^t = -500t \text{ A}$$

For  $2 \text{ ms} < t < 3 \text{ ms}$ :  $v(t) = -20 \text{ mV}$

$$\begin{aligned} i(t) &= -500 (2 \times 10^{-3}) + 5 \times 10^4 \int_{2 \text{ ms}}^t (-20 \times 10^{-3}) d\tau \\ &= -1 - 1000 \tau \Big|_{2 \text{ ms}}^t = 1 - 1000t \text{ A} \end{aligned}$$

For  $3 \text{ ms} < t$ :  $v(t) = 0$

$$i(t) = 1 - 1000 (3 \text{ ms}) = 1 - 3 = -2 \text{ A}$$

