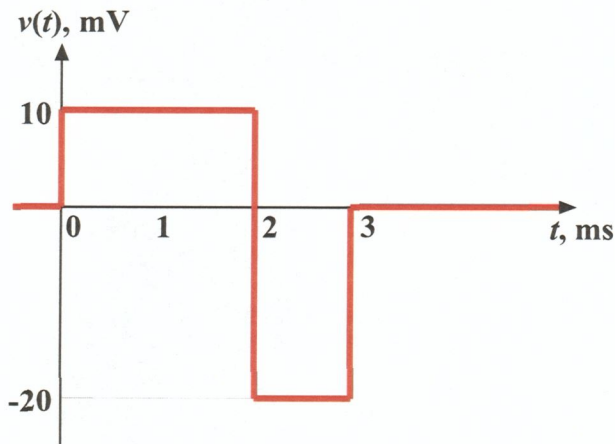


EE 2240  
**Problem #05**

The waveform for the voltage across a 20 mH inductor is shown. Determine, and accurately sketch, the waveform for the inductor current if  $v(t) = 0$  for  $t < 0$ .



$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^0 v(\tau) d\tau + \frac{1}{L} \int_0^t v(\tau) d\tau = 50 \int_0^t v(\tau) d\tau$$

For  $0 < t < 2 \text{ ms}$ :  $v(t) = 10 \text{ mV}$

$$i(t) = 50 \int_0^t (10 \times 10^{-3}) d\tau = 0.5t \text{ A}$$

For  $2 \text{ ms} < t < 3 \text{ ms}$ :  $v(t) = -20 \text{ mV}$

$$i(t) = 0.5(2 \times 10^{-3}) + 50 \int_{2 \text{ ms}}^t (-20 \times 10^{-3}) d\tau$$

$$= 0.001 - 1(t - 2 \text{ ms}) = 0.003 - t \text{ A}$$

For  $3 \text{ ms} < t$ :  $v(t) = 0$

$$i(t) = 0.003 - 0.003 = 0 \text{ A}$$

