

EE 2240
Problem #06

The current through a 60 mH inductor is shown. Determine and sketch the voltage across that inductor.

