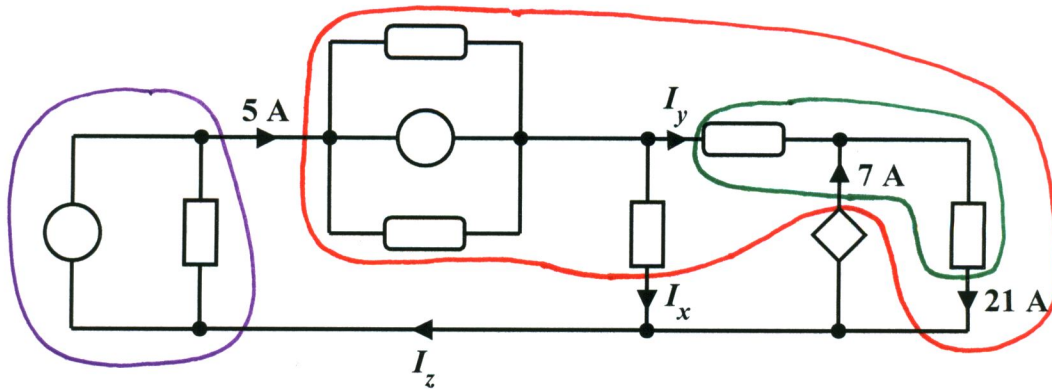


EE 2240  
Problem #07

Given the circuit shown below:



a. Determine the value of  $I_x$ .

$$5A - I_x + 7A - 21A = 0$$
$$\Rightarrow I_x = -9A$$

b. Determine the value of  $I_y$ .

$$I_y + 7A - 21A = 0$$
$$\Rightarrow I_y = 14A$$

c. Determine the value of  $I_z$ .

$$I_z - 5A = 0 \Rightarrow I_z = 5A$$