

EE 2240
Problem #09

Find V_{bd} and V_{ac} .

