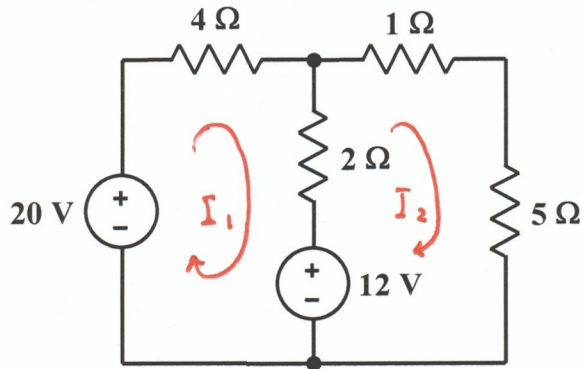


EE 2240
Problem #03



- a. How many equations are necessary to analyze this circuit by the mesh analysis method?

2

Use the method discussed in class to:

- b. Develop the mesh equations describing the circuit.

$$\begin{aligned} -20 + 4I_1 + 2(I_1 - I_2) + 12 &= 0 \\ -12 + 2(I_2 - I_1) + 1I_2 + 5I_2 &= 0 \end{aligned}$$

- c. Write the mesh equations in the matrix form discussed in class.

$$\begin{bmatrix} 6 & -2 \\ -2 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 8 \\ 12 \end{bmatrix}$$

- d. Solve the mesh equations.

$$I_1 = 2 \text{ A} \qquad I_2 = 2 \text{ A}$$

- e. Use the results of your mesh analysis to determine the amount of power absorbed by the 5Ω resistor.

$$P = (5\Omega)(I_2)^2 = 20 \text{ W}$$