

EE 2240
Problem #05

Find I_o using mesh analysis.

