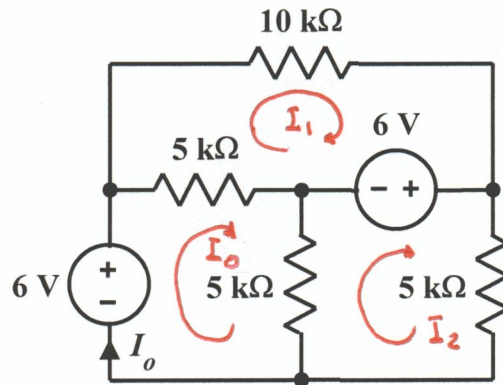


EE 2240  
**Problem #05**

Find  $I_o$  using mesh analysis.



$$\begin{aligned}
 -6 + 5000(I_0 - I_1) + 5000(I_0 - I_2) &= 0 && \text{(mesh 0)} \\
 5000(I_1 - I_0) + 10000I_1 + 6 &= 0 && \text{(mesh 1)} \\
 5000(I_2 - I_0) - 6 + 5000I_2 &= 0 && \text{(mesh 2)}
 \end{aligned}$$

In matrix form:

$$\begin{bmatrix} 10000 & -5000 & -5000 \\ -5000 & 15000 & 0 \\ -5000 & 0 & 10000 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -6 \\ 6 \end{bmatrix}$$

Solving yields  $I_0 = 1.2 \text{ mA}$