

EE 2240
Problem #02

Find V_x using the nodal analysis method.

