

EE 2240
Problem #03

Use the nodal analysis method to determine the voltage across each conductance. Then apply Ohm's Law to determine the values of I_1 and I_2 .

