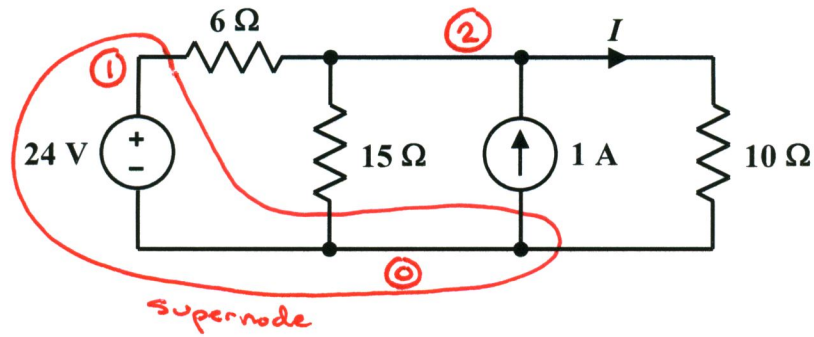


EE 2240  
Problem #05

Use the nodal analysis method to determine the voltage across the  $10\ \Omega$  resistor. Then apply Ohm's Law to determine  $I$ .



$$V_1 = 24V \quad (\text{supernode constraint equation})$$

$$\frac{V_2 - V_1}{6\Omega} + \frac{V_2}{15\Omega} - 1 + \frac{V_2}{10\Omega} = 0 \quad (\text{KCL at node 2})$$

$$\begin{bmatrix} 1 & 0 \\ -1/6 & 1/3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 24 \\ 1 \end{bmatrix}$$

$$V_2 = 15V$$

$$I = \frac{V_2}{10\Omega} = 1.5A$$