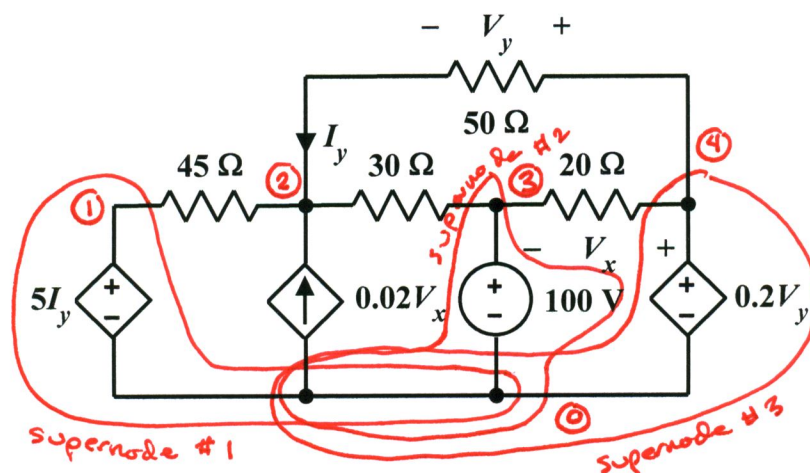


EE 2240  
**Problem #07**

Use the nodal analysis method to determine  $V_x$  and  $I_y$ .



$$V_1 = 5 I_y \quad (\text{constraint equation for supernode \#1})$$

$$V_3 = 100 \text{ V} \quad (\text{constraint equation for supernode \#2})$$

$$V_4 = 0.2 V_y \quad (\text{constraint equation for supernode \#3})$$

$$\frac{V_2 - V_1}{45 \Omega} - 0.02 V_x + \frac{V_2 - V_3}{30 \Omega} + \frac{V_2 - V_4}{50 \Omega} = 0 \quad (\text{KCL at node 2})$$

$$V_x = V_4 - V_3 \quad (\text{control variable definition})$$

$$V_y = V_4 - V_2 \quad (\text{control variable definition})$$

$$I_y = \frac{V_4 - V_2}{50 \Omega} \quad (\text{control variable definition})$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -5 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & -0.2 & 0 \\ -1/45 & 17/225 & -1/30 & -1/50 & -0.02 & 0 & 0 \\ 0 & 0 & 1 & -1 & 1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & 1 & 0 \\ 0 & 1/50 & 0 & -1/50 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_x \\ V_y \\ I_y \end{bmatrix} = \begin{bmatrix} 0 \\ 100 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$V_x = -103.77 \text{ V} \quad , \quad I_y = -0.3774 \text{ A}$$