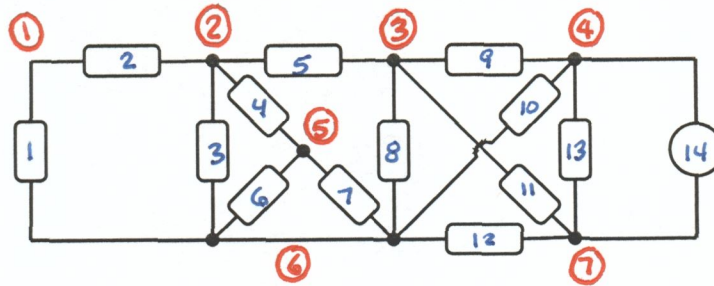


EE 2240
Problem #05



a. How many nodes does the circuit have?

7

b. How many branches does the circuit have?

14